

## EE3C11 Team exercise 5

1. Design negative feedback amplifier configurations for the transmit amplifier.
2. Design negative feedback amplifier configurations for the receive amplifier.

