

EE3C11 Team exercise 6

1. Assign values for the feedback elements of the receive amplifier of the hearing loop system, given a maximum transmitter current drive capability from the previous homework.
2. Determine the maximum values for the equivalent-input noise voltage spectral density and the equivalent-input noise current spectral density of the controller in the receiver. Ignore the noise contribution of the transmitter.

