
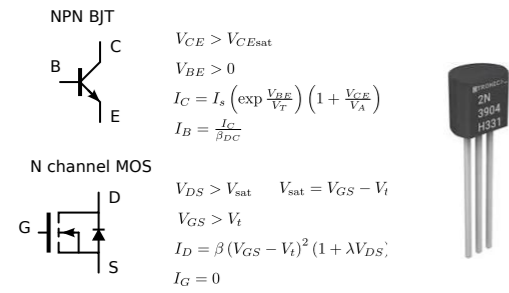






# Basic CE and CS stages

 

Voltage-controlled notation of a nonlinear two-port:




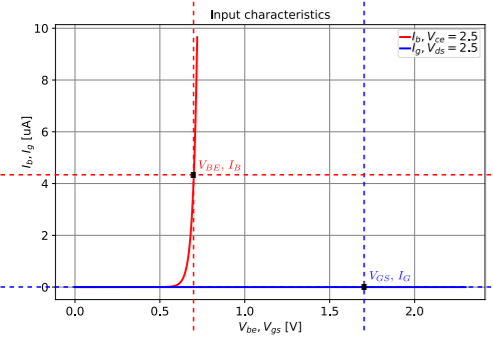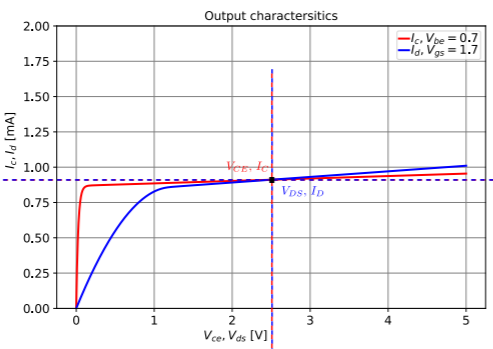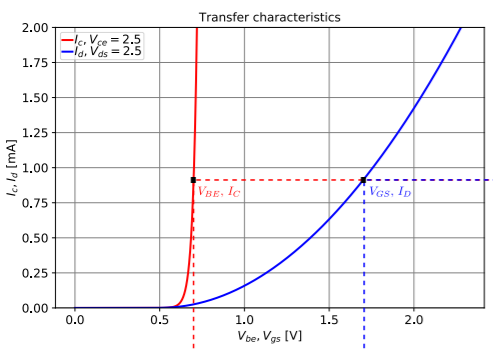 Current-controlled notation of the complementary two-port:




For processing bipolar signals:

 - Select operating point at output port:
  - Voltage and current drive capability
  - Noise performance
  - Small-signal dynamic performance



 Create zero bias conditions for the external circuitry by adding bias sources at both the input port the output port.



# Amplifier stages with discrete transistors

## Balanced stages

Obtain odd transfer characteristics

- compensation of offset
- reduction of even-order nonlinearity


Improvement of port isolation

- Four-terminal stages
- Natural two-port approximation



Implementation techniques

- Anti-series connection
- Complementary-parallel connection



## Anti-series stage

 

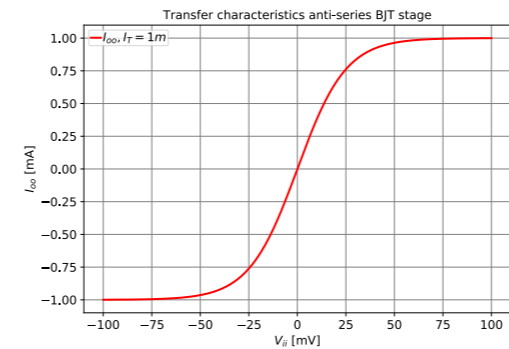 
Compressing (limiting) voltage-to-current transfer



## Small-signal model

  


## Stationary noise model

 


Consider behavioral modifications of the CE and the CS stage as the result of the application of balancing techniques.
 
# Local feedback stages

Biased transistor: the simplest implementation of the nullor




 CC-stage (BJT) of CD stage (FET): Nonenergic, non-inverting, unity-gain, negative feedback voltage amplifier (voltage follower)



Use asymptotic-gain feedback model to evaluate the effect of feedback: See example capacitively loaded CC-stage with 2N3904.

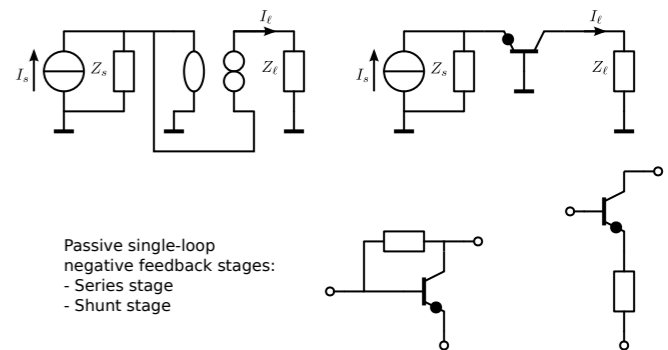CB-stage (BJT) of CG stage (FET): Nonenergic, non-inverting, unity-gain, negative feedback current amplifier (current follower)




Passive single-loop negative feedback stages:

- Series stage
- Shunt stage

## Implementation of biasing: redirect current sources over the power supply

 Example with grounded device and single supply:



$I_{OQ}$  Determines maximum positive (sourcing) output current.  
 $V_{OQ}$  Determines maximum negative (sinking) output voltage.

Voltage sources (level shifts):

- Absorbed in external circuitry
- Replace with capacitors (AC coupling)
- Implemented with current sources and (nonlinear) resistors


Current sources implemented with:

- Voltage reference and low-noise transmittance amplifiers
- Replace with inductors (AC coupling)
- Implemented with (nonlinear) resistors

Temperature stability and sensitivity for device tolerances  
 Use error-reduction techniques to improve the accuracy of the biasing:

- Negative feedback biasing (if frequencies of interest to not include zero)
- Auto-zero techniques
- Compensation techniques
 
## Modeling of the small-signal dynamic behavior and stationary noise behavior in the operating point.



Relate small-signal parameters to device parameters and operating conditions

BJT	MOS
$r_i = \frac{\beta_{AC}}{g_m}$	$r_i = \infty$
$g_m = \frac{I_C}{V_T}$	$g_m = 2\sqrt{\beta I_D}$
$r_o = \frac{V_{CE} + V_A}{I_C}$	$r_o = \frac{1}{\lambda I_D}$
$c_i = \frac{I_C}{V_T} \tau_F + C_{JE}$	$c_i = \frac{2}{3} C_{OX}$
$c_r = C_{JC}$	$c_r = C_{DG}$
$S_{in1} = 2qI_B$	$c_o = C_{DB} + C_{SB}$
$S_{in0} = 2qI_C$	$S_{in1} = 2qI_G$
$\beta_{AC} = \frac{\partial I_C}{\partial I_B}$ = small-signal current gain	$S_{in0} = 4kT \frac{2}{3} g_m$
$\tau_F$ = forward transit time	$f_T = \frac{1}{2\pi} \frac{g_m}{c_i + c_r}$
$C_{JC}$ = collector-base junction depletion capacitance	$C_{OX}$ = oxide capacitance
$C_{JE}$ = emitter-base junction depletion capacitance	$C_{DG}$ = drain-gate overlap capacitance
	$C_{DB}, C_{SB}$ = drain-bulk and source-bulk junction capacitances, respectively

## T1 matrix parameters

$$\mu = \frac{1}{A} = -g_m r_o \frac{1 - s \frac{c_r}{g_m}}{1 + s r_o (c_o + c_r) + r_i (c_i + c_r (1 + g_m r_o)) + s^2 r_i r_o (c_i c_o + (c_i + c_o) c_r)}$$


$$\zeta = \frac{1}{C} = -g_m r_i r_o \frac{1 - s \frac{c_r}{g_m}}{1 + s r_o (c_o + c_r) + r_i (c_i + c_r (1 + g_m r_o)) + s^2 r_i r_o (c_i c_o + (c_i + c_o) c_r)}$$

$$\gamma = \frac{1}{B} = -g_m \left( 1 - s \frac{c_r}{g_m} \right)$$



$$\alpha = \frac{1}{D} = -g_m r_i \frac{1 - s \frac{c_r}{g_m}}{1 + s r_i (c_i + c_r)}$$

Miller effect



## Complementary-parallel stage

 

Expanding voltage-to-current transfer

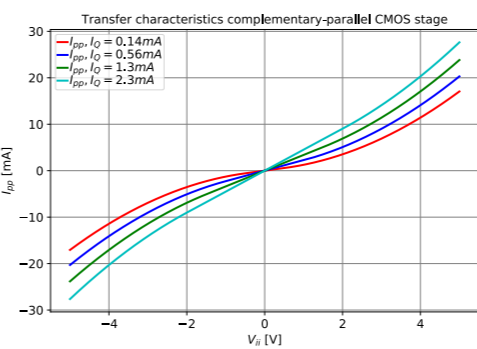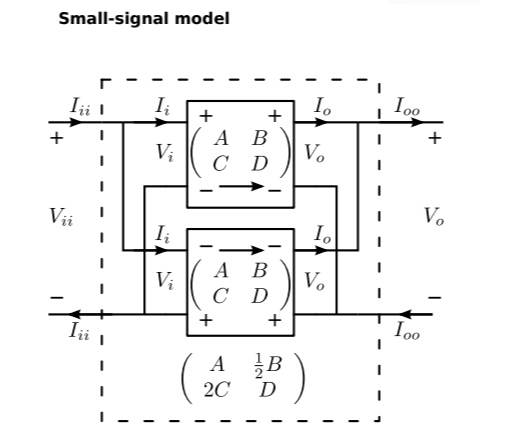

## Stationary noise model

  


Consider behavioral modifications of the CE and CS stage as the result of the application of negative feedback and/or balancing techniques.

High loop gain:  
 Large change of the behavior compared with the basic stage:

- Improved accuracy
- Decreased weak nonlinearity
- Increased bandwidth
- Series feedback at a port: increased port impedance
- Parallel feedback at a port: decreased port impedance
- Noise as with feedback amplifiers: input referred noise sources: at best equal to those of basic stage
- Drive capability, power efficiency and energy storage as with feedback amplifiers: at best equal to those of basic stage
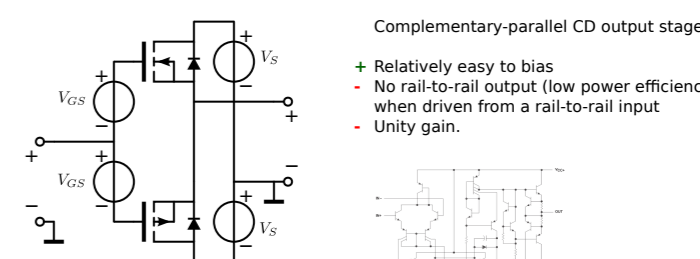
## Combination of balancing and negative feedback



Complementary-parallel CD output stage


- + Relatively easy to bias
- No rail-to-rail output (low power efficiency) when driven from a rail-to-rail input
- Unity gain.

## Indirect feedback stages

Indirect sensing: Sense a copy of the load quantity

Indirect comparison: Compare feedback quantity with a copy of the source quantity

 Current mirror: Inverting, indirect feedback unity-gain current amplifier



Voltage mirror: Inverting, indirect feedback unity-gain voltage amplifier

Indirect voltage comparison: No increase of input impedance