

# Analog filters

## Introduction

### Function

Here: selection in the frequency domain or correction of the response

### Application

- Anti-aliasing filters and reconstruction filters
- Frequency selection in modulation and demodulation systems
- Equalization filters for correction of the frequency-domain response of a system
- Pulse-shaping filters (e.g. in class E and F amplifiers)
- Power supply filters

### Performance measures

#### Function performance measure


- Pass-band frequency range
- Pass-band attenuation
- Stop-band frequency range
- Stop-band attenuation
- Stop-band ripple
- Phase characteristic
- Phase ripple
- ...

#### Other performance measures

- Noise performance
- Power dissipation
- Current / voltage handling capability
- Linearity
- Accuracy and temperature dependency
- ...
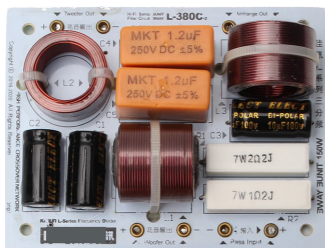
### Technology

- Passive (LRC) filters
- Active filters with discrete operational amplifiers
- Integrated circuit active filters with application-specific amplifiers
- Integrated circuit switched capacitor filters
- Integrated circuit CCD filters
- Crystal and ceramic resonator filters
- Surface Acoustic Wave (SAW) filters
- Transmission line and stripline filters
- Helical resonator filters
- Digital filters (IC, FPGA)



## LC filters


### Design form normalized low-pass prototypes

Normalized drive and/or termination resistance (1 Ohm)  
Normalized cut-off frequency (usually -3dB, 1 rad/s)

### Design by equating coefficients:

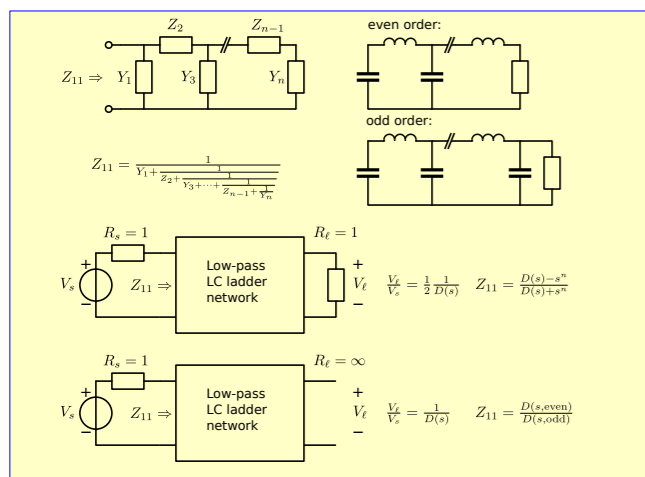
### All-pole low-pass prototypes

All-pole low-pass filter prototypes can be synthesized by Expansion of Driving-Point Impedance



### Use properties of networks to obtain alternative low-pass configurations:


Thevenin-Norton Duality Reciprocity

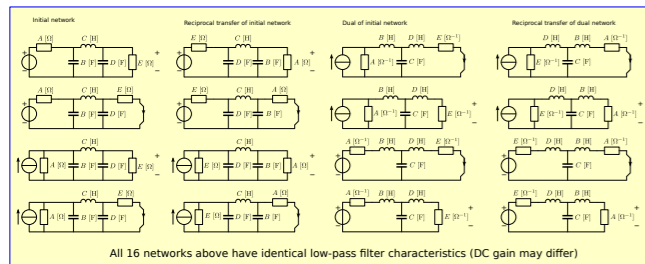
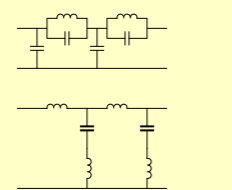
### Low-pass elliptic filter prototypes

Elliptic filters (Cauer filters) have the steepest transition from the passband to the stopband compared with other types of filters of the same order. Transmission zeros are realized with parallel resonant circuits in series with the signal path or series resonant circuits in parallel with the signal path.

Elliptic filters can be designed from their pole-zero pattern and polynomial expansion or from normalized prototypes (tables)



## Design of LC low-pass filters from prototypes

1. Obtain the desired normalized prototype either from the Expansion of Driving Point Impedance or from handbooks on filter design.
2. Denormalize the components:

$$R \Leftarrow \text{drive and/or termination resistance. } L \Leftarrow \frac{Rl}{\omega_c} \quad C \Leftarrow \frac{1}{\omega_c R}$$

## Design of LC high-pass filters from prototypes

The transfer function of a normalized high-pass filter can be obtained from that of a normalized low-pass filter by replacing  $s$  by  $1/s$  in the transfer function of the low-pass prototype.

$$\text{low-pass } s \leftrightarrow \frac{1}{s} \quad \text{high-pass } \begin{matrix} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{matrix} \Leftrightarrow \begin{matrix} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{matrix} \begin{matrix} C = \frac{1}{\omega_c} \\ L = \frac{1}{\omega_c} \end{matrix}$$

1. Obtain the desired normalized prototype either from the Expansion of Driving Point Impedance or from handbooks on filter design.
2. Replace inductors with capacitors and vice versa
  - normalized capacitor values of the high-pass filter equal the reciprocal value of the corresponding normalized inductors of the low-pass prototype and vice versa
3. Denormalize the components as described above

## Design of LC band-pass filters from prototypes

### Approach for narrow-band band-pass filters:

The transfer function of a normalized band-pass filter can be obtained from that of a normalized low-pass filter by replacing  $s$  by  $(s+1/s)/B$  in the transfer function of the low-pass prototype.

$$\text{low-pass } s \leftrightarrow \frac{1}{2B} (s + \frac{1}{s}) \quad \text{band-pass}$$

1. Obtain the desired normalized prototype either from the Expansion of Driving Point Impedance or from handbooks on filter design.
2. Denormalize the low-pass filter as indicated below
  - normalized  $3\text{-dB}$  bandwidth of the band-pass filter

$$R \Leftarrow \text{drive and/or termination resistance. } L \Leftarrow \frac{Rl}{2\pi B} \quad C \Leftarrow \frac{1}{2\pi B R}$$

3. Replace the inductors with series resonance circuits and the capacitors with parallel resonance circuits as indicated below.

$$\begin{matrix} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{matrix} \Leftrightarrow \begin{matrix} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{matrix} \begin{matrix} L \\ C = \frac{1}{4\pi^2 f_c^2 L} \end{matrix} \quad \begin{matrix} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{matrix} \Leftrightarrow \begin{matrix} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{matrix} \begin{matrix} C \\ L = \frac{1}{4\pi^2 f_c^2 C} \end{matrix}$$

## Design of LC band-stop filters from prototypes

### Approach for narrow-band band-stop filters:

The transfer function of a normalized band-stop filter can be obtained from that of a normalized high-pass filter by replacing  $s$  by  $s-1/s$  in the transfer function of the high-pass prototype.


$$\text{high-pass } s \leftrightarrow s - \frac{1}{s} \quad \text{band-stop}$$

1. Obtain the desired normalized prototype either from the Expansion of Driving Point Impedance or from handbooks on filter design.
2. Conversion of high-pass to band-reject is similar to the conversion of low-pass to band-pass.

### Tables for normalized element values can be found in books on filter design


Filter type	Filter Data Electronic Filter Design Handbook 4th ed.									
	passband attenuation	stopband attenuation	group delay	impulse response	stop response	pole locations	LC values prototype	RC values active		
Butterworth	F 2-34	F 2-34	F 2-35	F 2-36	F 2-37	T 11-1	T 11-2	T 11-2	T 11-2	T 11-21
Butterworth, uniform dissipation							T 11-3 - T 11-11			
Butterworth, lossy L network							T 11-12 - T 11-20			
Chebyshev 0.01 [dB]	F 2-41	F 2-41	F 2-46	F 2-49	F 2-50	T 11-22	T 11-27	T 11-27	T 11-27	T 11-36
Chebyshev 0.1 [dB]	F 2-42	F 2-42	F 2-47	F 2-51	F 2-52	T 11-23	T 11-28	T 11-28	T 11-28	T 11-37
Chebyshev 0.25 [dB]	F 2-43	F 2-43				T 11-24	T 11-29	T 11-29	T 11-29	T 11-38
Chebyshev 0.5 [dB]	F 2-44	F 2-44	F 2-48	F 2-53	F 2-54	T 11-25	T 11-30	T 11-30	T 11-30	T 11-39
Chebyshev 1 [dB]	F 2-45	F 2-45				T 11-26	T 11-31	T 11-31	T 11-31	T 11-40
Chebyshev 0.1 [dB], uniform dissipation							T 11-32			
Chebyshev 0.25 [dB], uniform dissipation							T 11-33			
Chebyshev 0.5 [dB], uniform dissipation							T 11-34			
Chebyshev 1 [dB], uniform dissipation							T 11-35			
Bessel	F 2-56	F 2-56	F 2-57	F 2-58	F 2-59	T 11-41	T 11-42	T 11-42	T 11-42	T 11-43
Linear phase, 0.05 degrees	F 2-61	F 2-61	F 2-63	F 2-65	F 2-66	T 11-44	T 11-46	T 11-46	T 11-46	T 11-48
Linear phase, 0.5 degrees	F 2-62	F 2-62	F 2-64	F 2-67	F 2-68	T 11-45	T 11-47	T 11-47	T 11-47	T 11-49
Transitional Gaussian to 6 [dB]	F 2-69	F 2-69	F 2-71	F 2-73	F 2-74	T 11-50	T 11-52	T 11-52	T 11-52	T 11-54
Transitional Gaussian to 12 [dB]	F 2-70	F 2-70	F 2-72	F 2-75	F 2-76	T 11-51	T 11-53	T 11-53	T 11-53	T 11-55
Synchronously tuned	F 2-77	F 2-77	F 2-78	F 2-79	F 2-80					
Elliptic (Cauer)										
Maximally flat delay with Chebyshev stopband										T 11-56

## Impedance correction

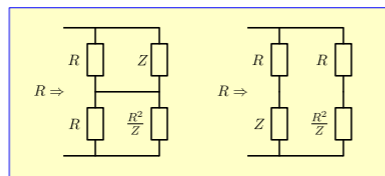

LC filters can be designed for resistive termination  
Use Zobel impedance correction for non-resistive loads.  
Correction requires dual network.
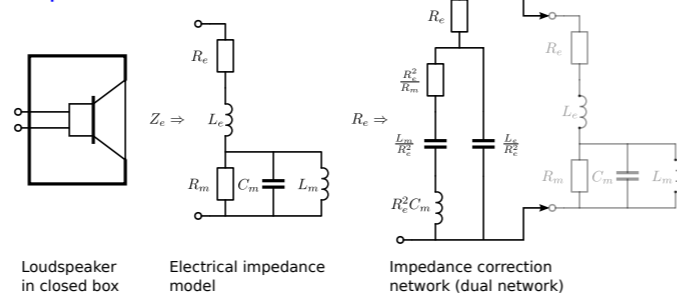
### Example correction impedance loudspeaker in closed box




## Active Filters

### Cascade connection of first, second and third order structures


- Transfer functions of cascaded sections are sensitive for component tolerances.
- Signal levels can be designed per section
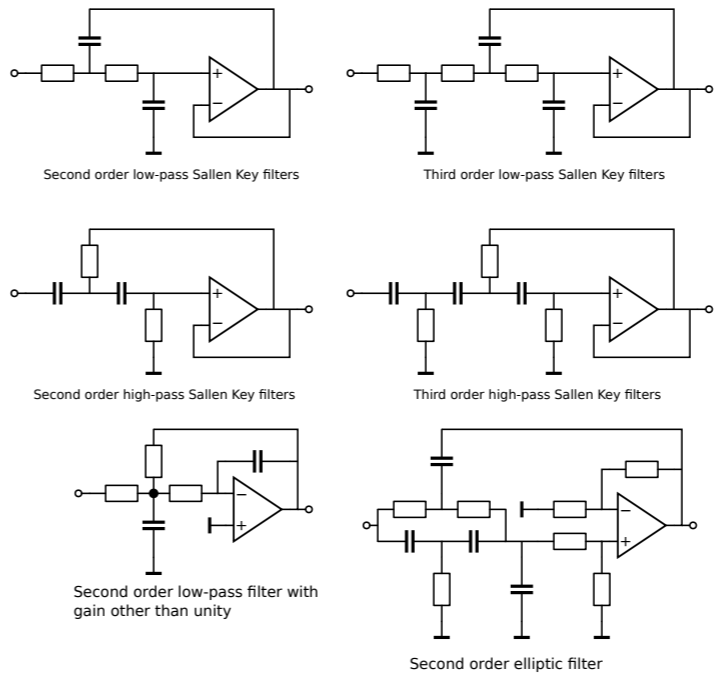
### Filter types



- Second and third order Sallen Key filters
- Design from tables (literature) or by equating coefficients
- Cascaded biquad sections
- Second order single OpAmp configurations
- Design equations found in literature
- Second order dual OpAmp configurations
- Design equations found in literature




### Two-integrator universal filter

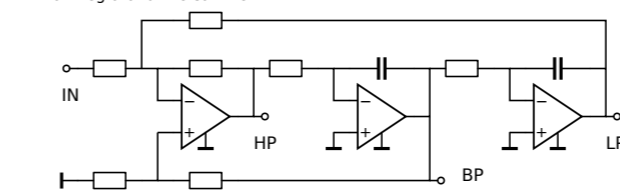

## Generalized Impedance converter

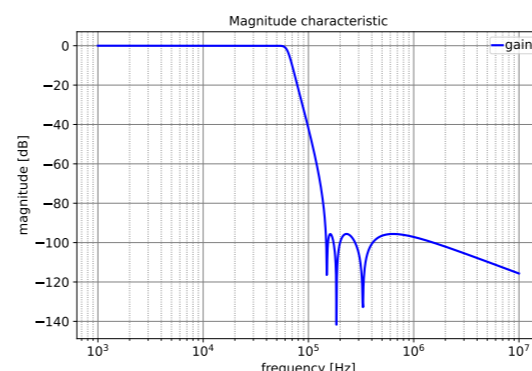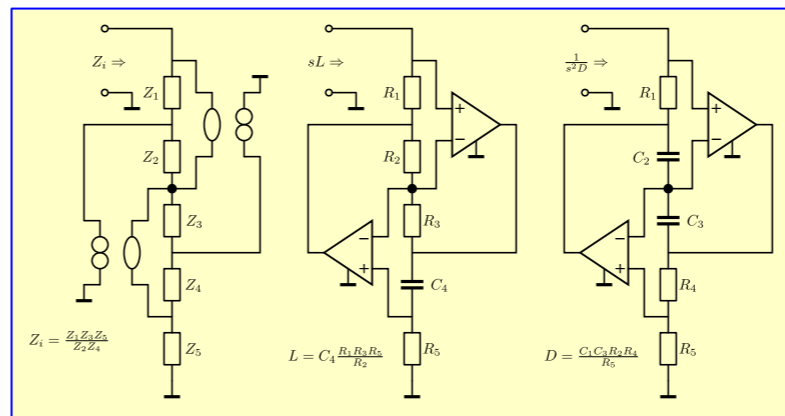

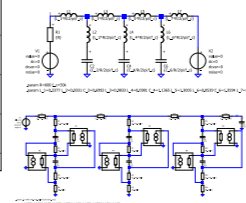Elliptic filter with D elements. Designed from reciprocal transfer of LC prototype [Zverev] Cauer n=7, rho=1%, K=inf. p. 259 no. 20. SLICAP example 50kHz -96dB anti-aliasing filter.





### Multiple feedback structures of arbitrary order



- Less sensitive to component tolerances
- Different signal levels at the various stages may seriously limit the dynamic range of the filter.
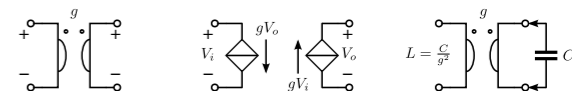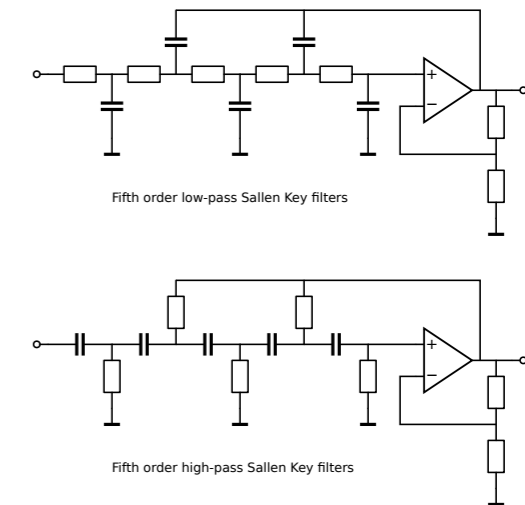
### Filter types

- Multiple-loop Sallen-Key filters
- Design from tables or by equating coefficients
- GIC filters
- Design from LC prototypes, convert R to C, L to R and C to D element.
- Gyration filters
- Design from LC prototypes, replace inductors with gyrator and capacitor
- Direct implementations of the transfer function
- Structures of which the element values show a simple relation to the coefficients of the transfer function



## Synthesis from the transfer function

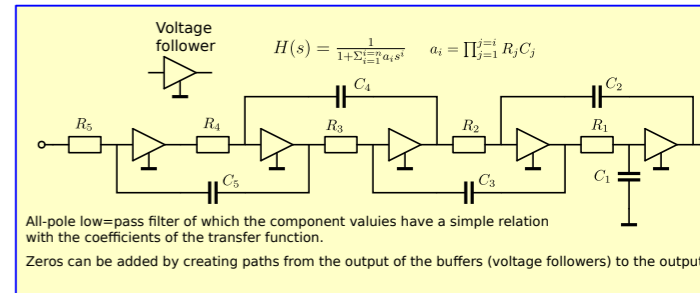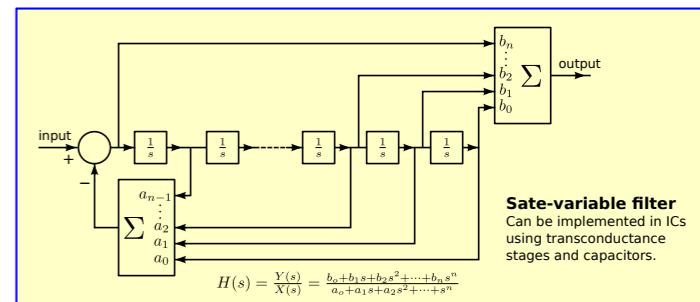

## Other Filters

### Switched Capacitor Filters

### Surface Acoustic Wave filters

### Crystal filters

### Delay line filters