

# Design of the amplifier's source-load transfer


## Amplification

### Information processing task


Accurately copy the source information, while increasing the available signal power
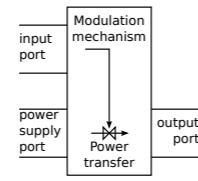
### Operating principle

The source signal modulates the power transfer from the power supply to the load


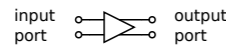
### Selection of electrical input and output quantity




### Sensor and actuator interfacing

The electrical input quantity of an amplifier should show the best possible correspondence with the source information


The electrical output quantity of an amplifier should show the best possible correspondence with the load information

Source and load, and input and output impedances can only be part of the transfer if accurately known

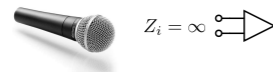
The voltage generated by a microphone is accurately related to the sound pressure



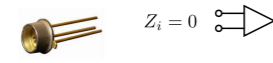
The current generated by a PIN diode is accurately related to the optical power



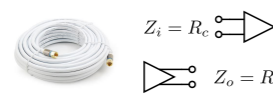A transmission line shows no reflections when driven from and terminated with its characteristic impedance



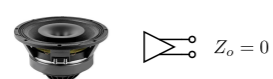The sound pressure generated by a loudspeaker is accurately related to the applied voltage




The force generated by a piezo actuator is accurately related to the electrical charge




### Signal addition, distribution, testability

Addition of currents

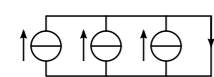

Distribution of voltages

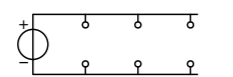

### Amplifier types


#### Port impedances

amplifier type	source quantity	load quantity	Zi	Zo
Voltage amplifier	voltage	voltage	∞	0
Transadmittance	voltage	current	∞	∞
Voltage to V/I	voltage	voltage or current	∞	Zo
Transimpedance	current	voltage	0	0
Current amplifier	current	current	0	∞
Current to V/I	current	voltage or current	0	Zo
V/I to voltage	voltage or current	voltage	Zi	0
V/I to current	voltage or current	current	Zi	∞
V/I to V/I	voltage or current	voltage or current	Zi	Zo

9 unilateral types:  
input impedance independent of load impedance  
output impedance independent of source impedance

### Amplifier types

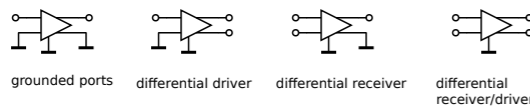
#### Port configuration and common-mode port impedances




	grounded ports	differential driver	differential receiver	differential receiver/driver
Zicm	0	∞	Rc	Rc
Zocm	0	∞	Rc	Rc
Number of types	9	27	27	81
Total 144 (unilateral) amplifier types				

### Amplifier functional model

#### Modeling of the ideal behavior

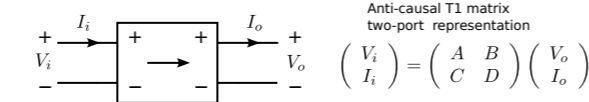

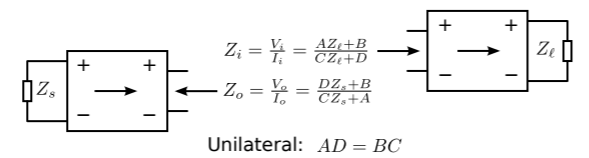Model for differential-mode and for common-mode behavior



### Design of amplifier types

amplifier type	Zi	Zo	A	B	C	D
Voltage amplifier	∞	0	A	0	0	0
Transadmittance amplifier	∞	∞	0	B	0	0
Voltage input, finite nonzero output impedance	∞	Zo	A	B	0	0
Transimpedance amplifier	0	0	0	0	C	0
Current amplifier	0	∞	0	0	0	D
Current input, finite nonzero output impedance	0	Zo	0	0	C	D
Finite nonzero input impedance, voltage output	Zi	0	A	0	0	0
Finite nonzero input impedance, current output	Zi	∞	0	B	0	D
Finite nonzero input and output impedance	Zi	Zo	A	B	C	D

### Design of port impedances

The input impedance should be designed such that the electrical input quantity accurately represents the source information

The output impedance should be designed such that the electrical output quantity accurately represents the load information


### Brute-force techniques

Tune the port impedance to its desired value through insertion of an impedance in series or in parallel with the port

Pros	Cons
Simple	At input port: Reduction of SNR At output port: Reduction of power efficiency
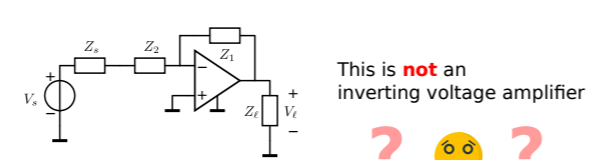
### Design of high-performance amplifiers

Thou shalt not insert impedances in series or in parallel with the signal path!



### Feedback techniques

Cons	Pros
Less simple	Allows orthogonal design of performance aspects Performance primarily set by feedback network that does not need an available power gain larger than unity.

### Design of amplifier types using negative feedback

- Sense the load quantity of interest  
Sensing of a voltage: in parallel with the load (output parallel feedback)  
Sensing of a current: in series with the load (output series feedback)


- Convert it into a copy of the source quantity  
The feedback network converts the load signal of the amplifier into a copy of the source signal

- Nullify the difference between the source quantity and its copy by controlling the load quantity

Comparison of voltages: anti-series connection of source voltage and feedback voltage (input series feedback)

Comparison of currents: anti-parallel connection of source current and feedback current (input parallel feedback)

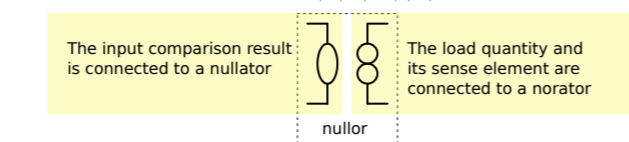
The nullor is the ideal controller  $(\begin{matrix} V_i \\ I_i \end{matrix}) = \begin{pmatrix} 0 & 0 \\ 0 & 0 \end{pmatrix} (\begin{matrix} V_o \\ I_o \end{matrix})$  **Tellegen 1954**


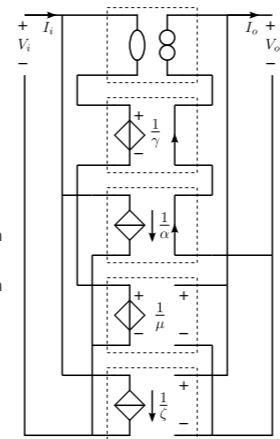
### Synthesis of Feedback Amplifiers

Each T1 matrix parameter fixed with one feedback loop.

- parallel sensing series comparison
- series sensing series comparison parallel sensing parallel comparison
- series sensing parallel comparison
- series sensing parallel comparison



16 combinations:  
- 9 unilateral  
- 6 non-unilateral  
- nullor


Type	A	B	C	D
Nullor	0	0	0	0
Voltage amplifier (unilateral)	1/μ	0	0	0
Transadmittance amplifier (unilateral)	0	1/γ	0	0
Transimpedance amplifier (unilateral)	0	0	1/κ	0
Current amplifier (unilateral)	0	0	0	1/α
Zi = β/γ, Zo = ∞ (unilateral)	0	1/γ	0	0
Zi = β/μ, Zo = 0 (unilateral)	1/μ	0	1/κ	0
Zi = 0, Zo = β/α (unilateral)	0	0	1/κ	1/α
Zi = ∞, Zo = β/γ (unilateral)	1/μ	1/γ	0	0
Transformer-like amplifier (non-unilateral)	0	1/γ	1/κ	0
Gyrator-like amplifier (non-unilateral)	0	1/γ	1/κ	0
Triple loop 1 (non-unilateral)	1/μ	1/γ	1/κ	0
Triple loop 2 (non-unilateral)	1/μ	1/γ	0	1/α
Triple loop 3 (non-unilateral)	1/μ	0	1/κ	1/α
Triple loop 4 (non-unilateral)	0	1/γ	1/κ	1/α
Quadruple loop	1/μ	1/γ	1/κ	1/α

### Ideal gain

Source-load transfer of a feedback amplifier in which all controllers are replaced with nullors
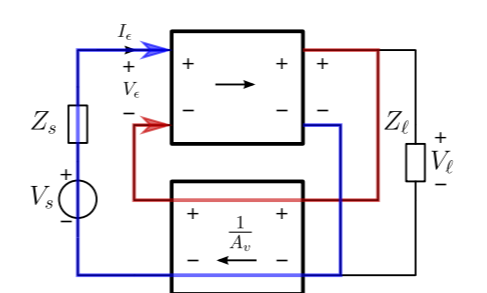
### Negative feedback

- Corrective feedback
- Controller = high-gain error amplifier
- Odd number of minus signs in the loop transfer




### Synthesis of Common-mode impedances

In the case of zero common-mode source-load transfer

- Transformer coupling
- Brute-force technique
- Common-mode feedback on a port

- Else also:
- Over-all common-mode feedback

### SPICE nullor subcircuit

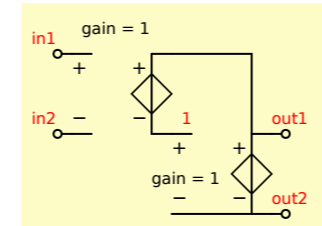

```
.subckt nullor out1 out2 in1 in2
E1 out1 in1 in2 1
E2 out2 in1 in2 1
.ends
```


### Nonenergetic feedback

Feedback networks are nonenergetic:


- no energy storage
- no losses

Nonenergetic network elements:

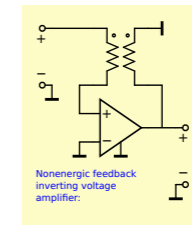
- Transformer
- Gyrator
- Open circuit
- Short circuit



### Passive feedback

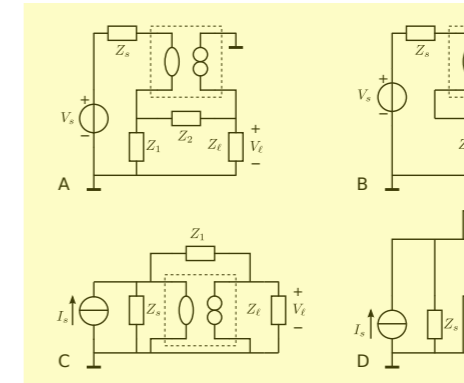


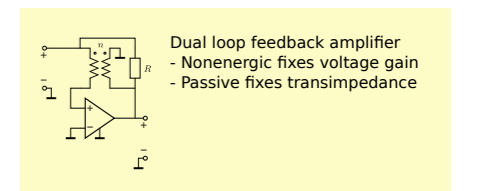Properties of nonenergetic feedback amplifiers:  
No noise performance degradation due to feedback network  
No power efficiency degradation due to feedback network




Single-loop passive feedback amplifiers with grounded source and load:

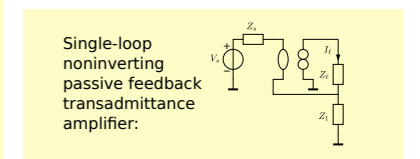- A: Voltage amplifier  $V_o/V_s = \frac{Z_1+Z_2}{Z_1}$
- B: Transadmittance amplifier  $I_o/V_s = -\frac{1}{Z_1}$
- C: Transimpedance amplifier  $V_o/I_s = -Z_1$
- D: Current amplifier  $I_o/I_s = \frac{Z_1+Z_2}{Z_1}$




### Active feedback

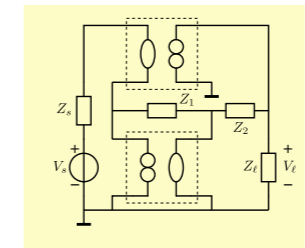

Active feedback  
Inverting voltage amplifier


Nullators and norators can be paired differently

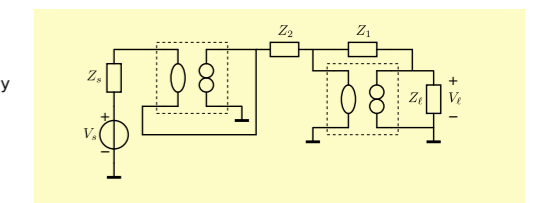There exists no relation between nullators and norators:  
- Nullator sets network condition  
- Norator introduces a free variable to satisfy this condition



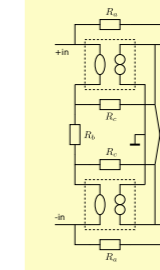
### Balanced feedback

Balanced amplifiers can be obtained through anti-series connection of unbalanced amplifiers  
Cross coupling can be used for sign inversion of a differential-mode transmission coefficient




Differential-mode cross coupling does not affect the common-mode feedback.  
Extra measures need to be taken to prevent positive common-mode feedback
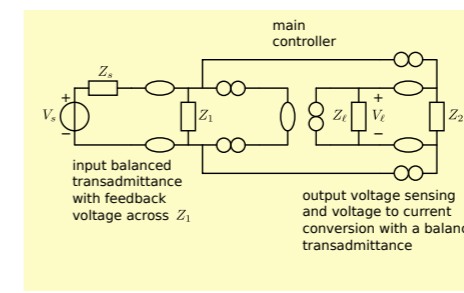
### Balanced feedback with improved port isolation



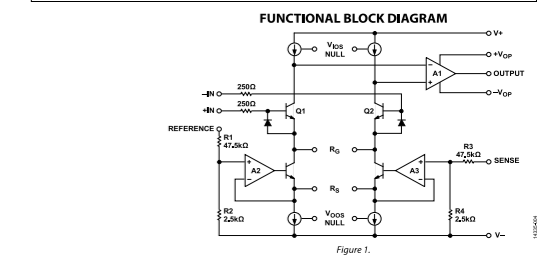
### ANALOG DEVICES Low Noise, Precision Instrumentation Amplifier AMP01



Protected under U.S. Patents 4,471,321 and 4,503,381.
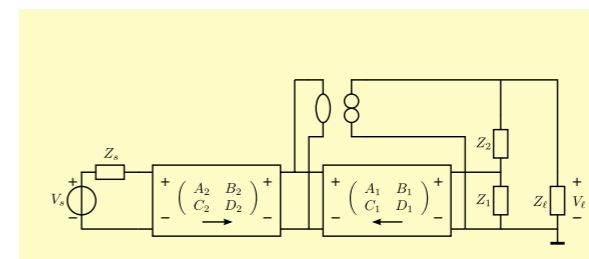
### Indirect (model-based) feedback

Instrumentation amplifier with indirect voltage comparison



Inverting current amplifier with indirect current sensing

