


The Oscilloscope Probe

A SLiCAP demonstration of the analysis of linear dynamic circuits

Circuit data

Circuit diagram


Component model

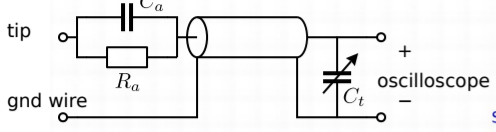

Voltage attenuation at low frequencies determined by R_a and the input resistance of the oscilloscope.

Voltage attenuation at high frequencies determined by C_a , C_b , the cable capacitance, and the input capacitance of the oscilloscope.

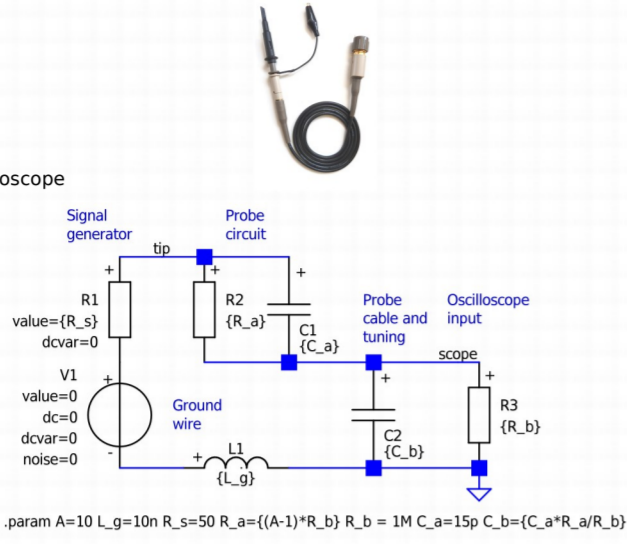C_t should be tuned for equal attenuation at low and high frequencies.



.param A=10 L_g=10n R_s=50 R_a=((A-1)*R_b) R_b = 1M C_a=15p C_b=(C_a*R_a/R_b)

Netlist: ProbeSymbolic.cir

```
"ProbeSymbolic"
* Z:\mnt\DATA\www\SEDwebsite\_build\SLiCAPprojects\ProbeCircuit\cir\ProbeSymbolic.asc
C1 tip scope {C_a}
C2 scope 0 {C_b}
R2 tip scope {R_a}
R3 scope 0 {R_b}
V1 P001 N001 V value=0 dc=0 dcvar=0 noise=0
L1 N001 0 {L_g}
R1 tip P001 r value={R_s} dcvar=0
* Signal generator
* Probe circuit
* Oscilloscope input
* Probe cable and tuning
* Ground wire
.param A=10 L_g=10n R_s=50 R_a=((A-1)*R_b) R_b = 1M C_a=15p C_b=(C_a*R_a/R_b)
.backanno
.end
```

Table: Element data of expanded netlist 'ProbeSymbolic'

RefDes	Nodes	Refs	Model	Param	Symbolic	Numeric
C1	tip scope	C	value	C_a	$1.5 \cdot 10^{-11}$	
C2	scope 0	C	value	C_b	$1.35 \cdot 10^{-10}$	
L1	N001 0	L	value	L_g	$1.0 \cdot 10^{-8}$	
R1	tip P001	r	value	R_s	50.0	
			dcvar		0	
R2	tip scope	R	value	R_a	$9.0 \cdot 10^6$	
R3	scope 0	R	value	R_b	$1.0 \cdot 10^6$	
V1	P001 N001	V	value		0	
			dc		0	
			dcvar		0	
			noise		0	

Table: Parameter definitions in 'ProbeSymbolic'.

Name	Symbolic	Numeric
A	10	10
C_a	$1.5 \cdot 10^{-11}$	$1.5 \cdot 10^{-11}$
C_b	$\frac{C_a R_a}{R_b}$	$1.35 \cdot 10^{-10}$
L_g	$1.0 \cdot 10^{-8}$	$1.0 \cdot 10^{-8}$
R_a	$R_b (A - 1)$	$9.0 \cdot 10^6$
R_b	$1.0 \cdot 10^6$	$1.0 \cdot 10^6$
R_s	50	50.0

Go to ProbeSymbolic_index

SLiCAP: Symbolic Linear Circuit Analysis Program, Version 1.1 © 2009-2022 SLiCAP development team
For documentation, examples, support, updates and courses please visit: analog-electronics.eu
Last project update: 2022-02-10 13:29:16

Perform symbolic analysis and create HTML reports

```
#####
#
# Symbolic matrix equation
#
#####
# Create an HTML page to display the results
htmlPage("MNA matrix equation")
head2html("Circuit diagram")
img2html("probe.jpg", 100)
img2html(fileName + ".svg", 500)
# Put some text on the HTML page
text2html("The MNA matrix equation of the circuit is:")
i1.setGainType('vi')
i1.setDataTypes('matrix')
result = i1.execute()
matrices2html(result)
#####
# Symbolic analysis of the Laplace transfer of the gain
#
#####
# Create an HTML page to display the results
htmlPage("Symbolic Laplace Transform")
head2html("Circuit diagram")
img2html("probe.jpg", 100)
img2html(fileName + ".svg", 500)
# Define the source and the detector, and the gain type.
i1.setSource('V1')
i1.setDetector('V_scope')
i1.setGainType('gain')
# Laplace transform of the transfer
i1.setSimType('symbolic')
i1.setDataTypes('laplace')
result = i1.execute()
symbolic_laplace = result.laplace
text2html("The Laplace Transform of the transfer  $\frac{V_{scope}}{V_s}$  is:")
eqn2html("V_scope/V_s", symbolic_laplace)
# Let's see the expression for in case the probe is calibrated
text2html("If the probe is correctly calibrated, we substitute:")
eqn2html(C_b, C_a*R_a/R_b)
text2html("The expression of the transfer then simplifies to:")
# Use sympy substitution
symbolic_laplace_calibrated = symbolic_laplace.subs(C_b, C_a*R_a/R_b)
eqn2html("V_scope/V_s", symbolic_laplace_calibrated)
text2html("If we factorize this result we obtain:")
# Use sympy factorization
symbolic_laplace_calibrated = sp.factor(symbolic_laplace_calibrated)
eqn2html("V_scope/V_s", symbolic_laplace_calibrated)
text2html("If we normalize this result, we obtain:")
# Use the SLiCAP "normalizeRational" function to see the DC transfer and the
# frequency-dependent part
symbolic_laplace_calibrated = normalizeRational(symbolic_laplace_calibrated)
eqn2html("V_scope/V_s", normalizeRational(symbolic_laplace_calibrated))
```

Define variables in a separate file

Values for 10x 15pF probe (350MHz @ 500hm)

```
attn = 10
R_scope = 1e6
C_scope = 20e-12

R_src = 50
L_gnd = 12e-9
C_cable = 100e-12
C_tune = 30e-12

R_a = R_scope*(attn - 1)
C_a = (C_cable + C_scope + C_tune)/(attn - 1)
C_b = C_cable + C_scope + C_tune

SHOW = False
```

Create a project, an instruction, and a circuit

```
from SLiCAP import *
import values

prj = initProject('Probe project')
fileName = 'ProbeNumeric'
# Create an instance of the instruction object
i1 = instruction()
# Define the circuit for this instruction and check its
i1.setCircuit(fileName + '.cir')
```

Define your own Python Objects and Functions

```
def stepParam(stepParameter):
    if stepParameter == 'cal':
        # Define and enable stepping of calibration +/- 25%
        i1.setStepVar('C_b')
        i1.setStepStart(0.75*C_b_comp)
        i1.setStepStop(1.25*C_b_comp)
        i1.setStepNum(3)
        i1.setStepMethod('lin')
        i1.stepOn()

    elif stepParameter == 'gnd':
        # Define and enable stepping of ground wire inductance
        i1.setStepVar('L_g')
        i1.setStepStart(10e-9)
        i1.setStepStop(1e-6)
        i1.setStepNum(5)
        i1.setStepMethod('log')
        i1.stepOn()

    elif stepParameter == 'src':
        # Define and enable stepping of source resistance
        i1.setStepVar('R_s')
        i1.setStepStart(10)
        i1.setStepStop(1e3)
        i1.setStepNum(5)
        i1.setStepMethod('log')
        i1.stepOn()

    else:
        i1.stepOff()

stepDict = {'cal': 'calibration', 'gnd': 'ground wire inductance',
            'src': 'source resistance'}
```

The 1-rst order ($R_s = 0$) detuned unit step response is found as:

$$\mu_t = \frac{R_b}{R_a + R_b} - \frac{(-C_a R_a^2 R_b + C_b R_a R_b^2) e^{-\frac{t(R_a + R_b)}{R_a R_b (C_a + C_b)}}}{R_a R_b (C_a + C_b) (R_a + R_b)} \quad (1)$$

The 1-rst order ($R_s \neq 0$, $C_b = C_a \frac{R_a}{R_b}$) tuned unit step response is found as:

$$\mu_t = \frac{R_b}{R_a + R_b + R_s} - \frac{R_b e^{-\frac{t(R_a + R_b + R_s)}{C_a R_a R_s}}}{R_a + R_b + R_s} \quad (2)$$


The settling error to the final value of a wrongly tuned probe can be written as a function of time:

$$\epsilon_t = \frac{(C_a R_a - C_b R_b) e^{-\frac{t(R_a + R_b)}{R_a R_b (C_a + C_b)}}}{(C_a + C_b) (R_a + R_b)} \quad (3)$$


After equating this value with a 1 LSB error, we find the settling time as function of the relative positive detuning δ of C_b :

$$\tau_s = \frac{9 C_a R_b (9\delta + 10) \log\left(\frac{9 \cdot 2^n \delta}{9\delta + 10}\right)}{10} \quad (4)$$

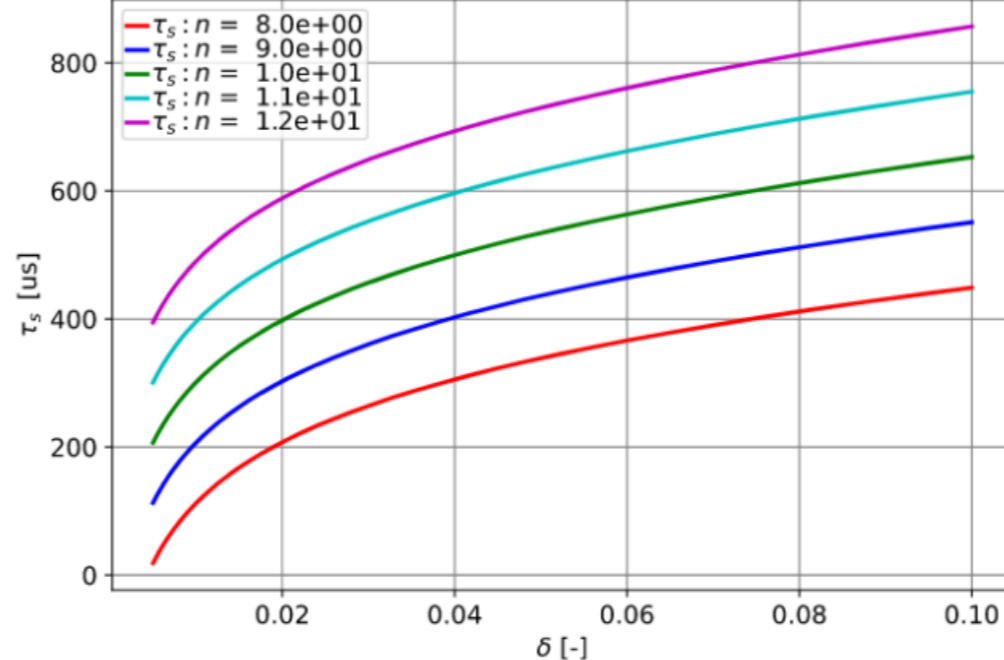
settling time as a function of the relative positive detuning




Poles versus ground wire inductance

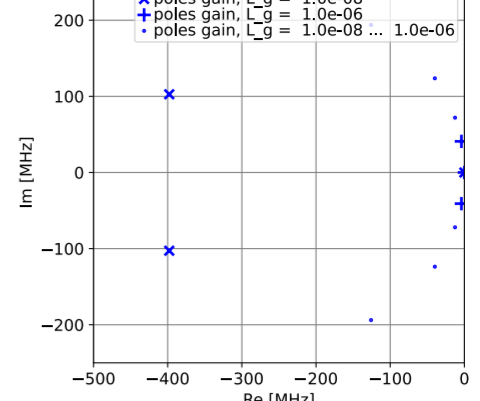

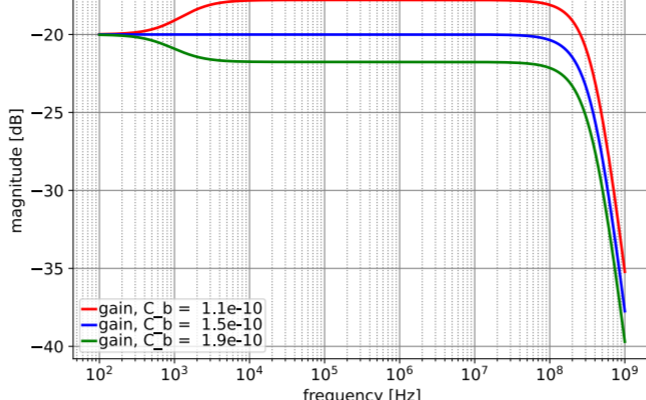
dB magnitude characteristics versus calibration




characteristics versus source resistance

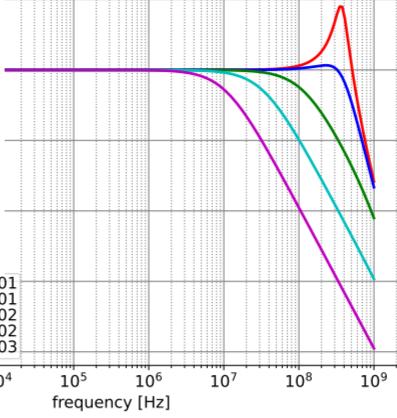

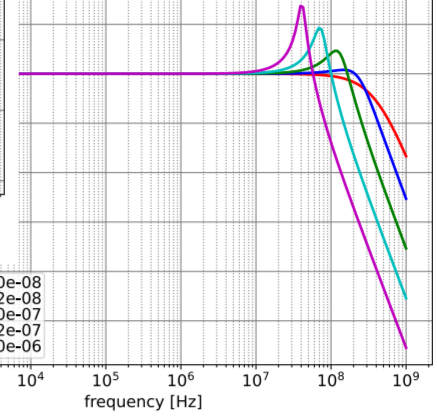
characteristics versus ground wire inductance




Unit step response versus calibration

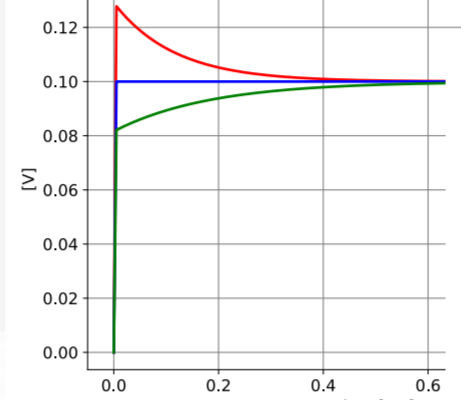

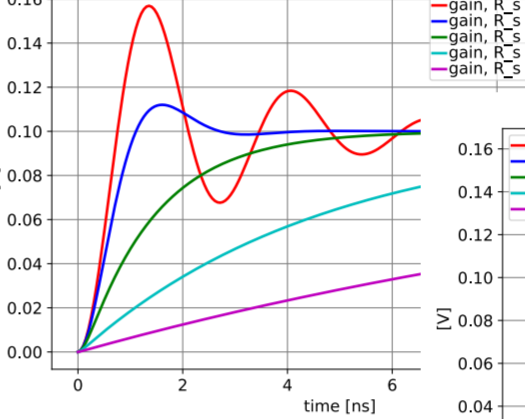Unit step response versus source resistance



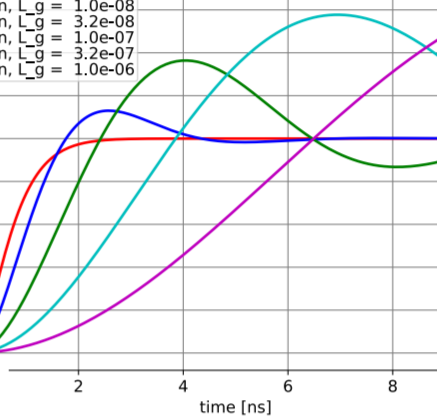Unit step response versus ground wire inductance



Display the circuit data on an HTML page

```
htmlPage("Circuit data")
head2html("Circuit diagram")
img2html("probe.jpg", 100)
img2html(fileName + ".svg", 500)
netlist2html(fileName + ".cir")
elementData2html(i1.circuit)
params2html(i1.circuit)
```

Define the source, the detector, and the gain type

```
i1.setSource('V1')
i1.setDetector('V_scope')
i1.setGainType('gain')
```

Create plots and place them in your HTML report

```
#####
#
# Frequency response versus detuning, wire inductance, and source resistance
#
#####
htmlPage('Frequency response')
head2html("Circuit diagram")
img2html("probe.jpg", 100)
img2html(fileName + ".svg", 500)
i1.setDataTypes('laplace')
for par in stepParams:
    head2html("Frequency response versus " + stepDict[par])
    stepParam(par)
    result = i1.execute()

    plotMag = plotSweep('dBmagProbe_' + par, 'dB magnitude characteristics ' +
        'versus ' + stepDict[par],
        result, 100, 1e9, 200, funcType='dBmag',
        show=values.SHOW)

    plotPhs = plotSweep('phaseProbe_' + par, 'Phase characteristics ' +
        'versus ' + stepDict[par], result,
        100, 1e9, 200, funcType='phase', show=values.SHOW)

    plotDly = plotSweep('delayProbe_' + par, 'Delay characteristics ' +
        'versus ' + stepDict[par], result,
        100, 1e9, 200, funcType='delay', show=values.SHOW)

    plotDlyZoom = plotSweep('delayProbeZoom_' + par, 'Delay characteristics ' +
        'versus ' + stepDict[par], result, 1e6, 1e9, 200,
        funcType='delay', show=values.SHOW)

    fig2html(plotMag, 600)
    fig2html(plotPhs, 600)
    fig2html(plotDly, 600)
    fig2html(plotDlyZoom, 600)
```

What is SLiCAP

- SLiCAP is an acronym for: S ymbolic L i near C ircuit A nalysis P rogram
- SLiCAP is a tool for algorithm-based analog design automation
- SLiCAP is intended for setting up and solving design equations of electronic circuits
- SLiCAP is an open source application written in Python and maxima CAS
- SLiCAP is part of the tool set for teaching 'Structured Electronic Design' at the Delft University of Technology

Why should you use SLiCAP

- SLiCAP facilitates analog design automation
- SLiCAP speeds up the circuit engineering process
- SLiCAP makes complex symbolic math doable
- SLiCAP integrates documentation and design
- SLiCAP facilitates design education and knowledge building

Features

- Accepts SPICE-like netlists as input
- Concurrent design and documentation
- Supports and facilitates structured analog design

Capabilities

- Conversion of hierarchically structured SPICE netlist into mixed symbolic/numeric matrix equation
- Symbolic and numeric noise analysis
- Symbolic and numeric noise integration over frequency
- Symbolic and numeric determination of transfer functions and polynomial coefficients of transfer functions
- Symbolic and numeric determination of the Routh array
- Symbolic and numeric inverse Laplace Transform
- Symbolic and numeric determination of network solutions
- Accurate numeric pole-zero analysis
- Root-locus analysis with a arbitrarily selected circuit parameters as root locus variable(s)
- Symbolic and numeric DC and AC variance analysis for determination of budgets for resistor tolerances and offset and bias quantities
- Symbolic and numeric derivation and solution of design equations for bandwidth, frequency response, noise performance, dc variance and temperature stability

Technology

- Python, Maxima CAS, HTML, CSS, LaTeX, MathJax, Python, Jupyter Lab