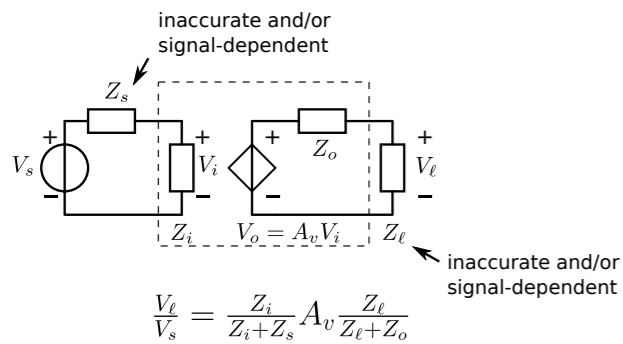


Application of negative feedback

Application of negative feedback

1. Amplification mechanism found in biased amplifying devices suffers from numerous imperfections
2. We need error reduction techniques to improve the performance-to-cost ratio


Example: The effects of **brute-force** reduction of the influence of source and load impedance variations on the accuracy of the transfer of a voltage amplifier



Negative (corrective) feedback

- Makes the properties of the amplifier less dependent on those of the biased amplifying devices
- Uses an accurate feedback network as reference for the transfer
- Allows the use of a feedback network with an available power gain equal or less than unity
- * Accurate (passive) components available for the feedback network
- Strongly facilitates **orthogonal** design of performance aspects

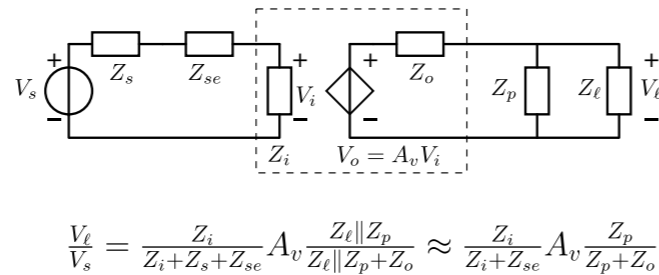Brute-force: Insert **dominant**, high-accuracy and linear impedances in the signal path:



Remember: Thou shalt not insert impedances in series or in parallel with the signal path

Conclusion: If you do: strong interaction between:


- accuracy and noise addition
- accuracy and power inefficiency
- accuracy and source-to-load transfer

- At the source: reduction of the signal to noise ratio
- At the load: decrease of power efficiency
- Source-to-load transfer: reduced as a result of attenuation

The House Of Quality

an application of:

Quality
Function
Deployment

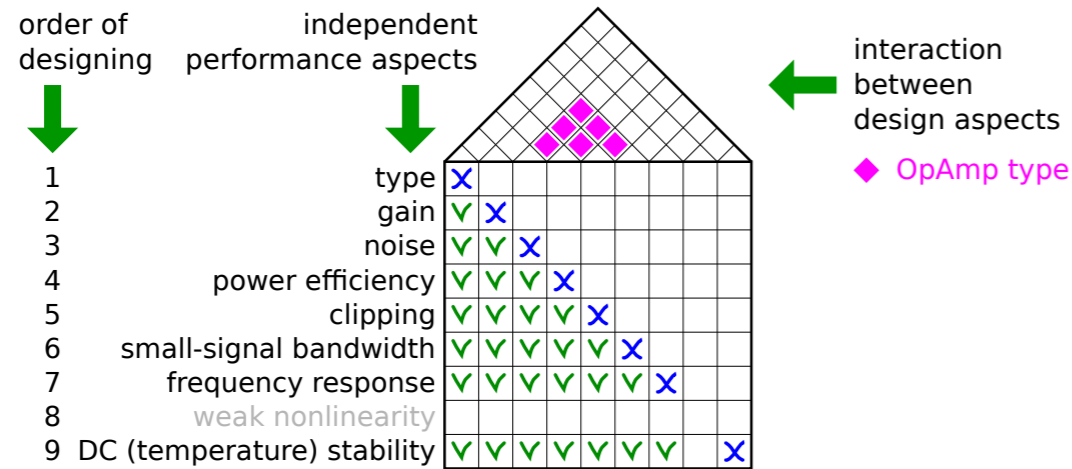

The House Of Quality

an application of:

Quality
Function
Deployment

feedback configuration

feedback network

equivalent input noise sources

quiescent current / headroom

V/I drive capability

gain-bandwidth product

frequency compensation

over-all biasing

Orthogonal design of negative feedback amplifiers with OpAmps

The Design Procedure

1. Measure the load signal (V or I)

- a. Voltage should be measured across (in parallel with) the load
- b. Current should be measured through (in series with) the load

2. Design a network that generates of copy of the source signal (V or I) from the measured load signal

- a. The transfer of this network is the reciprocal of the desired source-to-load transfer

3. Subtract the copy from the source signal

- a. In case of a voltage source signal, the signal source and the output of the feedback network should be connected anti-series
- b. In case of a current source signal, the signal source and the output of the feedback network should be connected anti-parallel

4. Nullify the difference

- a. In case of a voltage source signal, a nullator closes the loop of the above anti-series connection
- b. In case of a current source signal, a nullator is placed in parallel with the above anti-parallel connection
- c. In case of a voltage load signal, a norator is placed in parallel with the load
- d. In case of a current load signal, a norator closes the loop of the series connection of the load and the input of the feedback network

Single-loop negative Feedback Amplifiers

Source	Load	Amplifier	A, B, C, D	Feedback method
V	V	Voltage amplifier	A, 0, 0, 0	Output voltage sensing / parallel feedback Input voltage comparison / series feedback
V	I	Transadmittance	0, B, 0, 0	Output current sensing / series feedback Input voltage comparison / series feedback
I	V	Transimpedance	0, 0, C, 0	Output voltage sensing / parallel feedback Input current comparison / parallel feedback
I	I	Current amplifier	0, 0, 0, D	Output current sensing / series feedback Input current comparison / parallel feedback



Conclusions feedback configurations

1. All port (isolation) configurations can be realized using nonenergetic feedback with natural two-ports (gyrator, transformer)
2. If the feedback network is not a natural two-port:
 - a. Source and load are electrically connected
 - b. Sign of transfer depends on amplifier type
 - c. Port isolation and/or sign inversion requires:
 - Active feedback
 - Balanced feedback
 - Indirect feedback
 - Transformers

Error reduction capabilities of negative feedback

- With a high-gain controller the static and dynamic transfer are predominantly determined by the feedback network
- This is not the case for the noise behavior
 - a. The equivalent input noise sources of the controller should be kept small
 - b. Deterioration of the signal to noise ratio by the feedback network should be kept small

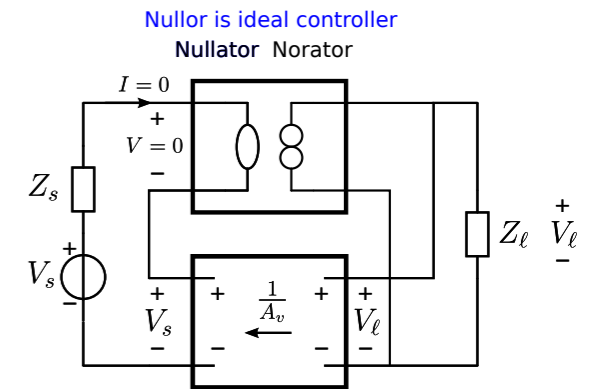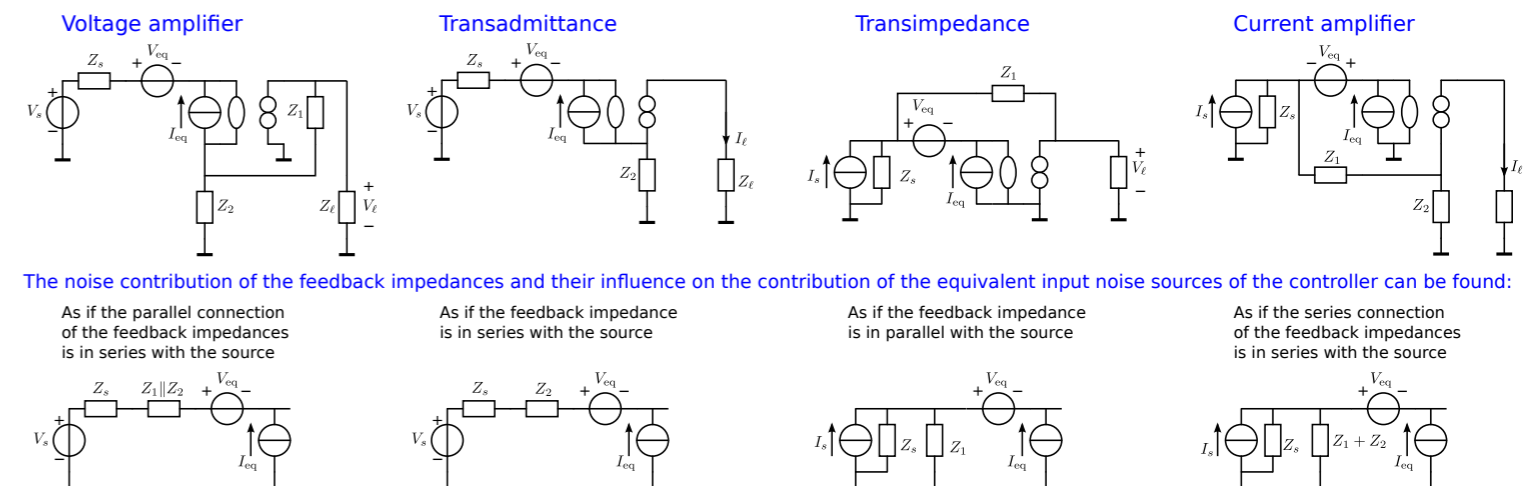Single-loop passive feedback configurations and their equivalent input noise models




Types of feedback

Implementation of the feedback network

1. Nonenergetic feedback
 - a. Transformers, gyrators
 - b. Short and open circuit
2. Passive feedback
 - a. Non-dissipative: inductors and/or capacitors
 - b. Dissipative: includes resistors
3. Active feedback
 - a. Feedback network comprises an amplifier

Negative feedback and ideal gain

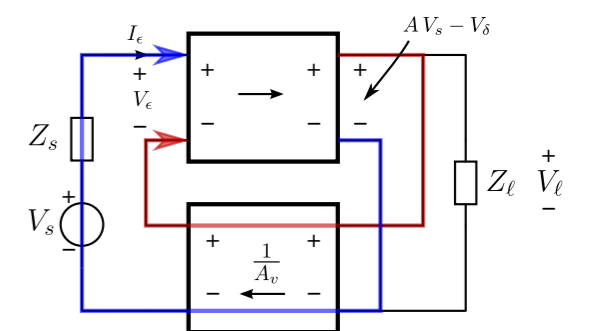

1. The ideal gain is the source-to-load transfer in the case of a nullor as controller
2. Practical controllers have a finite gain and bandwidth
 - a. Negative (corrective) feedback if transfer from the positive output of the controller to its positive input is inverting:

Noise performance nonenergetic feedback amplifiers

The equivalent input noise sources of the amplifier are equal to those of the controller

