


Structured Electronic Design

Capacitively Loaded CC-stage


Anton J.M. Montagne

Capacitively loaded CC stage

 
Concept:
capacitively loaded voltage follower



 
Implementation with BJT
Biased CE-stage is used as controller:



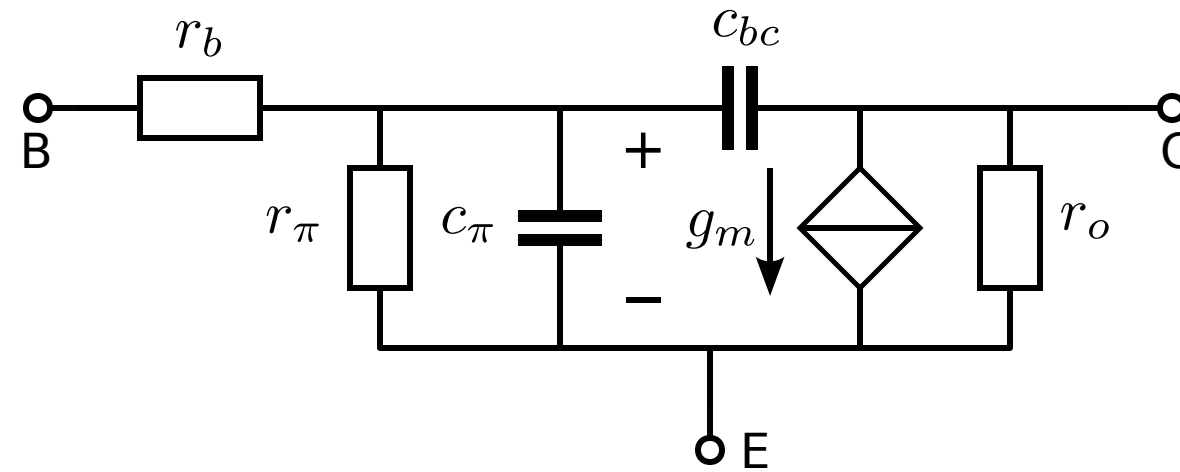small-signal hybrid-pi equivalent circuit
of a biased transistor



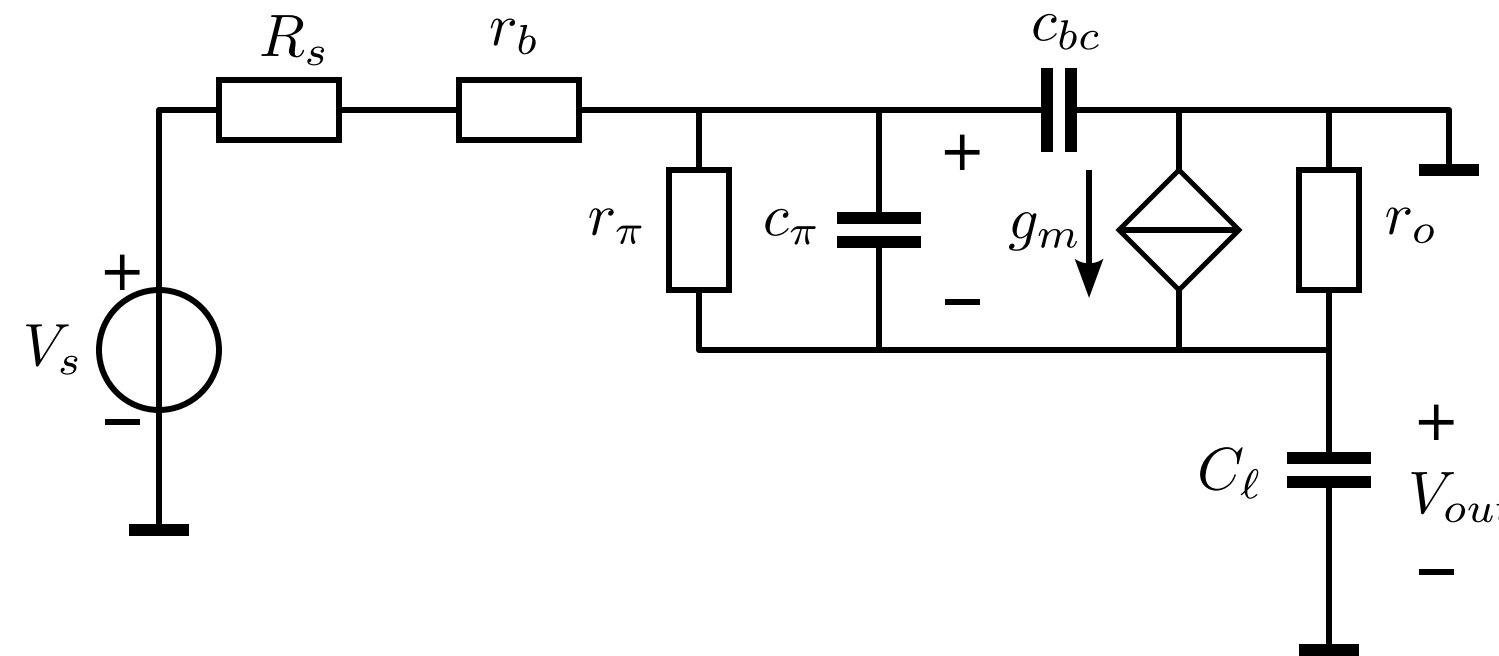
small-signal equivalent circuit of the
capacitively loaded CC-stage




LTspice .op

Name:	q1
Model:	2n3904
Ib:	3.09e-05
Ic:	9.97e-03
Vbe:	7.14e-01
Vbc:	-1.00e+01
Vce:	1.07e+01
BetaDC:	3.23e+02
Gm:	3.77e-01
Rpi:	8.37e+02
Rx:	2.00e+01
Ro:	1.10e+04
Cbe:	1.45e-10
Cbc:	1.66e-12
Cjs:	0.00e+00
BetaAC:	3.16e+02
Cbx:	0.00e+00
Ft:	4.09e+08

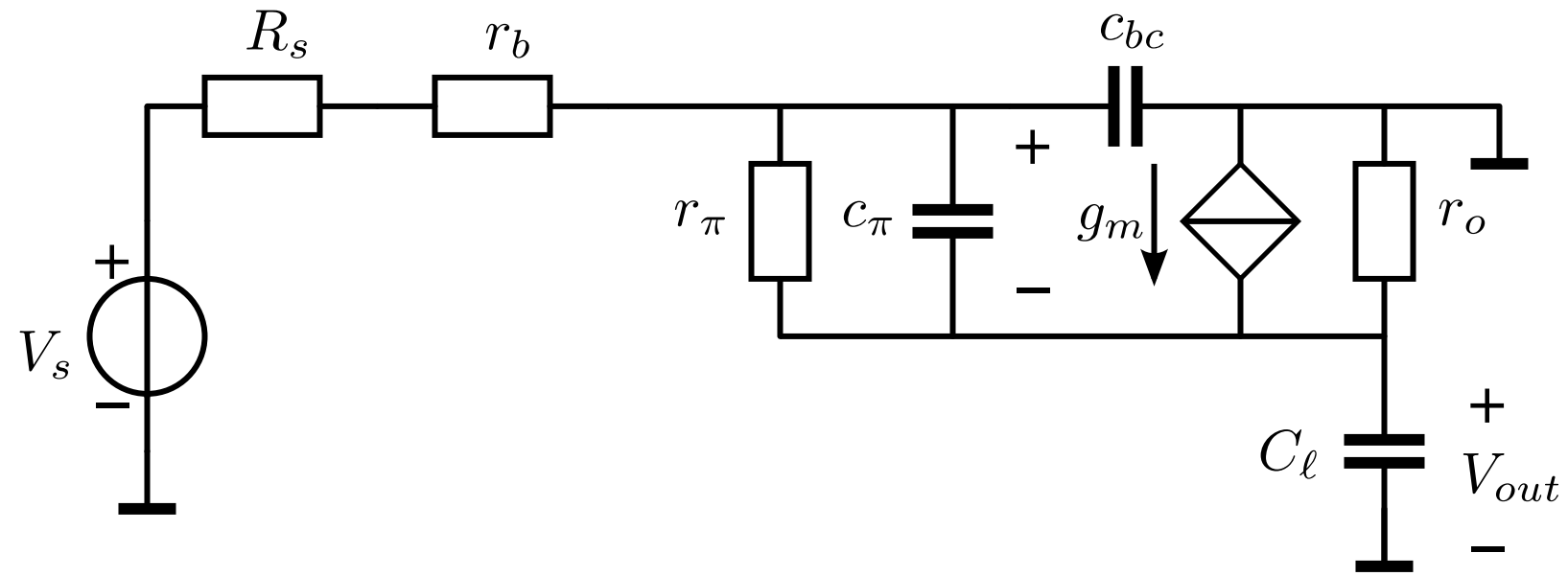
Asymptotic-gain model selection loop gain reference



Complete small-signal equivalent circuit

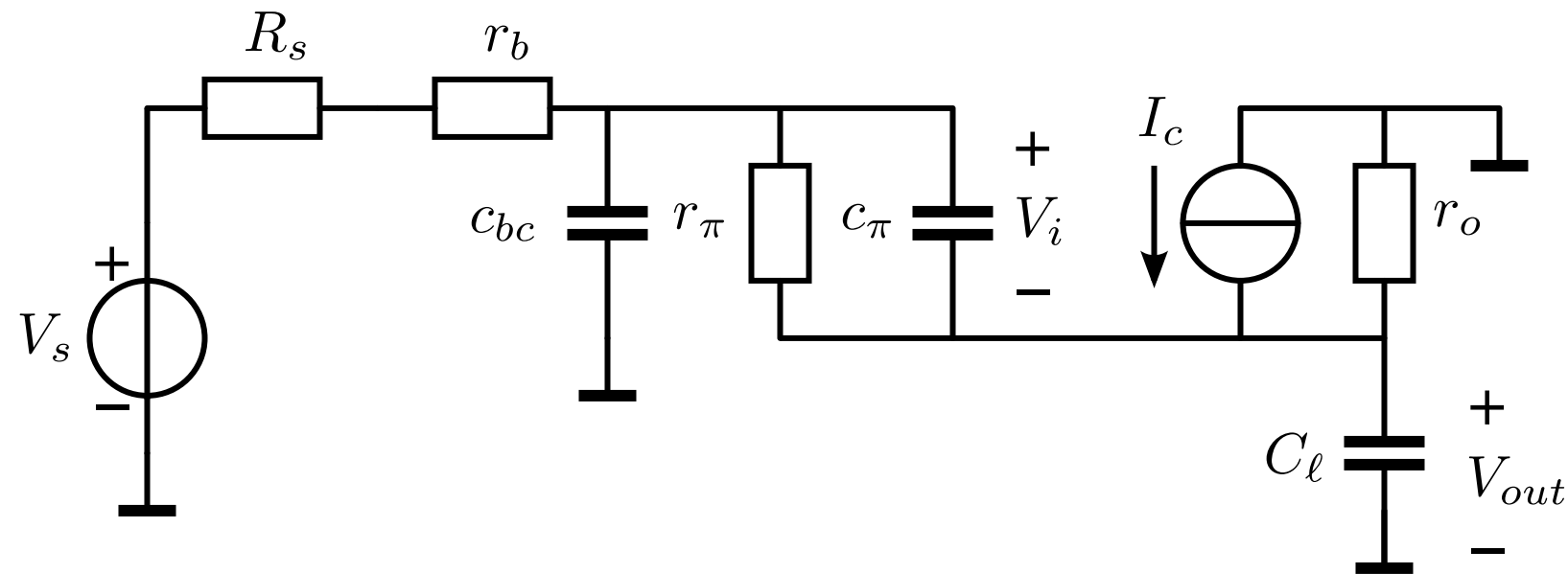

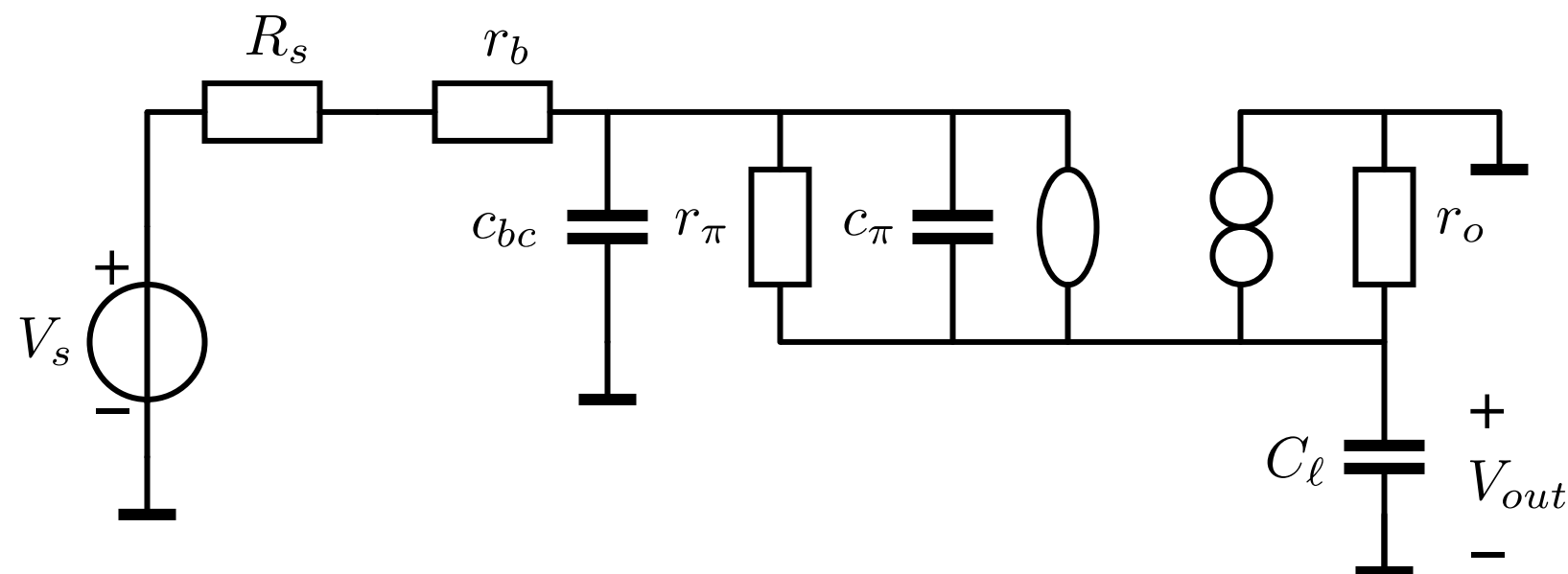
Controlled source selected as loopgain reference
 c_{bc} causes internal feedback loop
 can be placed outside the controller
 changes the ideal gain





asymptotic-gain equals the ideal gain

$$\frac{V_{out}}{V_s} = \frac{1}{1 + s(R_s + r_b)c_{bc}}$$


Evaluation DC loop gain

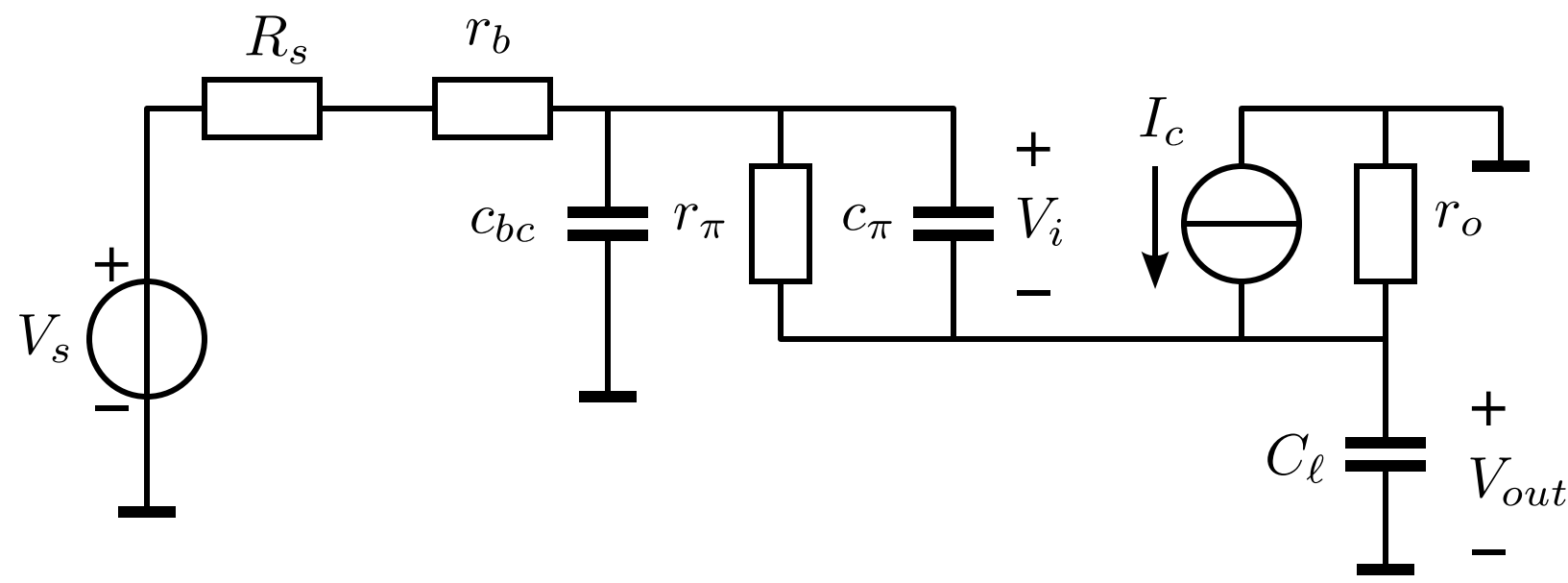

redraw
the circuit

  

DC equivalent circuit

 


$$L_{DC} = -g_m \frac{r_o}{r_o + r_b + R_s + r_\pi} r_\pi = -\beta_{AC} \frac{r_o}{r_o + r_b + R_s + r_\pi}$$

$$L_{DC} = -288$$

↑
current
gain

↑
current
division


Evaluation poles loop gain

 

How many poles?

number of capacitors - number of independent loops of capacitors (and voltage sources)

two

 


Method


Leave c_{bc} out (much smaller than the equivalent series capacitance of the other two)

Use time-constant method for estimation of poles


Evaluation poles loop gain

 


Leave c_{bc} out

 

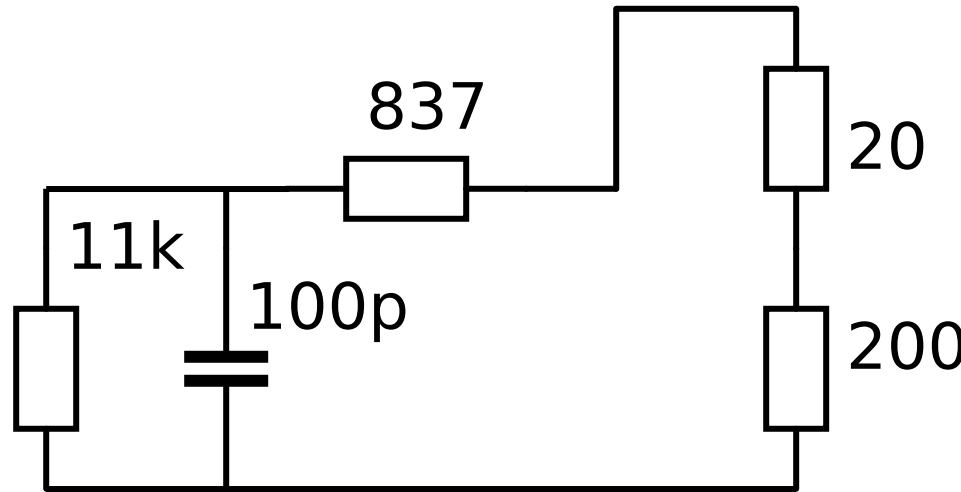Determine TC1:
 $145p // 837 // 11220 = 113ns$



 Determine TC2:
 $100p // 11000 // 1057 = 96ns$




Short port with dominant time-constant and update TC2:
 $100p // 11000 // 220 = 21.6ns$

$$\begin{aligned}
 p_1 &= -\frac{10^9}{2\pi 113} = -1.41 \text{ MHz} \\
 p_2 &= -\frac{10^9}{2\pi 21.6} = -7.37 \text{ MHz} \\
 L_{DC} &= -288 \\
 p_1 + p_2 &= -8.78 \text{ MHz}
 \end{aligned}
 \left. \vphantom{\begin{aligned} p_1 \\ p_2 \\ L_{DC} \\ p_1 + p_2 \end{aligned}} \right\} B_f = 54.8 \text{ MHz}$$

Sum of the poles much smaller than $\sqrt{2}$ times the bandwidth.
 MFM response requires frequency compensation!

Evaluation zeros of loop gain

 

Zero at frequency where:

$$\frac{V_i}{I_c} = 0$$

$$\text{if: } \frac{1}{r_b + R_s} = -s C_{bc}$$

$$z = -\frac{1}{C_{bc}(R_s + r_b)}$$

Frequency of the zero: -436 MHz

Poles and zeros of loop gain, conclusions

Zero matches SLiCAP simulation

Product of the poles (bandwidth) matches SLiCAP simulation

Sum of the poles wrong (higher order approximation required)

Sum of the (dominant) poles not much of interest for design of bandwidth

Accurate analysis and phantom-zero compensation: see SLiCAP example