
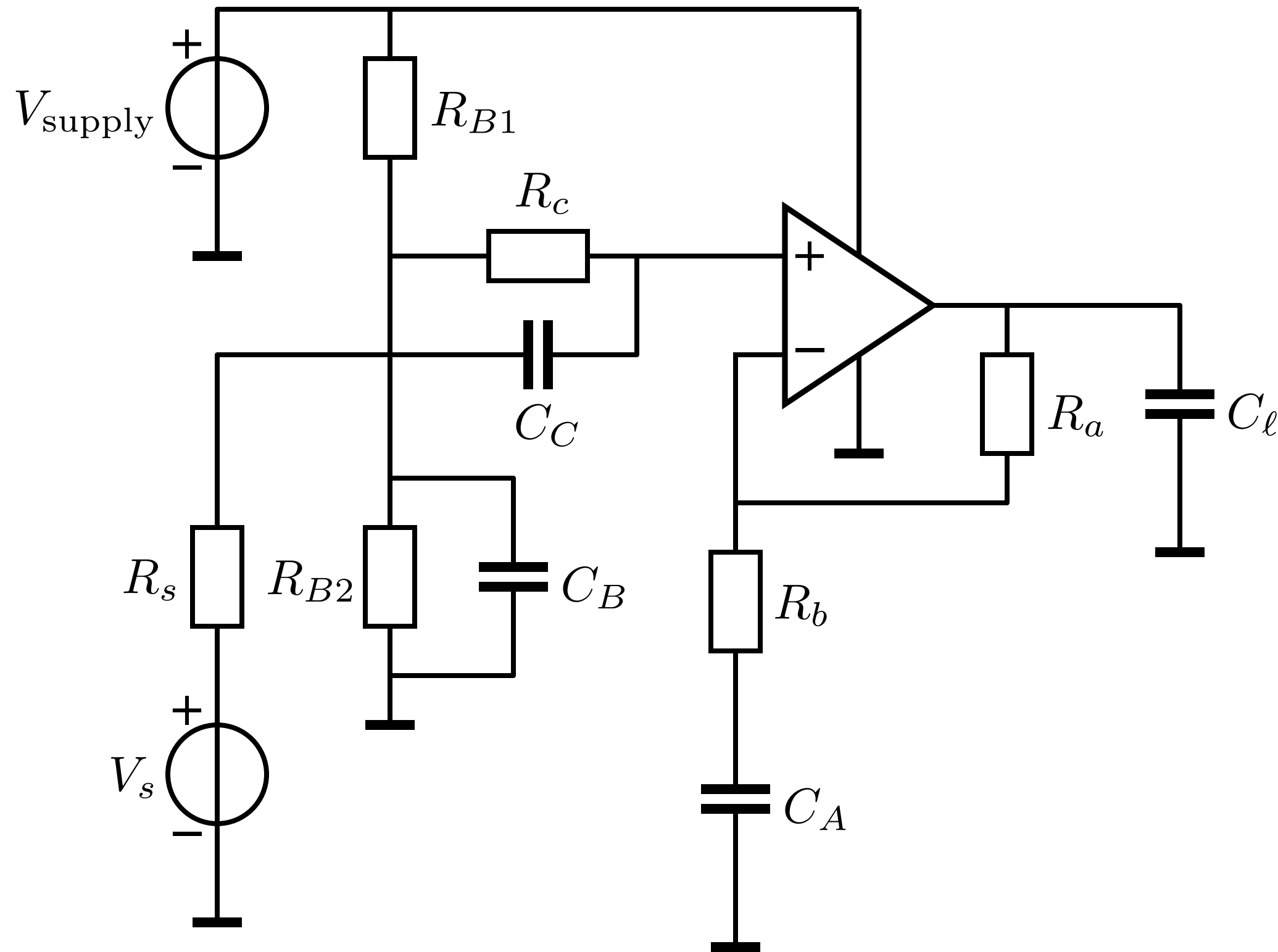


Component selection

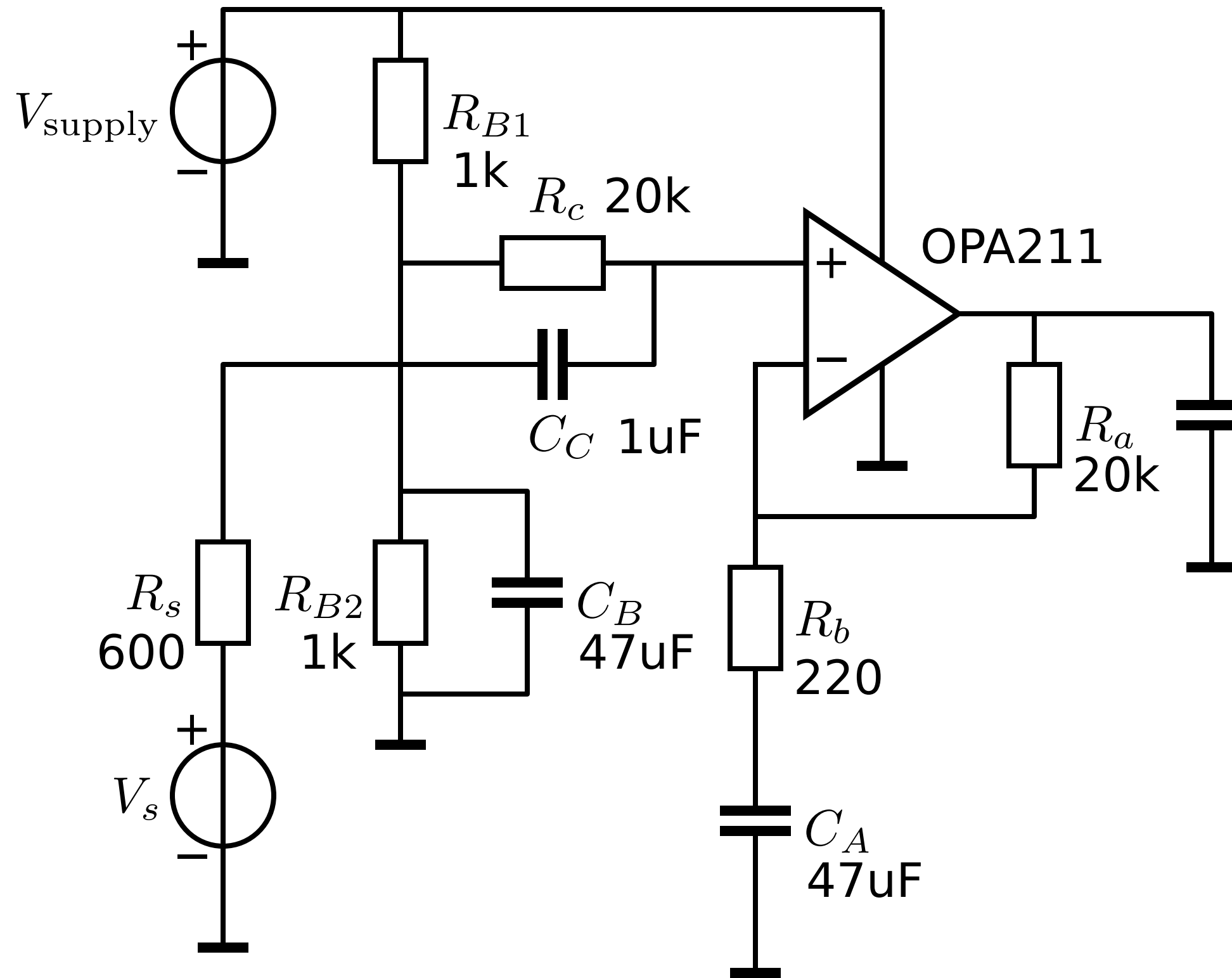

- Noise:
 - $R_b < 600\Omega$,
 - $R_c \gg 600\Omega$,
 - $\frac{1}{2\pi f C_C} \ll R_s$,
 - $S_{V_n} < 3.15 \frac{\text{nV}}{\sqrt{\text{Hz}}}$
 - $S_{I_n} < 5.25 \frac{\text{pA}}{\sqrt{\text{Hz}}}$
- Bandwidth:
 - $\frac{1}{2\pi f_{\text{low}} C_A} \leq R_b$
 - $\text{GB} > 45 \text{ MHz}$
 - $\frac{1}{2\pi f_{\text{low}} C_A} \leq R_b$
- Accuracy:
 - $R_c \gg R_s$
 - $A_0 \gg 33 \times 90 \approx 3000$
- Drive capability:
 - $I_{\text{source,sink}} > 5 \text{ mA}$
 - $\text{SR} > 1.5 \text{ V}/\mu\text{s}$
 - $V_{\text{sat}} < 0.25 \text{ V}$

Component selection



- Noise:

$$R_b < 600\Omega,$$

$$R_c \gg 600\Omega,$$

$$\frac{1}{2\pi f C_C} \ll R_s,$$

$$S_{V_n} < 3.15 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

$$S_{I_n} < 5.25 \frac{\text{pA}}{\sqrt{\text{Hz}}}$$

- Bandwidth:

$$\frac{1}{2\pi f_{\text{low}} C_A} \leq R_b$$

$$\text{GB} > 45 \text{ MHz}$$

$$\frac{1}{2\pi f_{\text{low}} C_A} \leq R_b$$

- Accuracy:

$$R_c \gg R_s$$

$$A_0 \gg 33 \times 90 \approx 3000$$

- Drive capability:


$$I_{\text{source,sink}} > 5 \text{ mA}$$

$$\text{SR} > 1.5 \text{ V}/\mu\text{s}$$

$$V_{\text{sat}} < 0.25 \text{ V}$$

Modeling OpAmp

Small-signal dynamic behavior OPA211

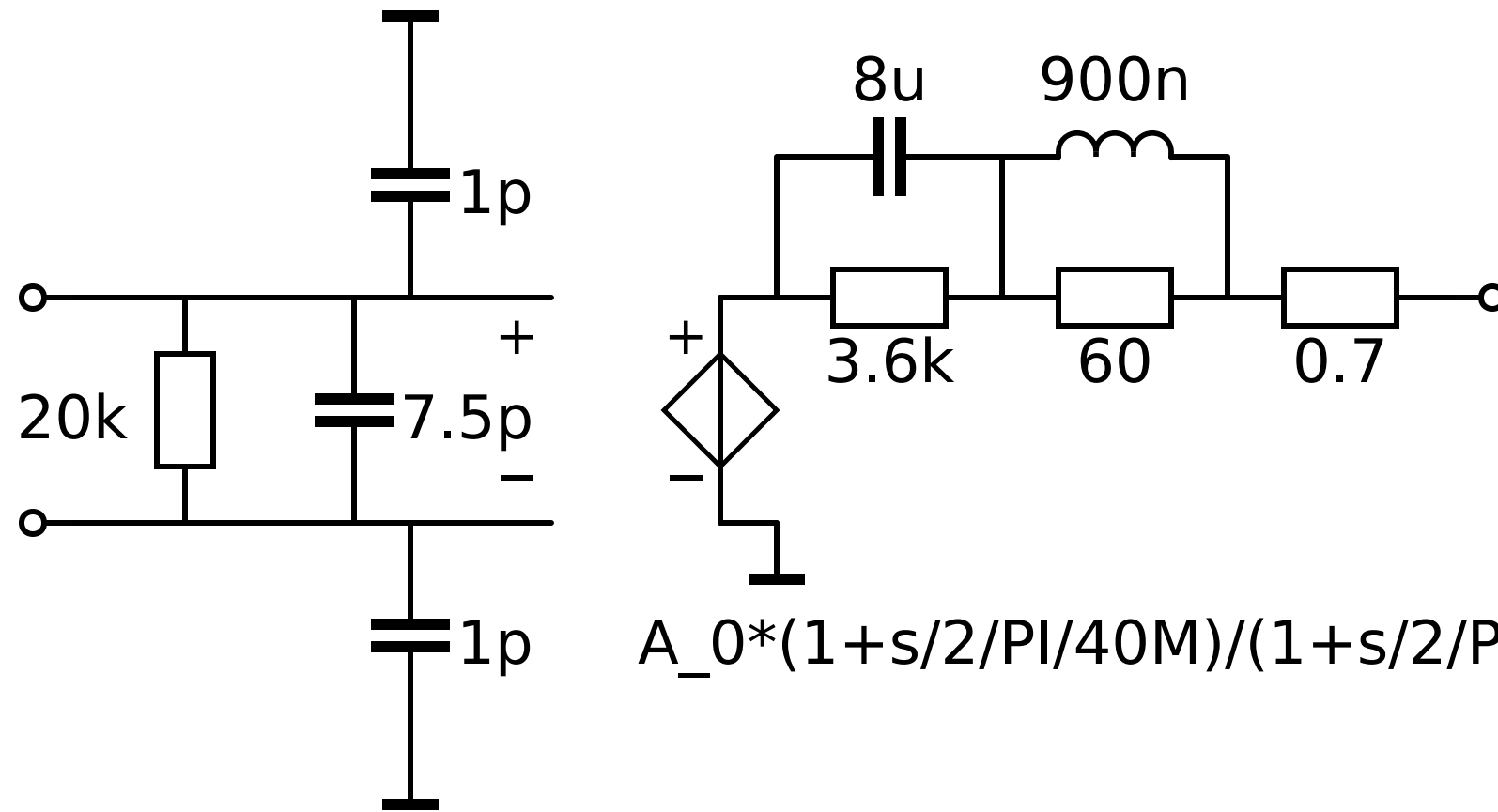

$$A_0 * (1 + s/2/\pi/40M) / (1 + s/2/\pi/120) / (1 + 2/2/\pi/20M)$$

```
.model OPA211_A0 OV
+ cd = 8p ; differential-mode input capacitance
+ gd = 50u ; differential-mode input conductance
+ cc = 2p ; common-mode input capacitance
+ av = {A_0*(1+s/2/PI/40M)/(1+s/2/PI/120)/(1+s/2/PI/20M)} ; voltage gain
+ zo = {3.6k/(1+s*3.6k*8u) + 0.7 + s*900n*60/(60+s*900n)} ; output impedance
```



OPA211, OPA2211

www.ti.com

SBOS377K – OCTOBER 2006 – REVISED SEPTEMBER 2018

Typical Characteristics (continued)

at $T_A = 25^\circ\text{C}$, $V_S = \pm 18\text{ V}$, and $R_L = 10\text{ k}\Omega$, unless otherwise noted.

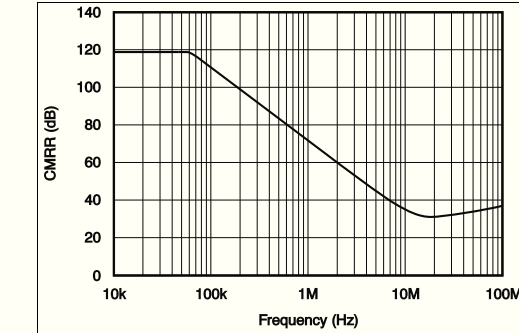


Figure 7. Common-Mode Rejection Ratio vs Frequency

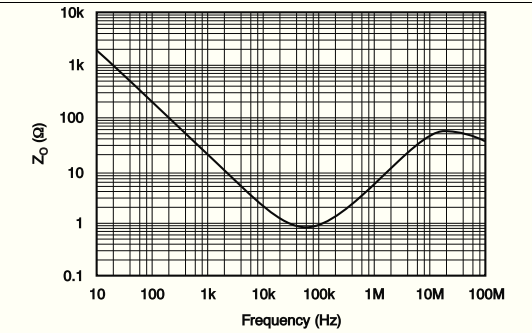


Figure 8. Open-Loop Output Impedance vs Frequency

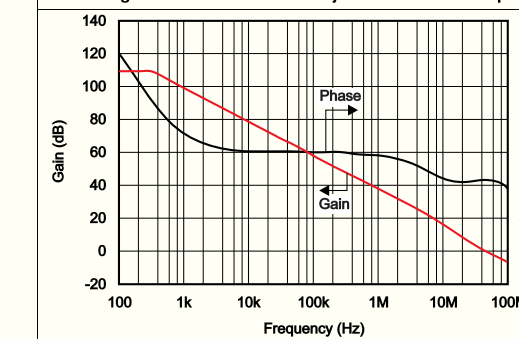


Figure 9. Gain and Phase vs Frequency

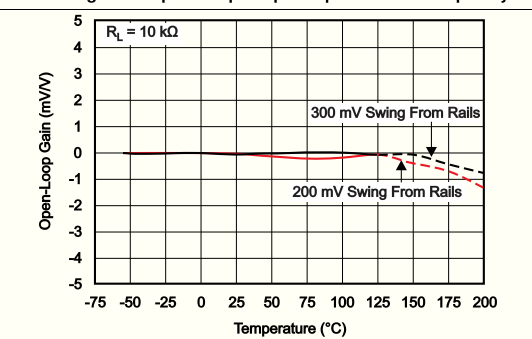


Figure 10. Open-Loop Gain vs Temperature

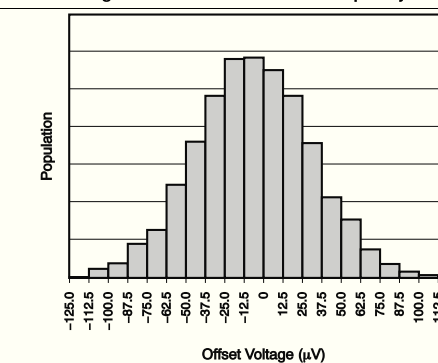


Figure 11. Offset Voltage Production Distribution

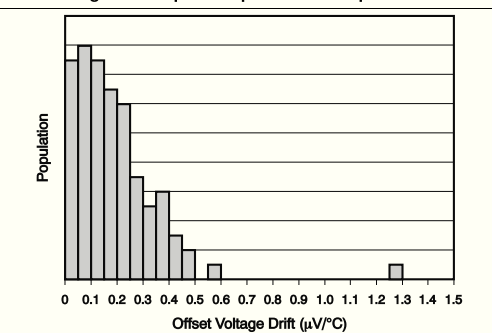


Figure 12. Offset Voltage Drift Production Distribution

Copyright © 2006–2018, Texas Instruments Incorporated

[Submit Documentation Feedback](#)

15

Product Folder Links: [OPA211](#) [OPA2211](#)

Modeling OpAmp



OPA211, OPA2211

SBOS377K – OCTOBER 2006 – REVISED SEPTEMBER 2018

www.ti.com

6.6 Electrical Characteristics: $V_S = \pm 2.25$ to ± 18 V (OPAx211)

at $T_A = 25^\circ\text{C}$, $R_L = 10\text{ k}\Omega$ connected to midsupply, $V_{CM} = V_{OUT} = \text{midsupply}$, (unless otherwise noted)

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT	
OFFSET VOLTAGE						
V_{OS}	Input offset voltage	OPA211: $V_S = \pm 15\text{ V}$		± 30	± 125	μV
		OPA2211: $V_S = \pm 15\text{ V}$		± 50	± 150	μV
dV_{OS}/dT	Input offset drift	$V_S = \pm 15\text{ V}$ $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		± 0.35	± 1.5	$\mu\text{V}/^\circ\text{C}$
PSRR	Input offset voltage vs power supply	$T_A = 25^\circ\text{C}$		0.1	1	$\mu\text{V}/\text{V}$
		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$			3	$\mu\text{V}/\text{V}$
INPUT BIAS CURRENT						
I_B	Input bias current	$V_{CM} = 0\text{ V}$		± 60	± 175	nA
		OPA211: $V_{CM} = 0\text{ V}$ $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$			± 200	nA
		OPA2211: $V_{CM} = 0\text{ V}$ $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$			± 250	nA
I_{OS}	Input offset current	$V_{CM} = 0\text{ V}$		± 25	± 100	nA
		$V_{CM} = 0\text{ V}$ $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$			± 150	nA
NOISE						
e_n	Input voltage noise	$f = 0.1$ to 10 Hz		80		nV_{PP}
	Input voltage noise density	$f = 10\text{ Hz}$		2		$\text{nV}/\sqrt{\text{Hz}}$
		$f = 100\text{ Hz}$		1.4		$\text{nV}/\sqrt{\text{Hz}}$
		$f = 1\text{ kHz}$		1.1		$\text{nV}/\sqrt{\text{Hz}}$
I_n	Input current noise density	$f = 10\text{ Hz}$		3.2		$\text{pA}/\sqrt{\text{Hz}}$
		$f = 1\text{ kHz}$		1.7		$\text{pA}/\sqrt{\text{Hz}}$
INPUT VOLTAGE RANGE						
V_{CM}	Common-mode voltage range	$V_S \geq \pm 5\text{ V}$		$(V-) + 1.8$	$(V+) - 1.4$	V
		$V_S < \pm 5\text{ V}$		$(V-) + 2$	$(V+) - 1.4$	V
CMRR	Common-mode rejection ratio	$V_S \geq \pm 5\text{ V}$ $(V-) + 2\text{ V} \leq V_{CM} \leq (V+) - 2\text{ V}$ $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		114	120	dB
		$V_S < \pm 5\text{ V}$ $(V-) + 2\text{ V} \leq V_{CM} \leq (V+) - 2\text{ V}$ $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		110	120	dB
INPUT IMPEDANCE						
	Differential		$20 \parallel 8$			$\text{k}\Omega \parallel \text{pF}$
	Common-mode		$10 \parallel 2$			$\text{G}\Omega \parallel \text{pF}$
OPEN-LOOP GAIN						

SLiCAP noise and bias models


SLiCAP O_{dcvar}
nullor with offset and bias

Standard deviation offset voltage $svo = 40 \times 10^{-6}$
 Standard deviation offset current $sio = 30 \times 10^{-9}$
 Mean value bias current $iib = 0$
 Standard deviation bias current $sib = 60 \times 10^{-9}$

SLiCAP O_{noise}
nullor with equivalent input noise sources


Spectral density noise voltage $sv = 1.2 \times 10^{-18}$
 Spectral density noise current $si = 2.9 \times 10^{-24}$

SLiCAP noise verification

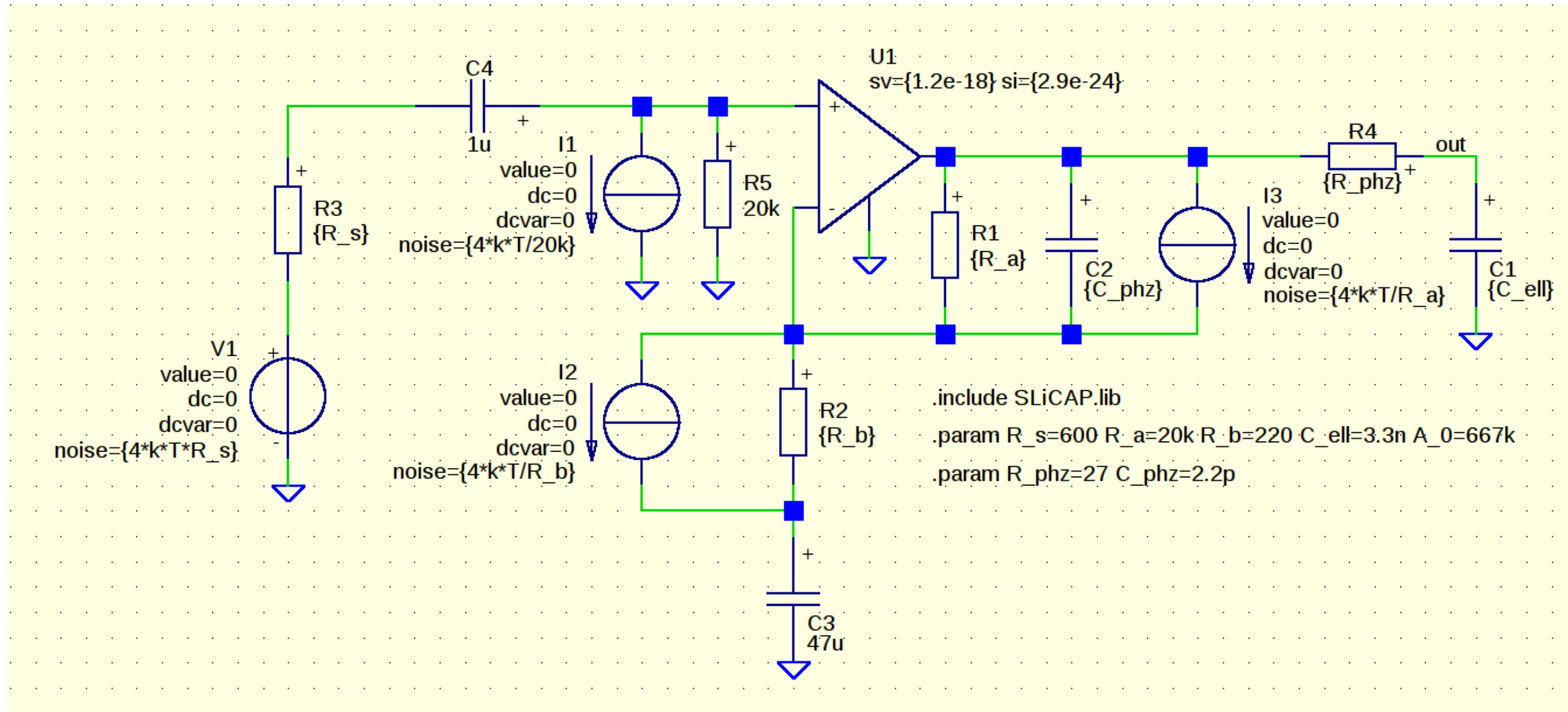

Noise figure 2.4dB over 1.57x500kHz bandwidth.




SLiCAP biasing verification

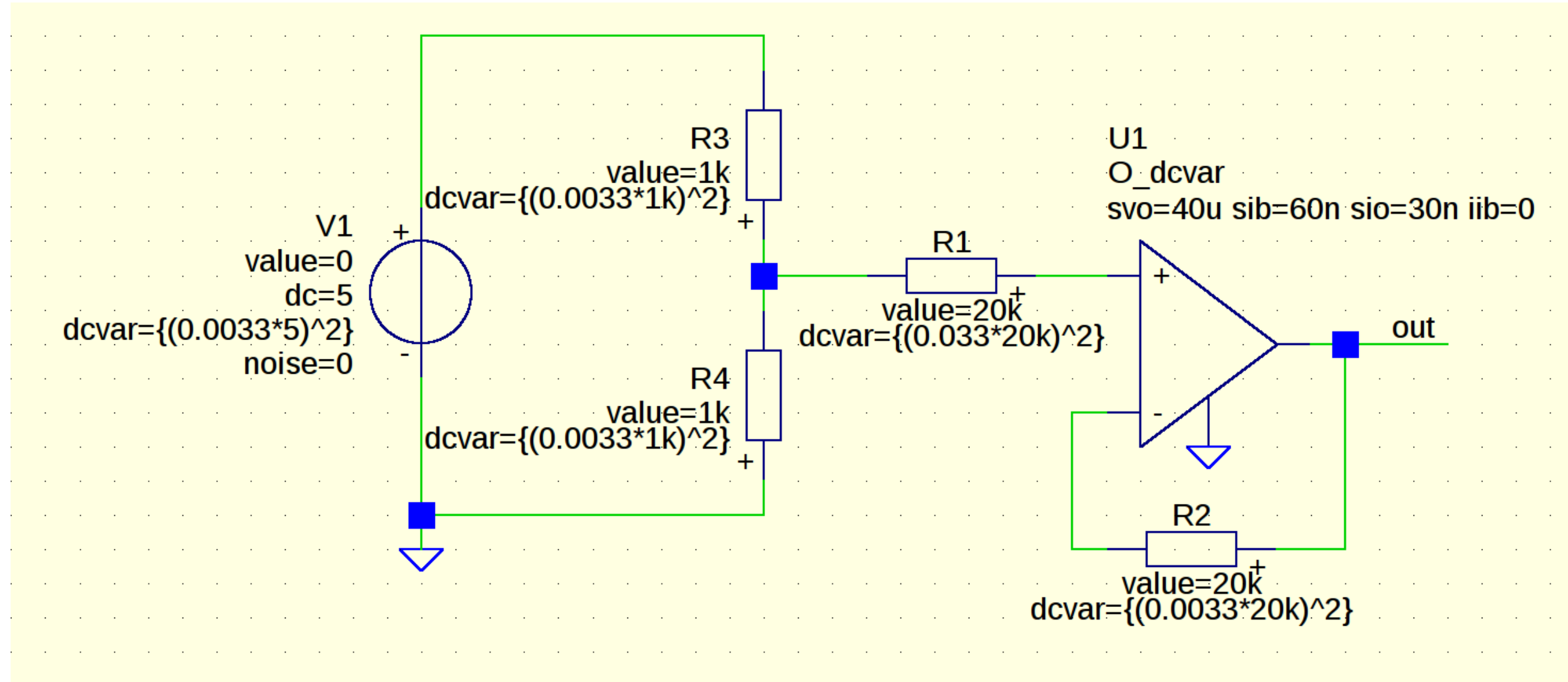

All component tolerances 1% (3-sigma)

Standard deviation of the output voltage: 10mV


Frequency response

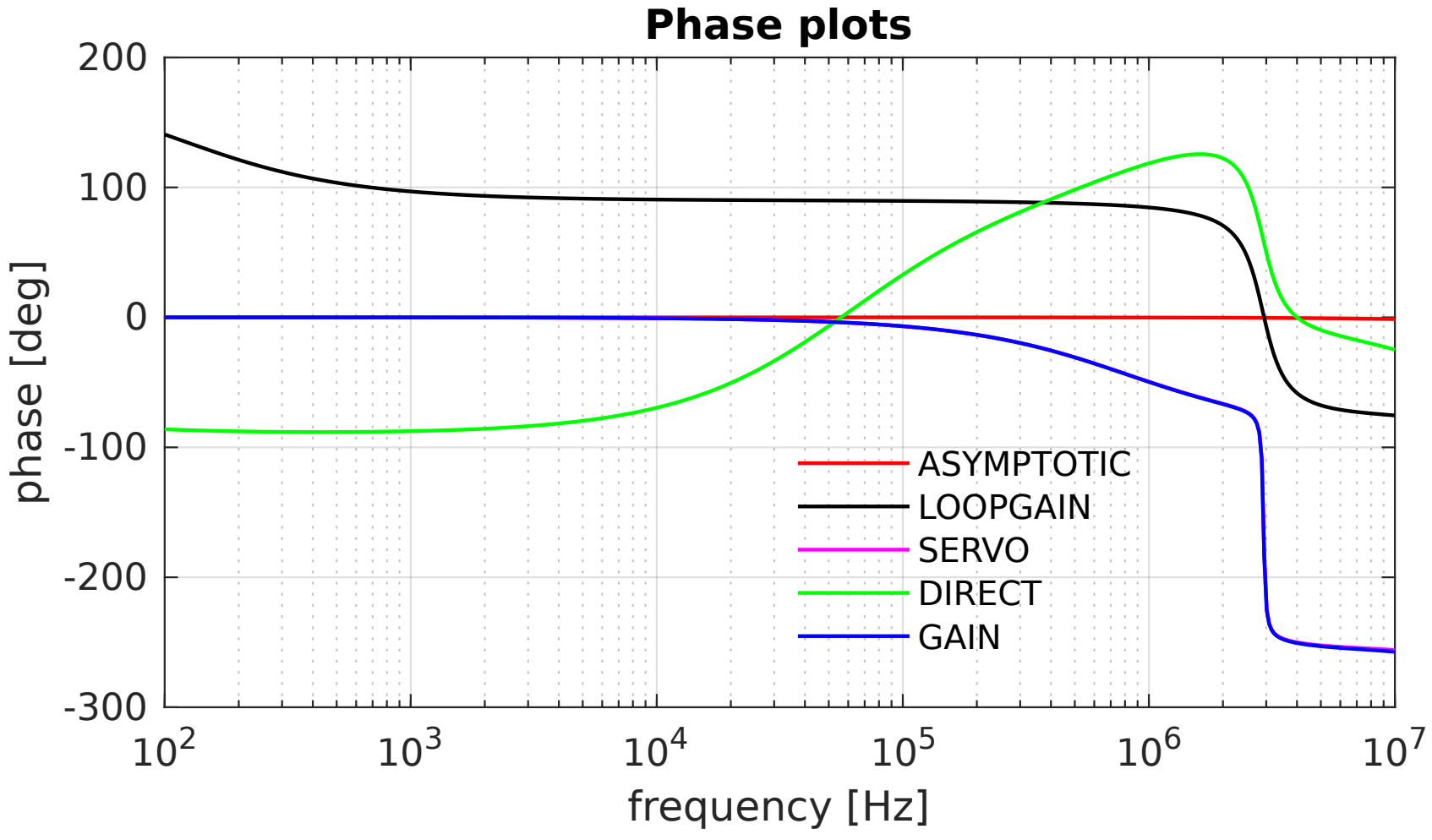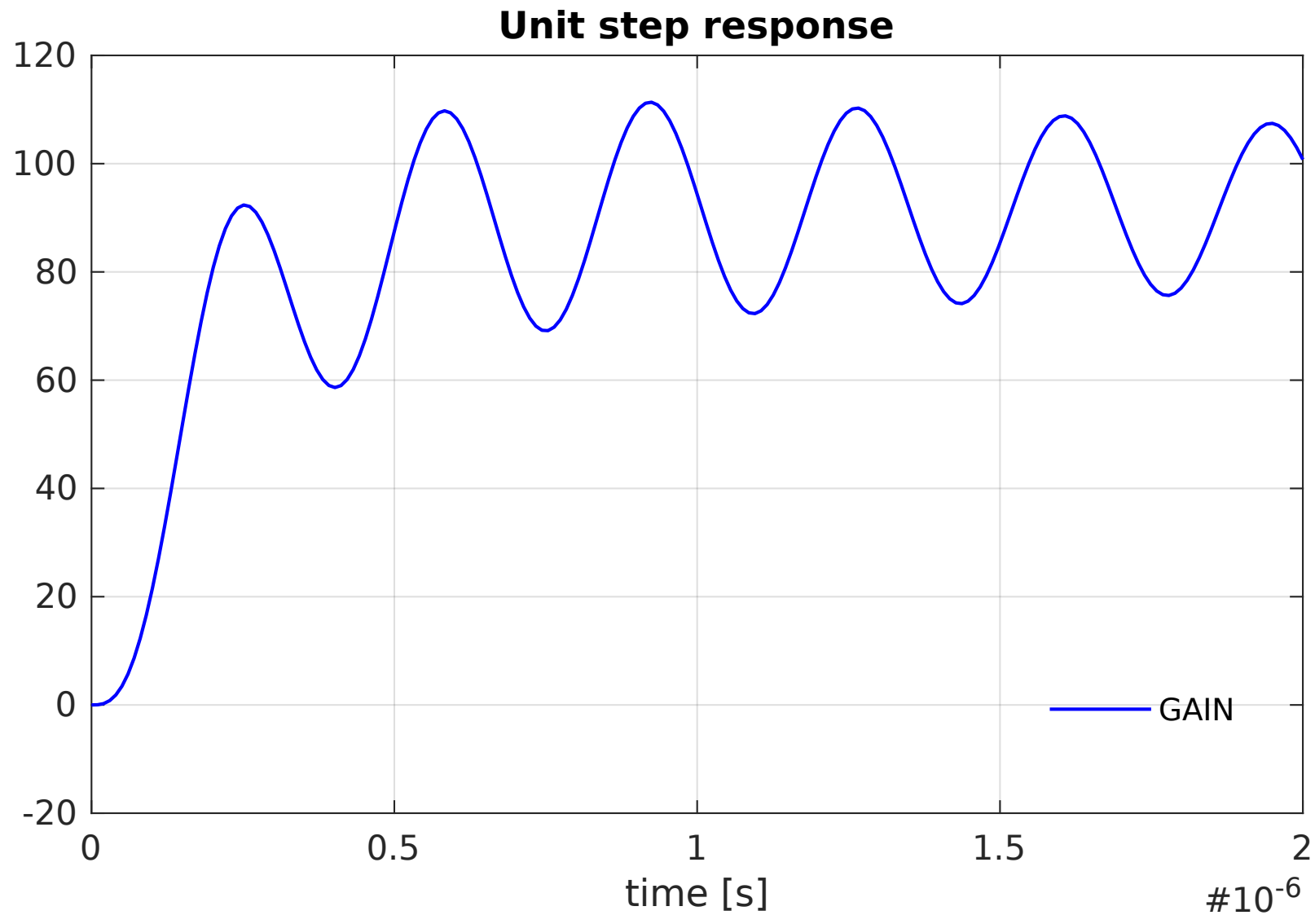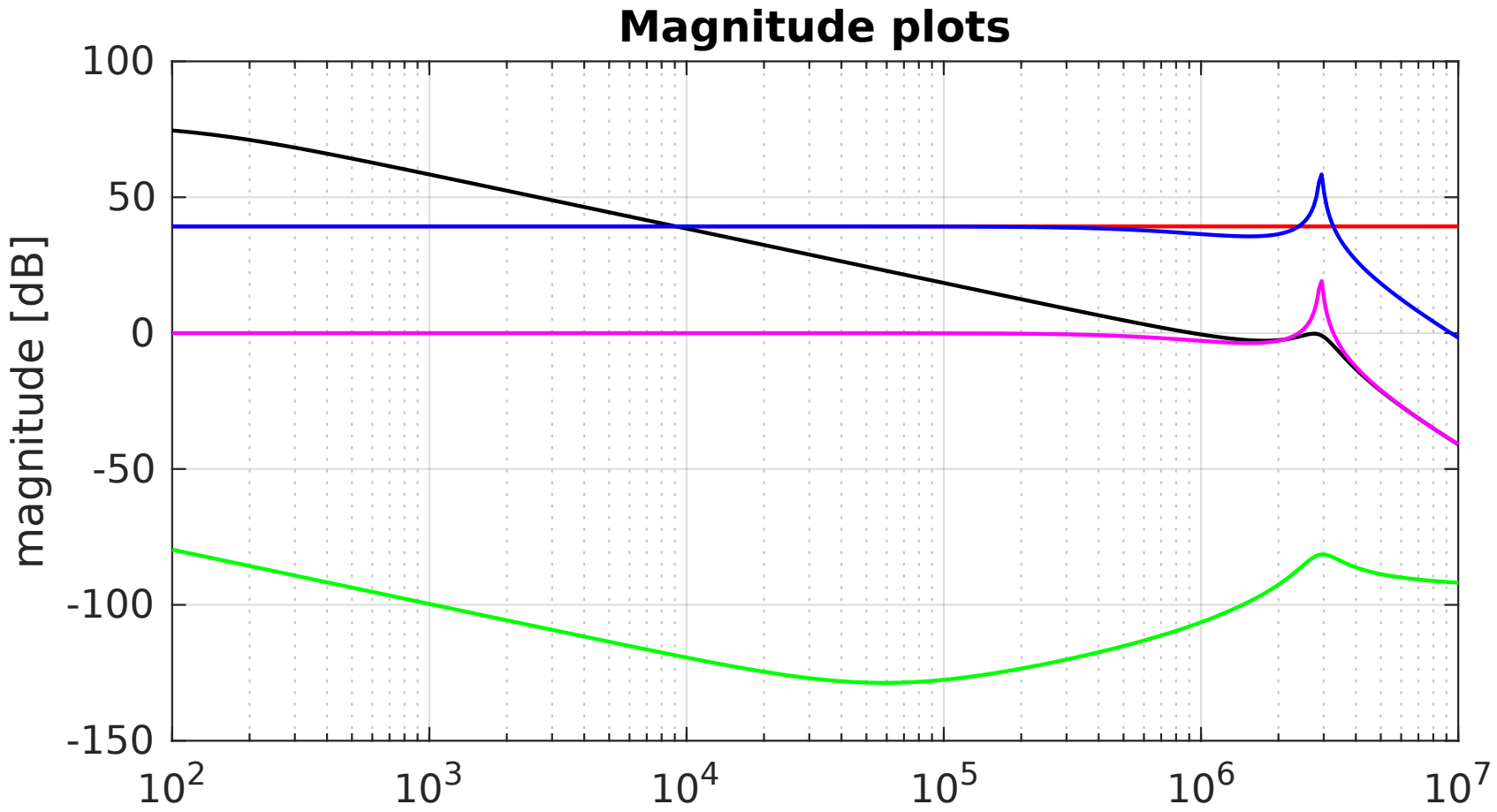


Uncompensated amplifier

Frequency compensation


Magnitude plots

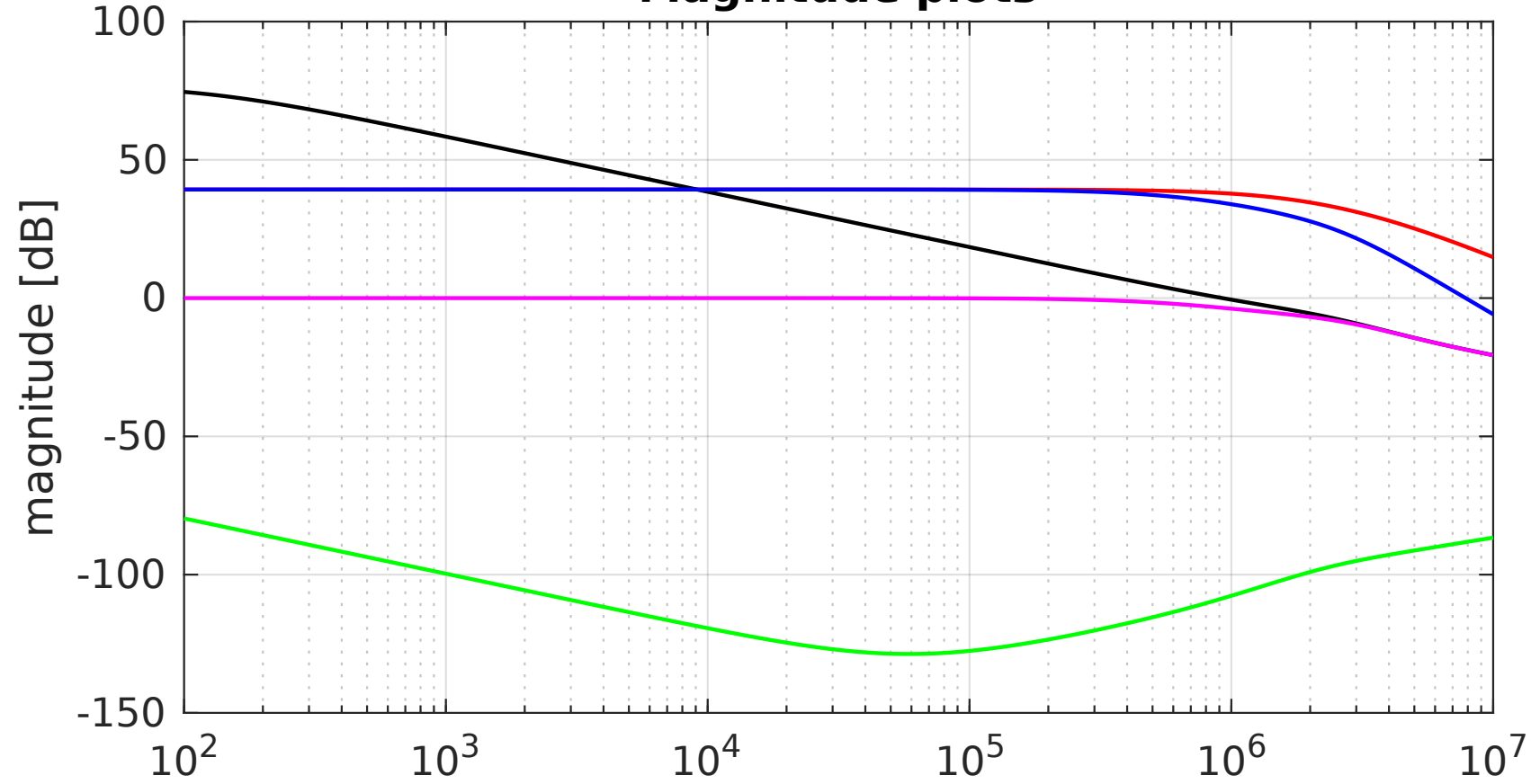

Phase plots


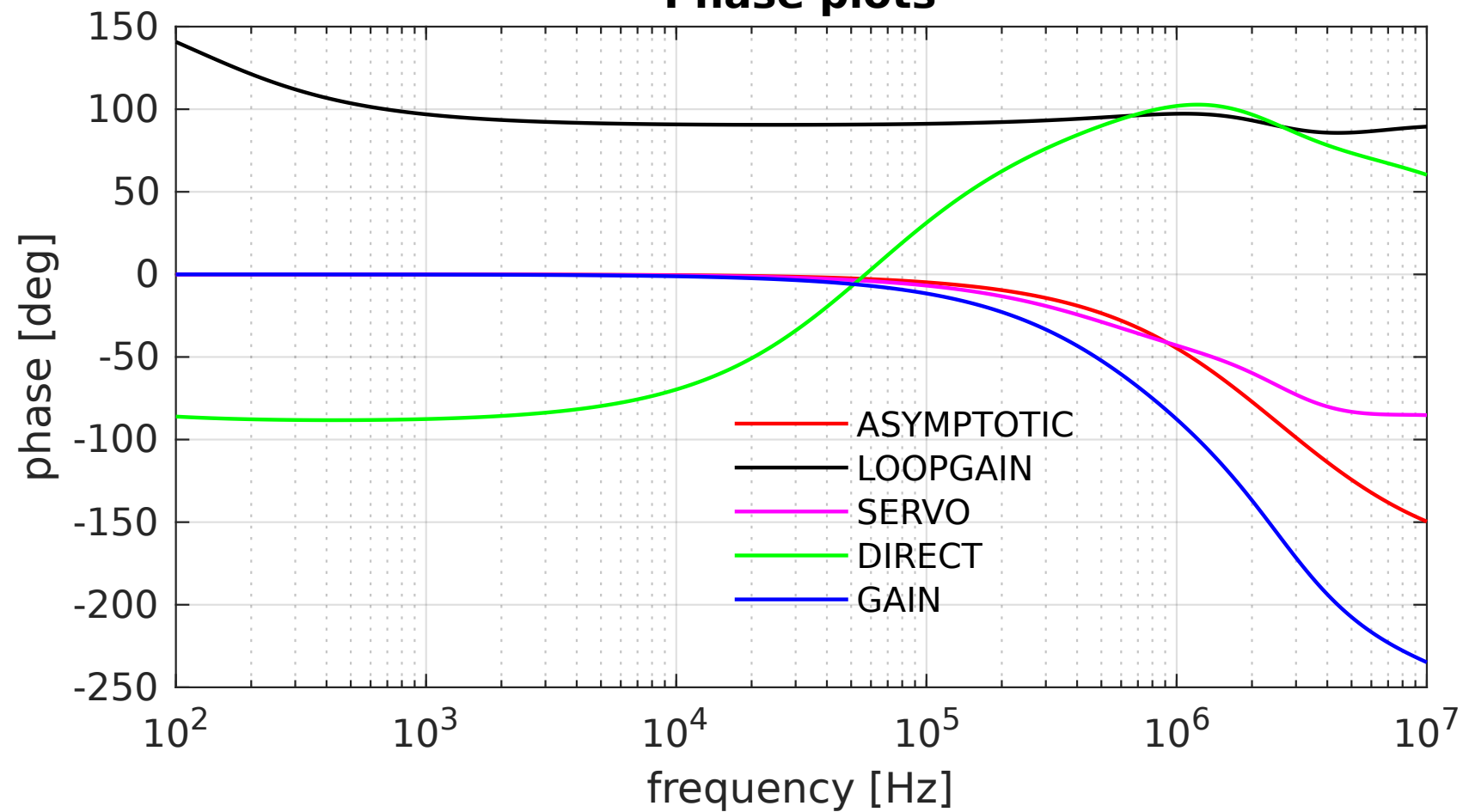


Unit step response

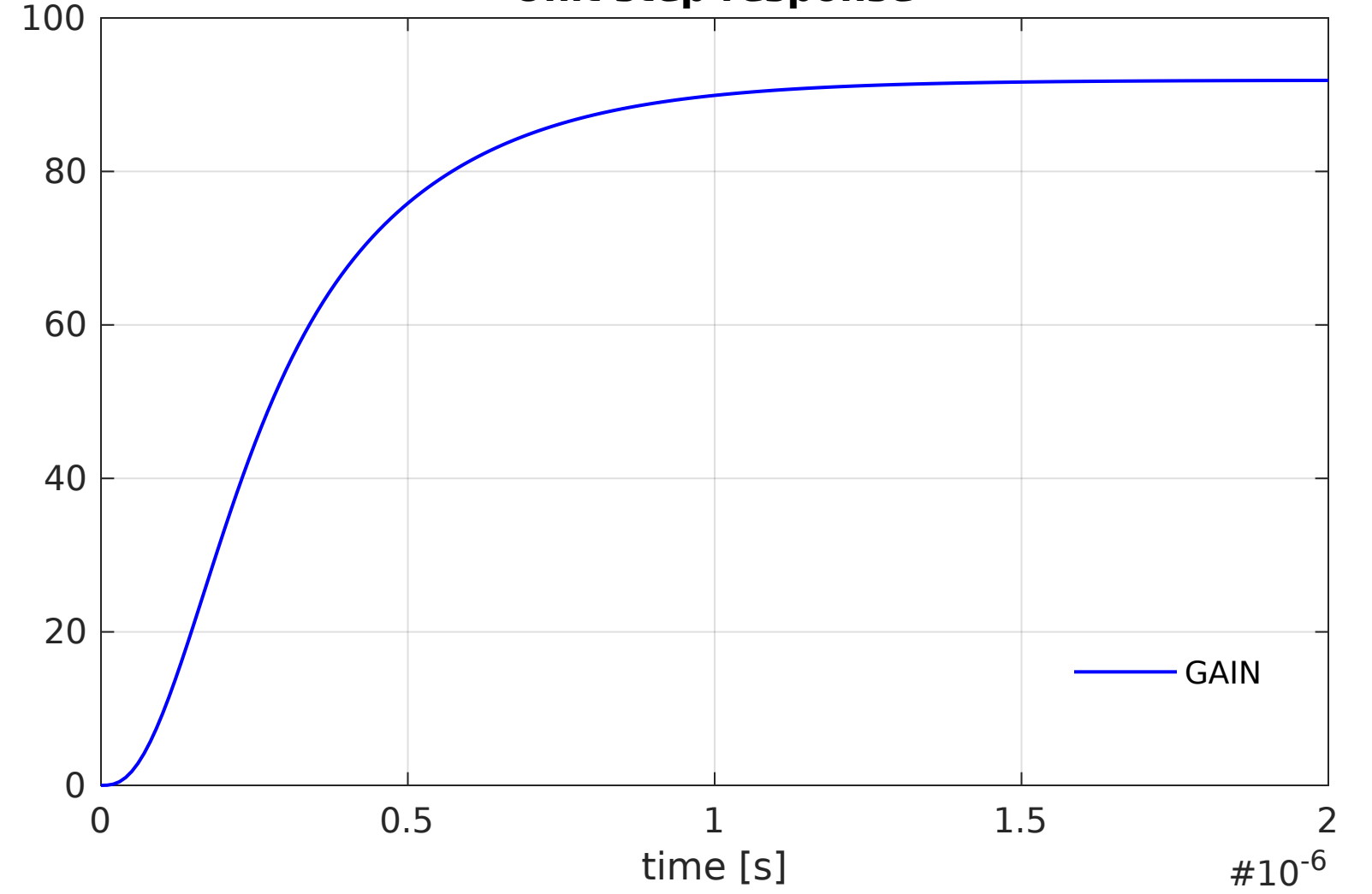


Compensated amplifier


Construction

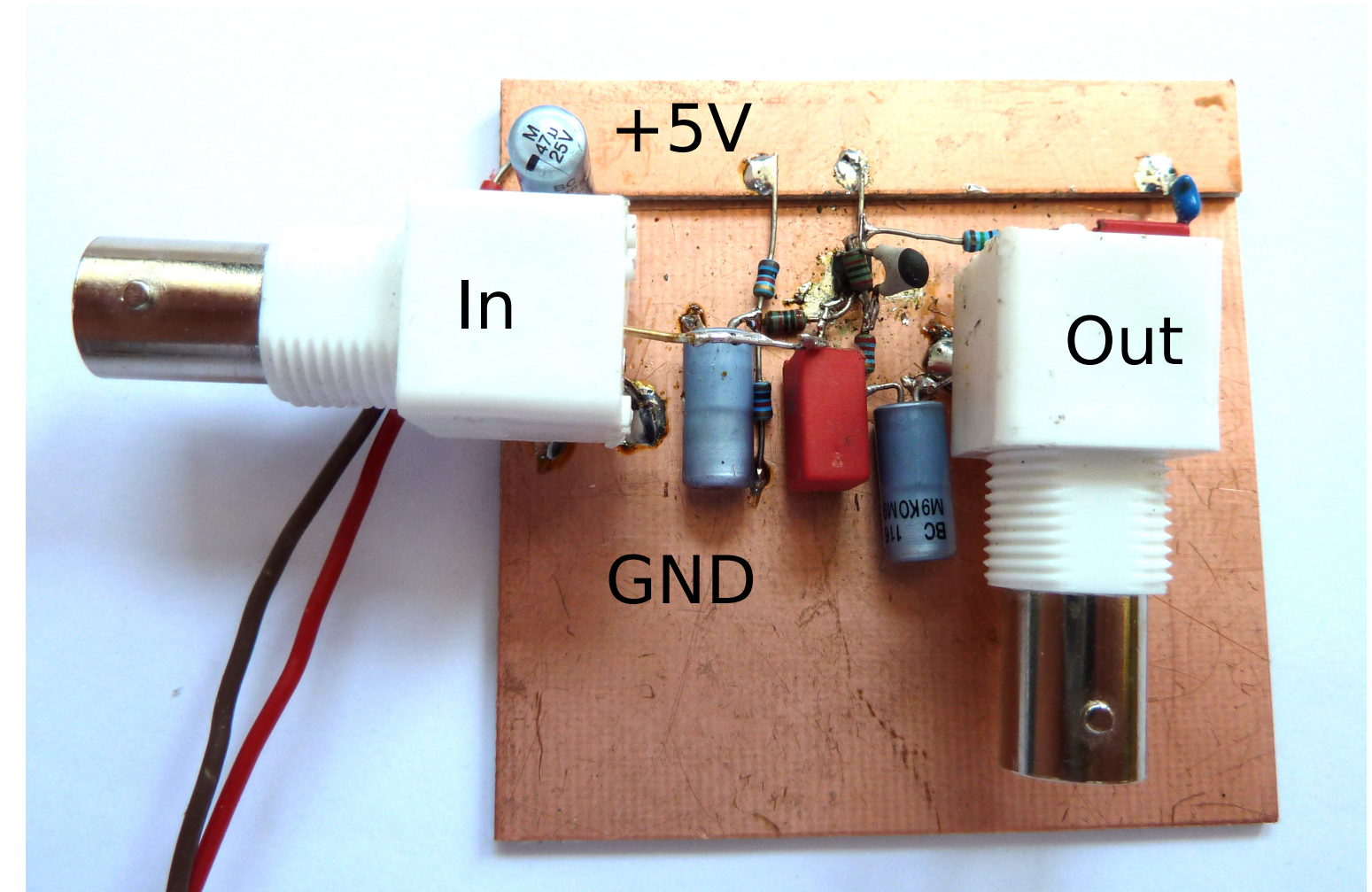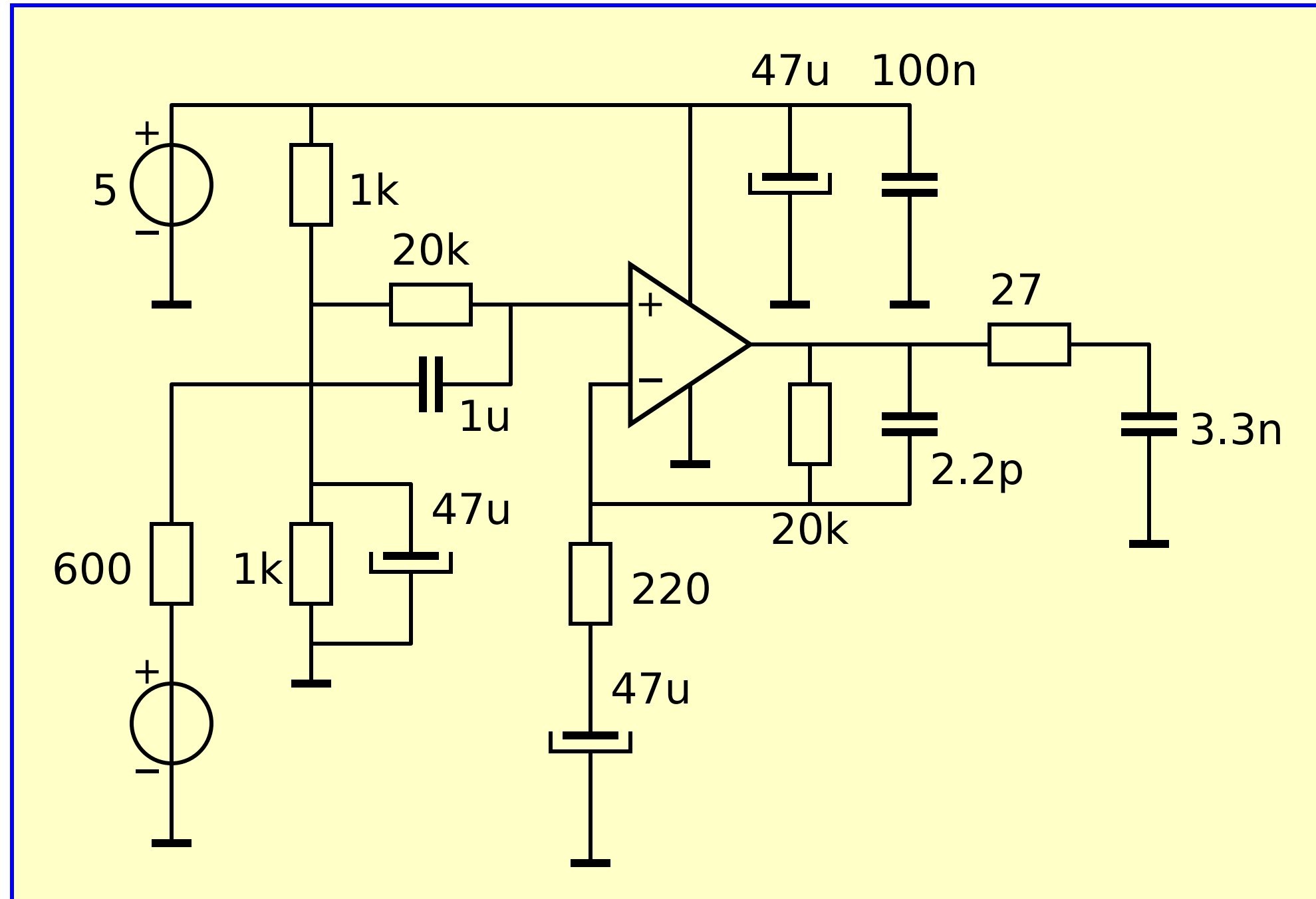


Test results

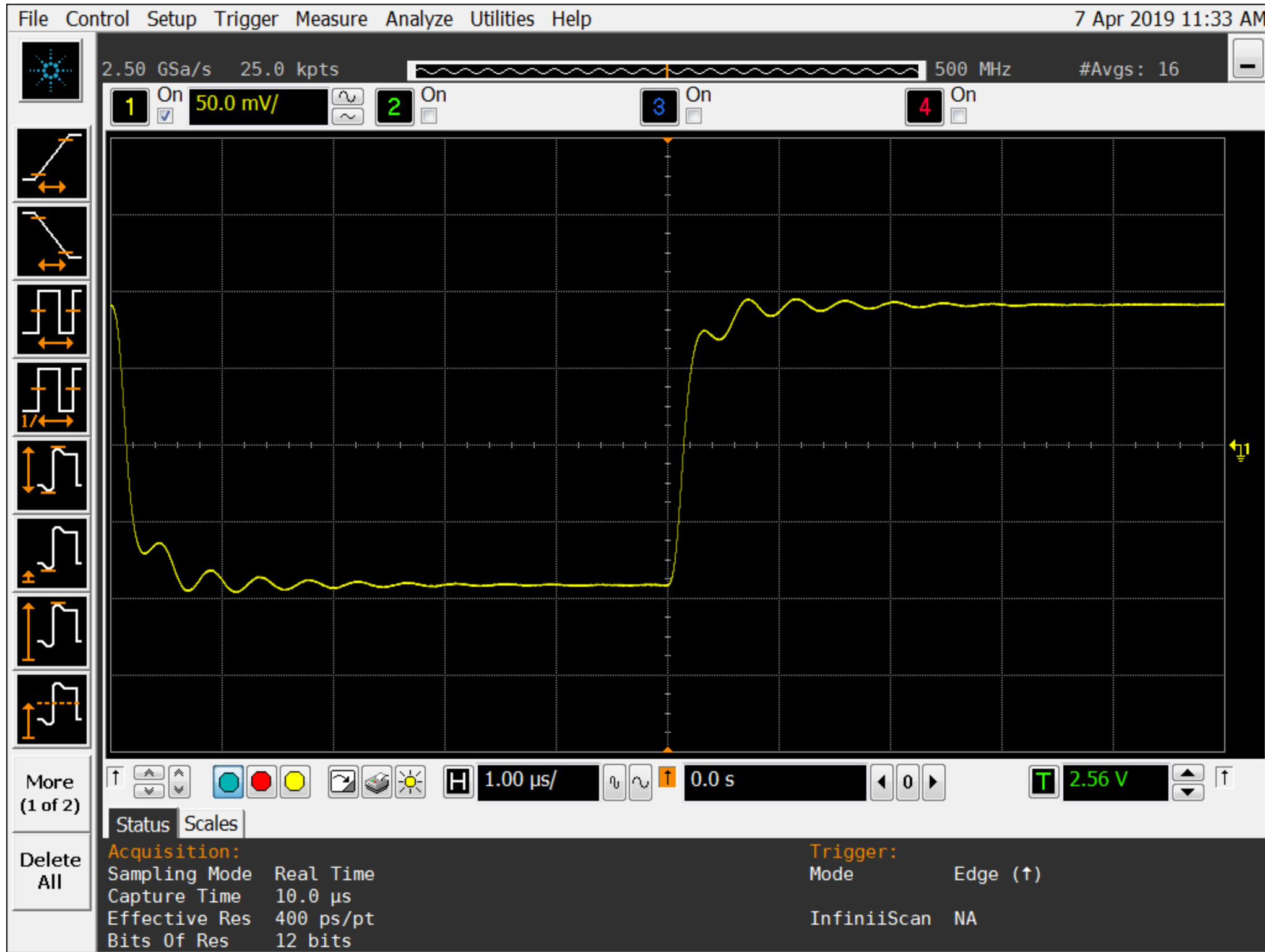

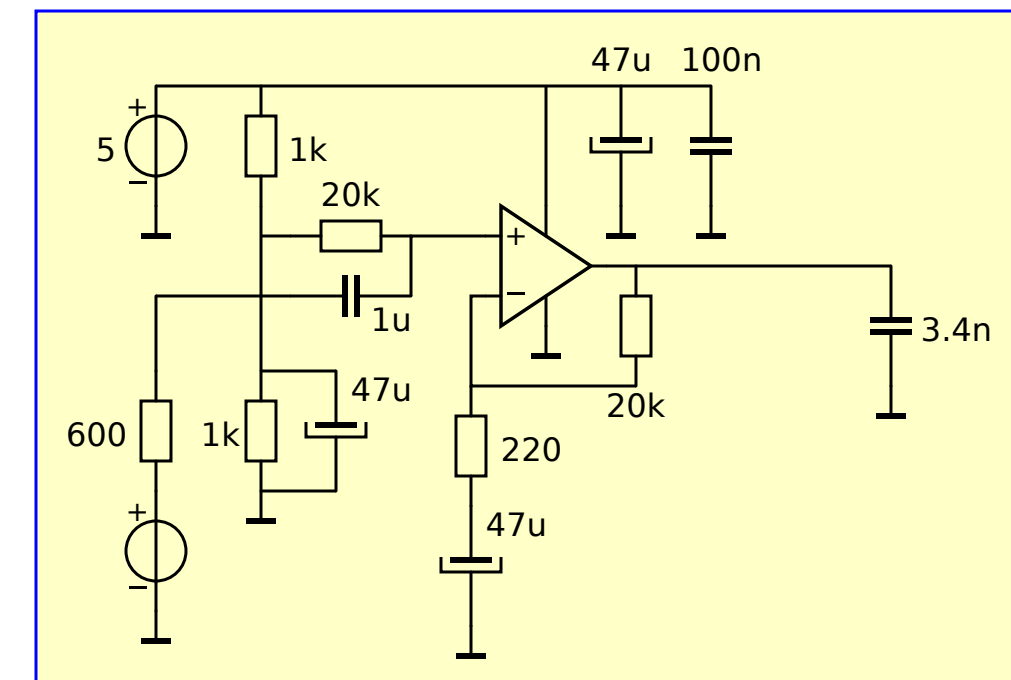
Small-signal step response
Source: 2mV_{pp} , 100kHz, 50%
Uncompensated amplifier
Total load capacitance 3.4nF




Test results

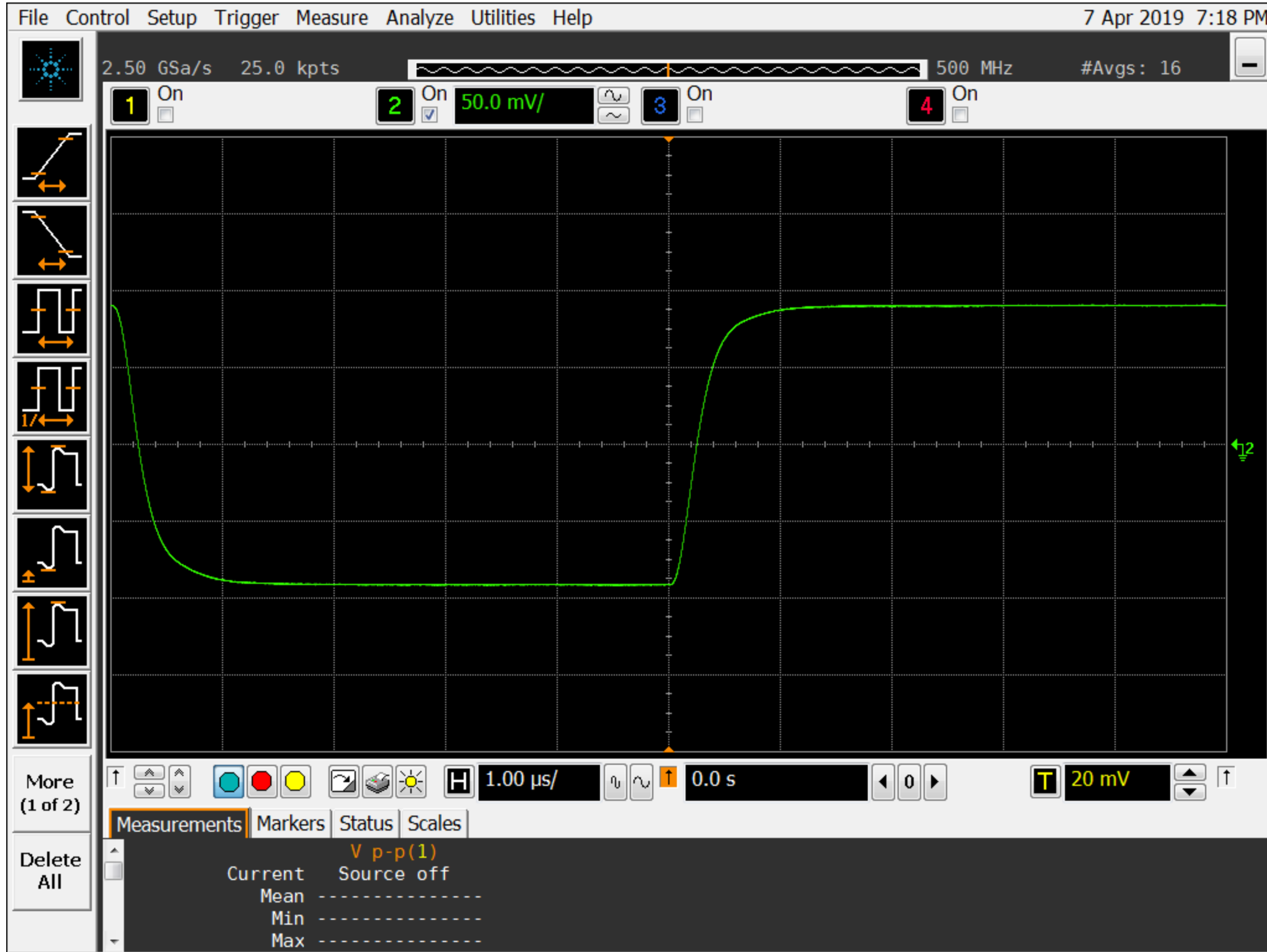

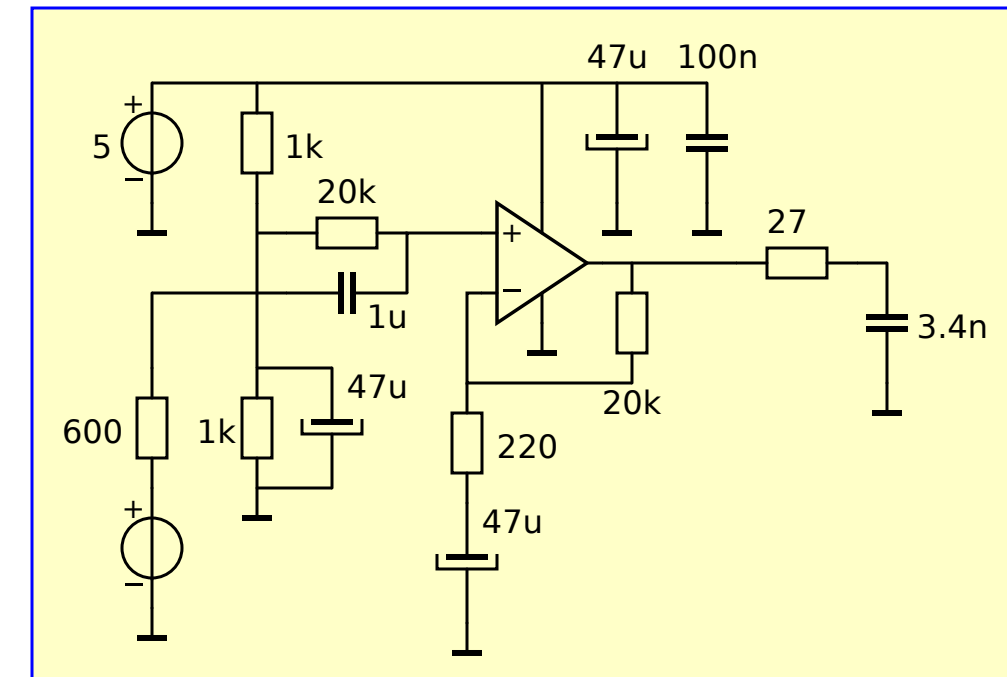
Small-signal step response
Source: 2mV_{pp}, 100kHz, 50%
Partly compensated amplifier
Total load capacitance 3.4nF




Test results

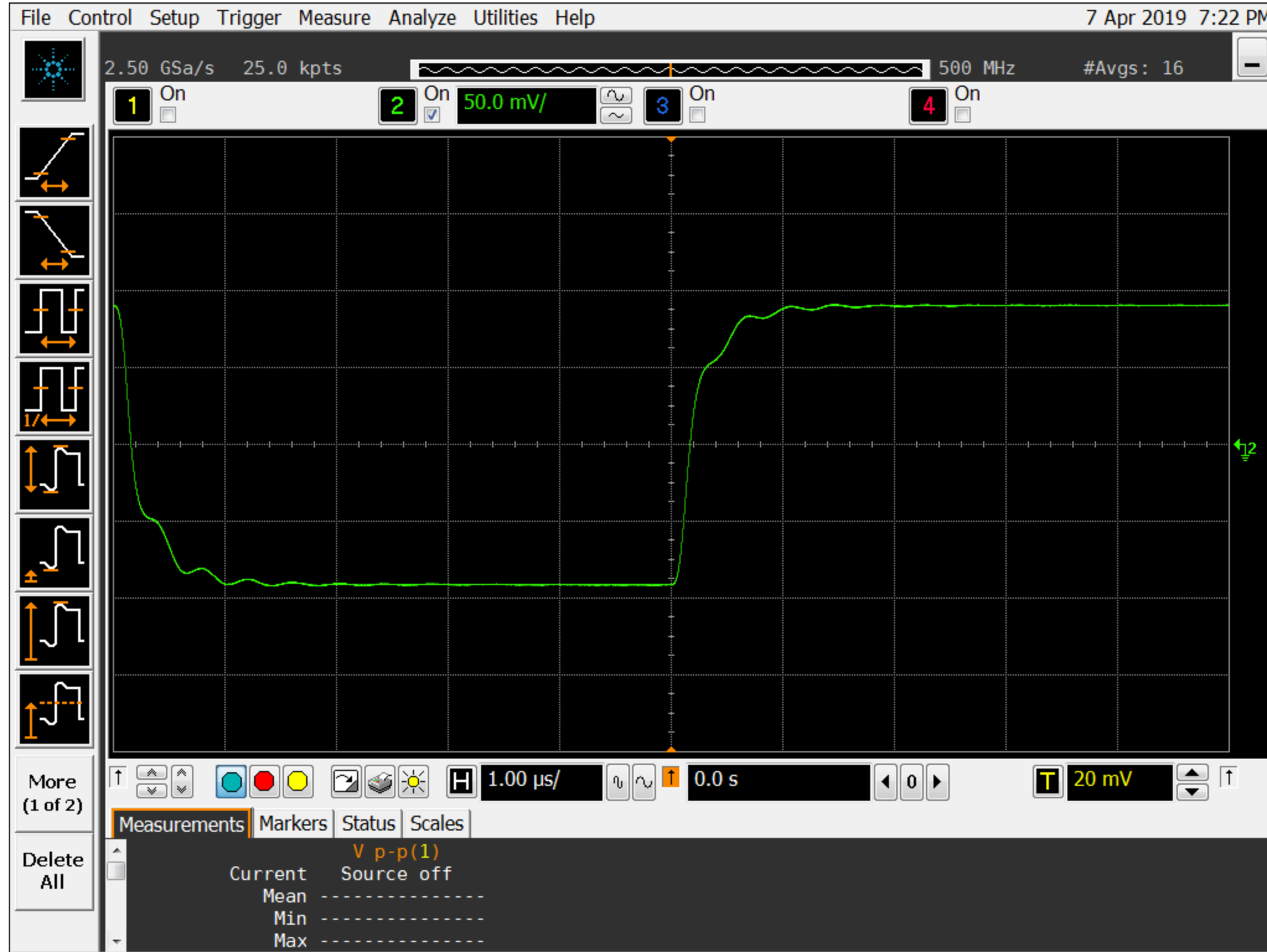

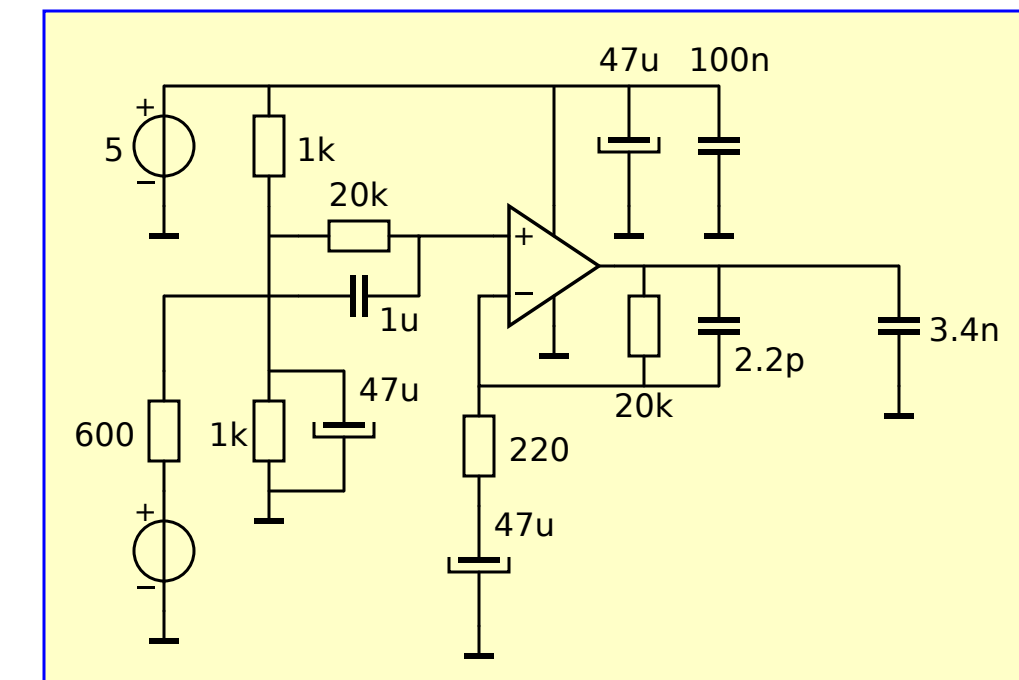
Small-signal step response
Source: 2mV_{pp}, 100kHz, 50%
Partly compensated amplifier
Total load capacitance 3.4nF




Test results

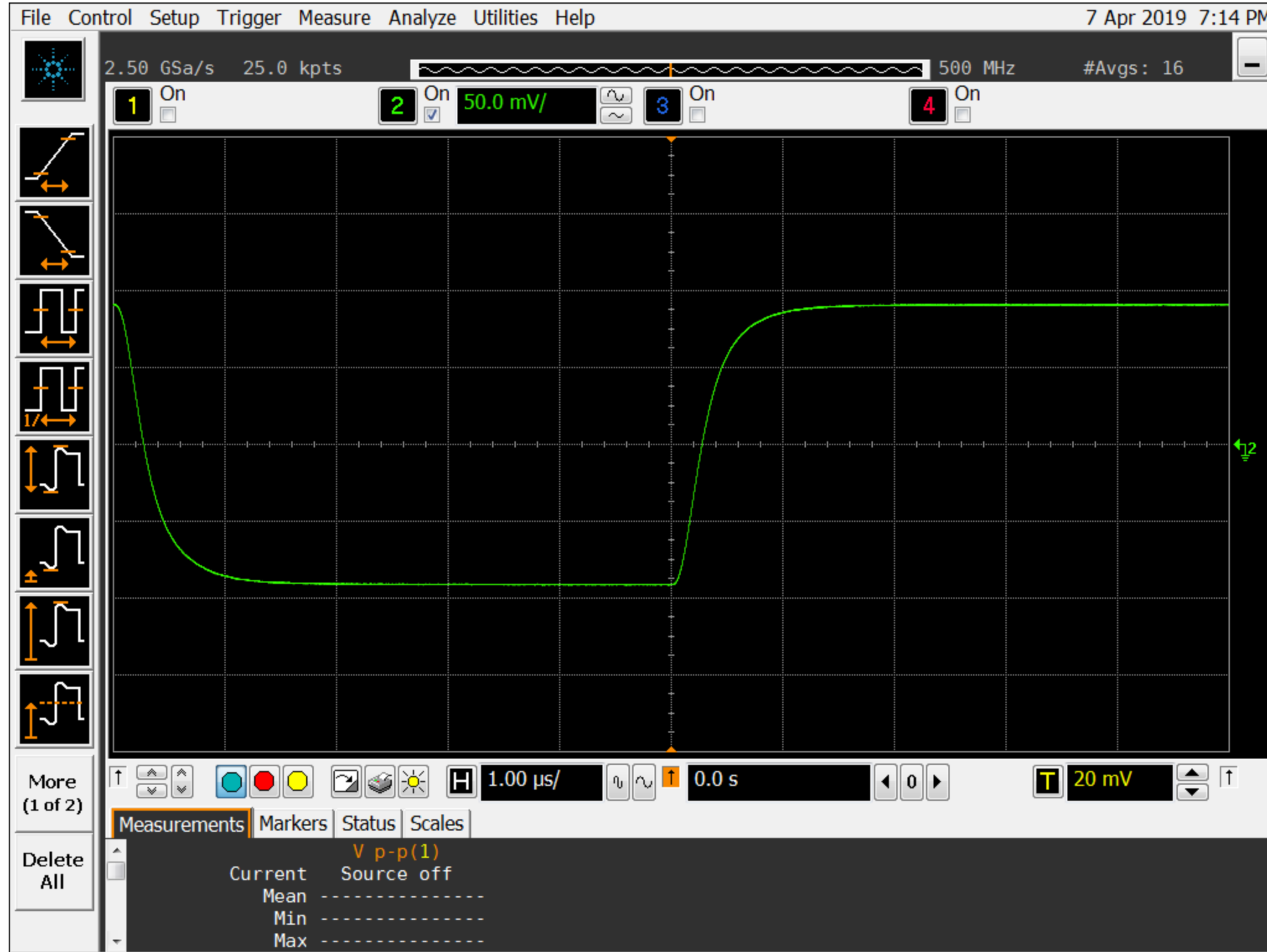

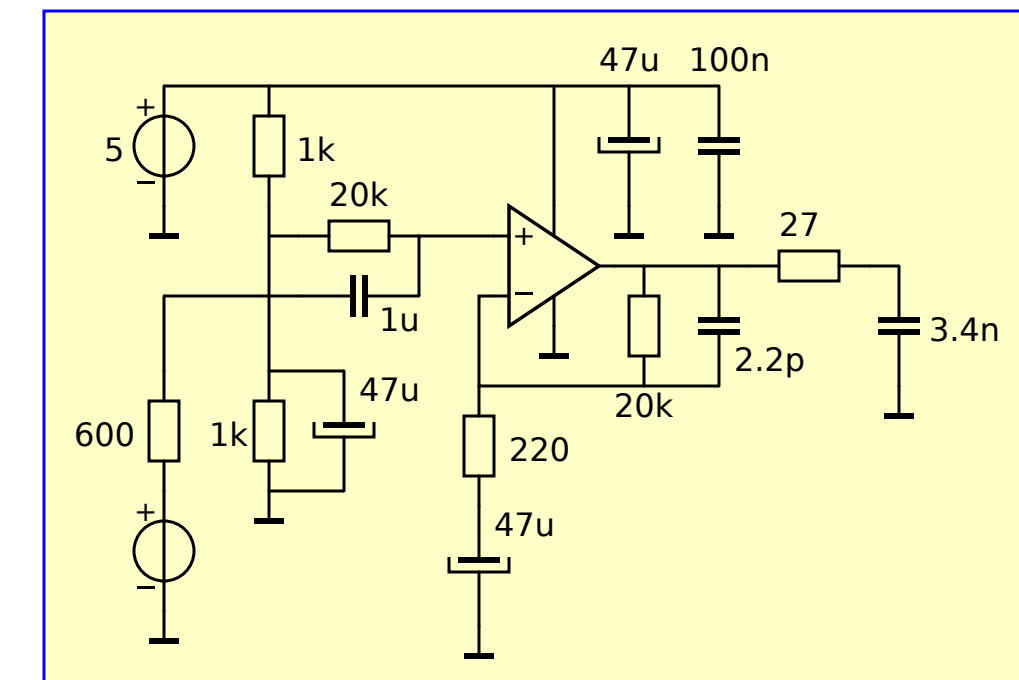Small-signal step response
Source: 2mV_{pp}, 100kHz, 50%
Compensated amplifier
Total load capacitance 3.4nF



Test results

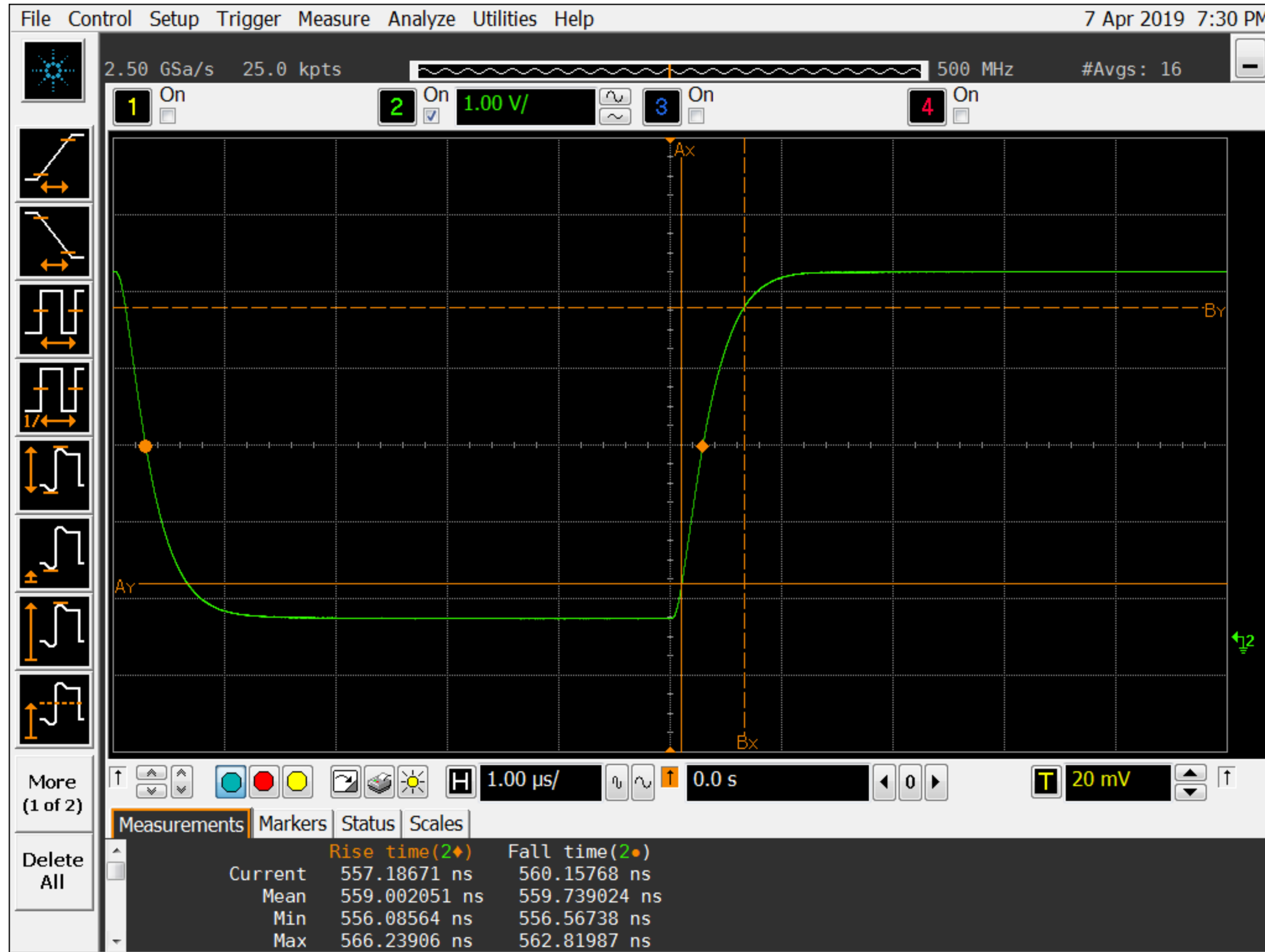


Large-signal step response


Source: 50mV_{pp} , 100kHz, 50%

Compensated amplifier

Total load capacitance 3.4nF

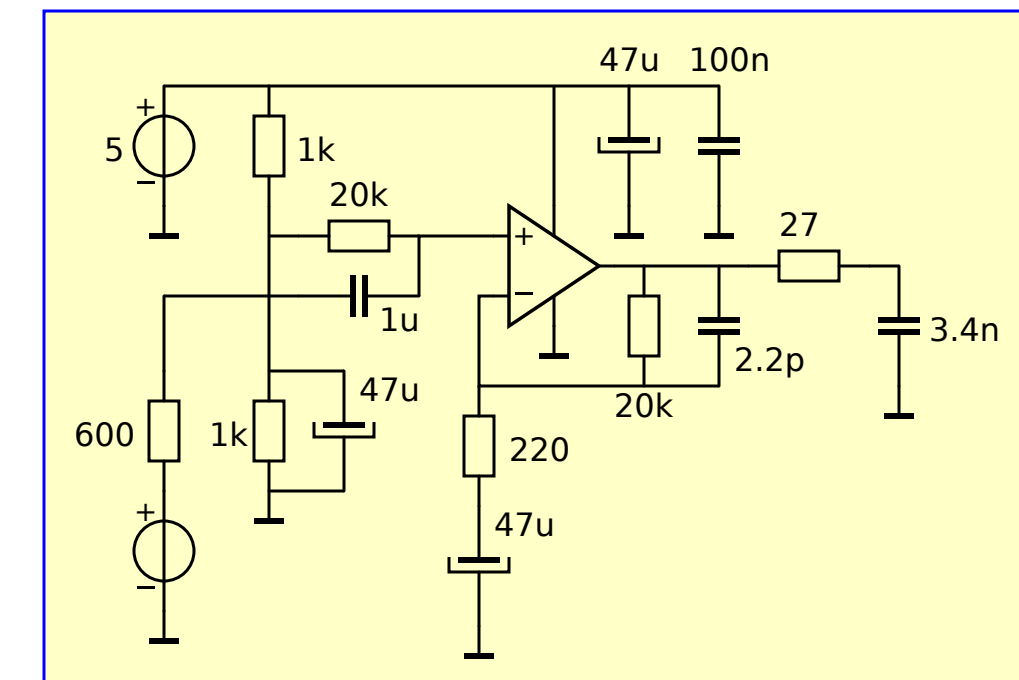

Test results

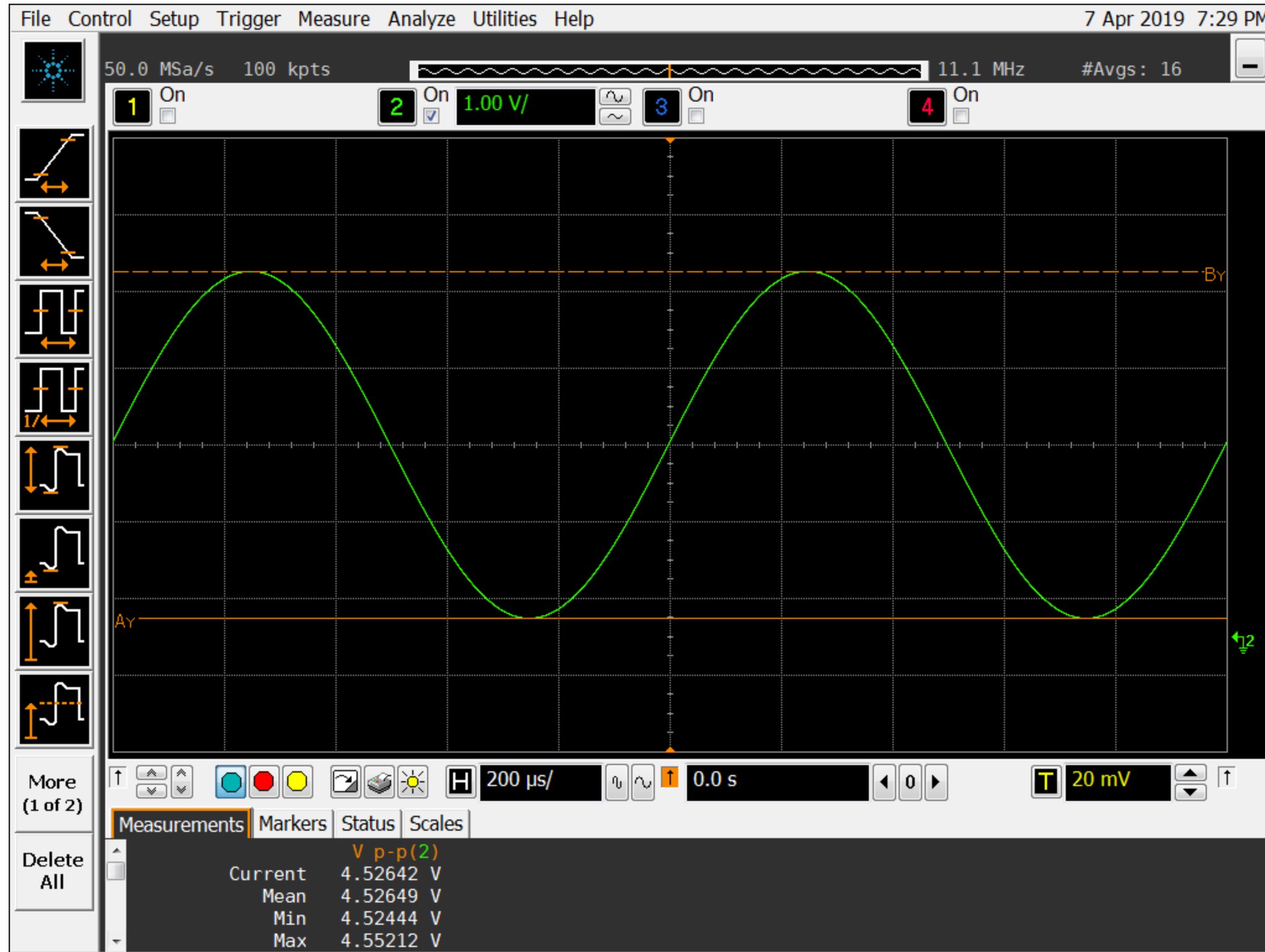


Large-signal sine response


Source: 50mV_{pp} , 100kHz

Compensated amplifier

Total load capacitance 3.4nF

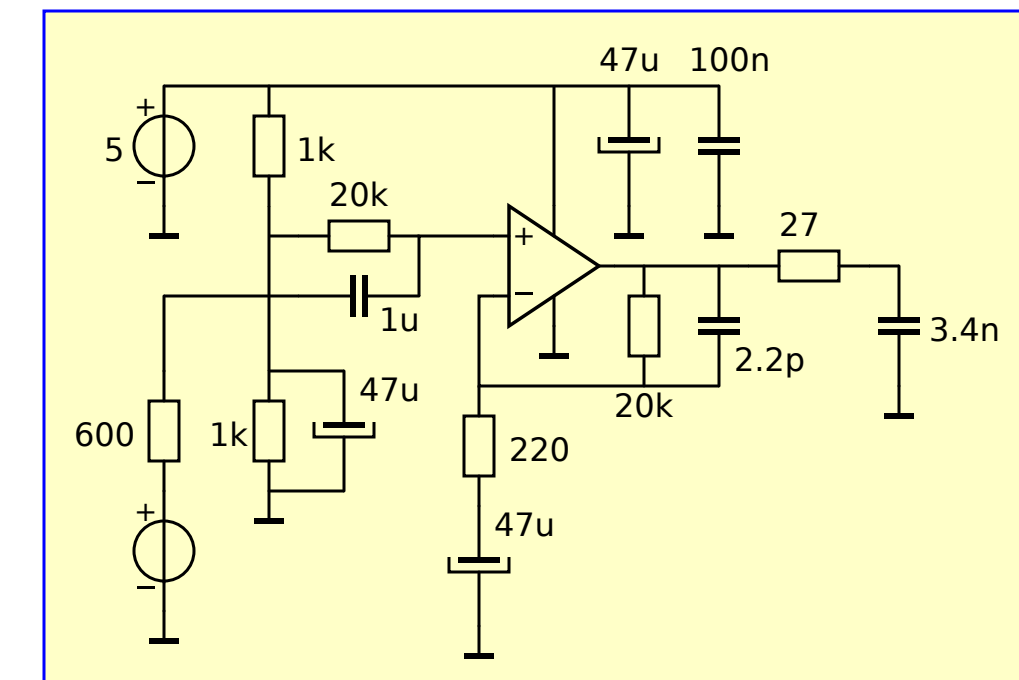

Test results

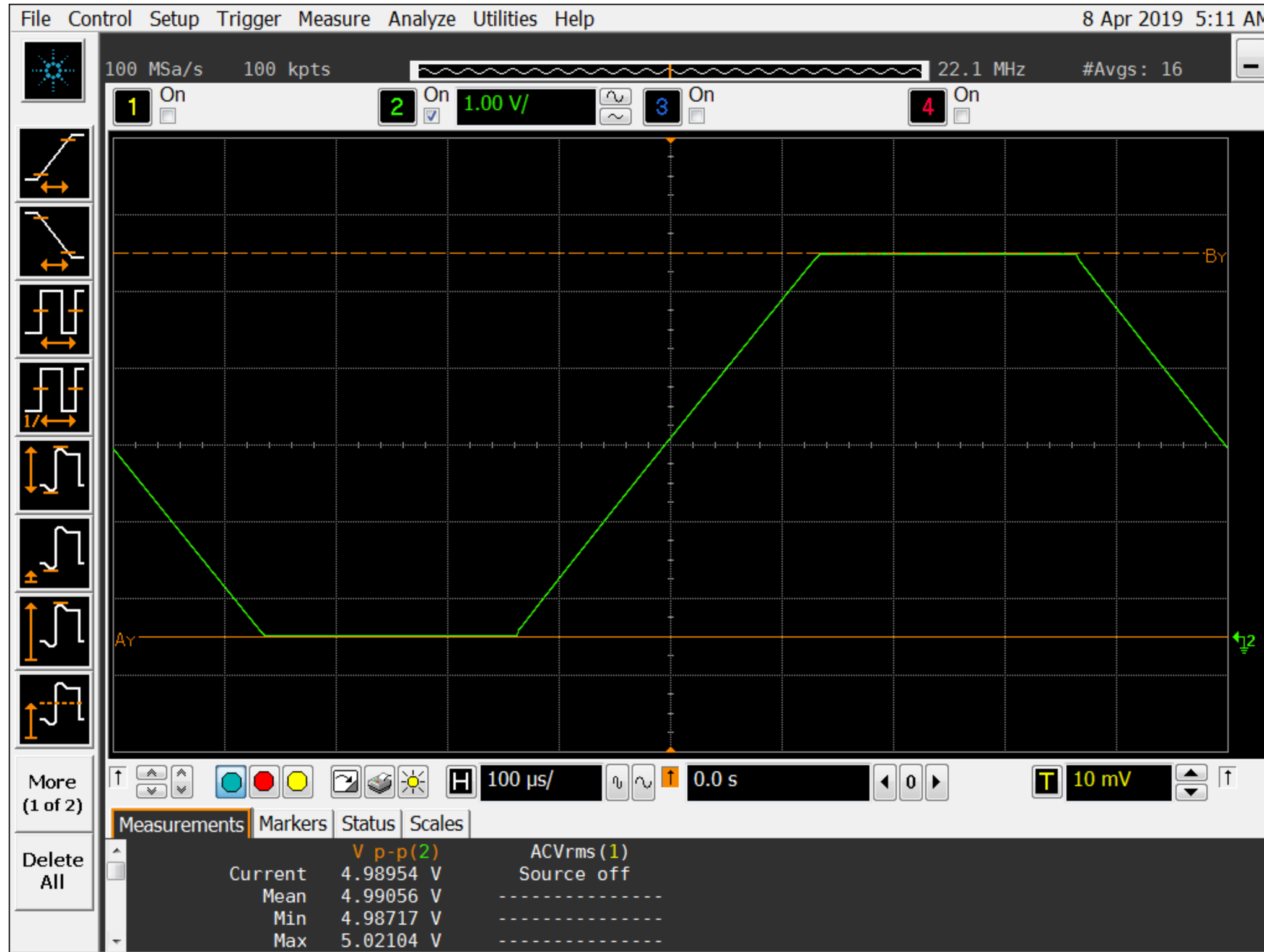


Large-signal overdrive

Source: 100mV_{pp} , 1kHz, triangle

Compensated amplifier

Total load capacitance 3.4nF

Source/sink voltage drop $< 10\text{mV}$

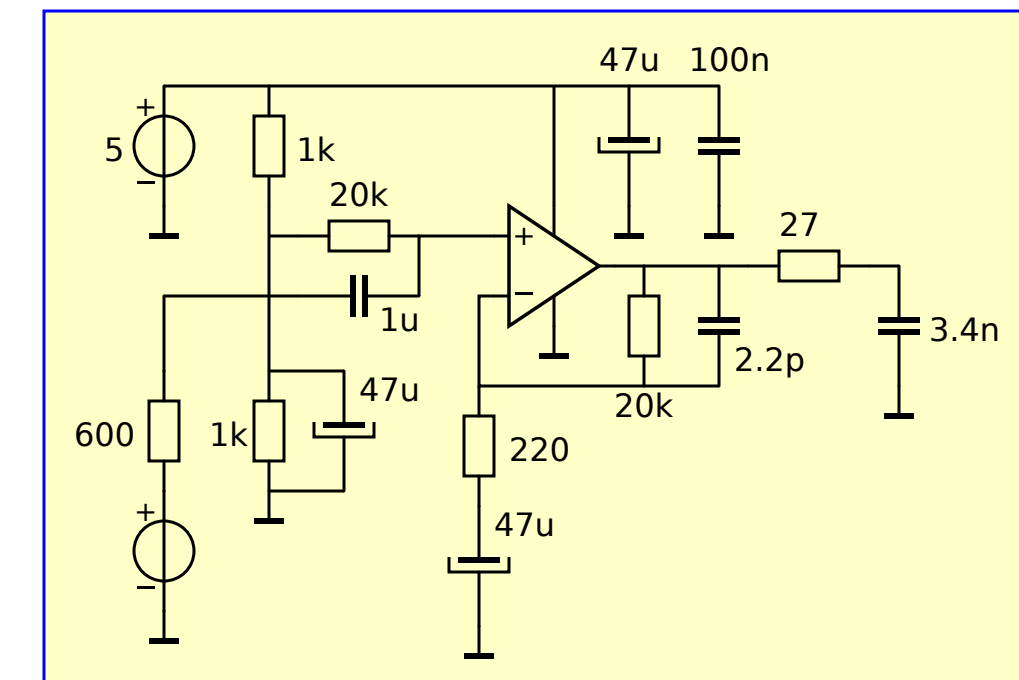

Test results




Small-signal transfer


HP4195A, source -40dBm

Compensated amplifier

Total load capacitance 3.4nF

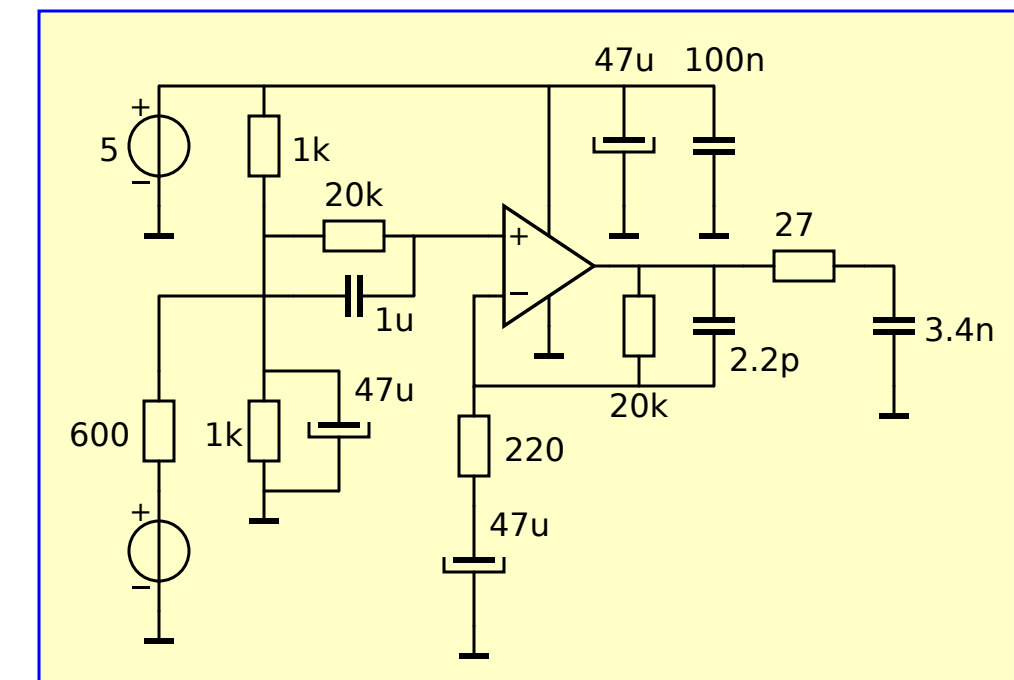

Test results

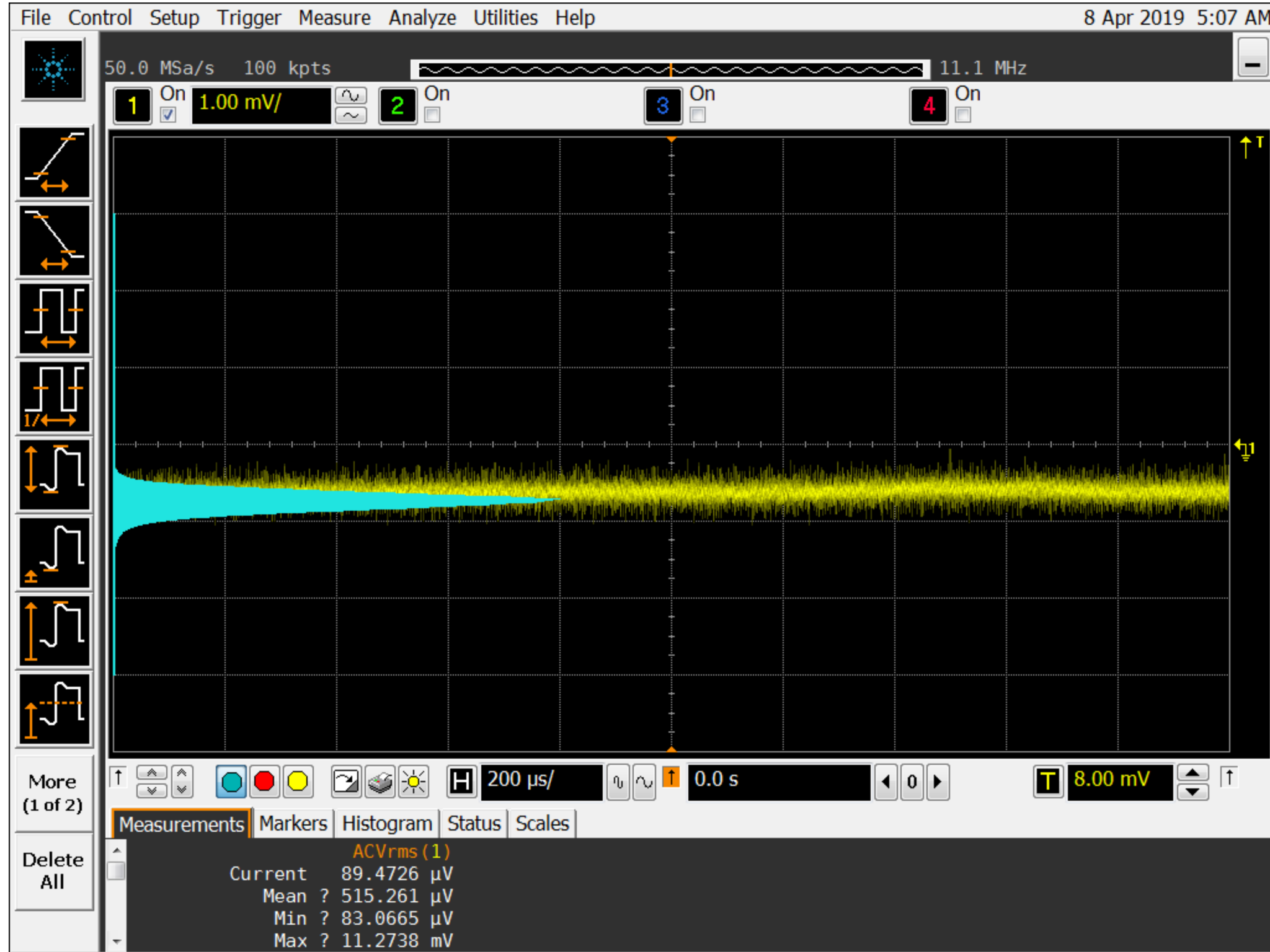


Oscilloscope noise

83uV RMS

Shorted input

Test results

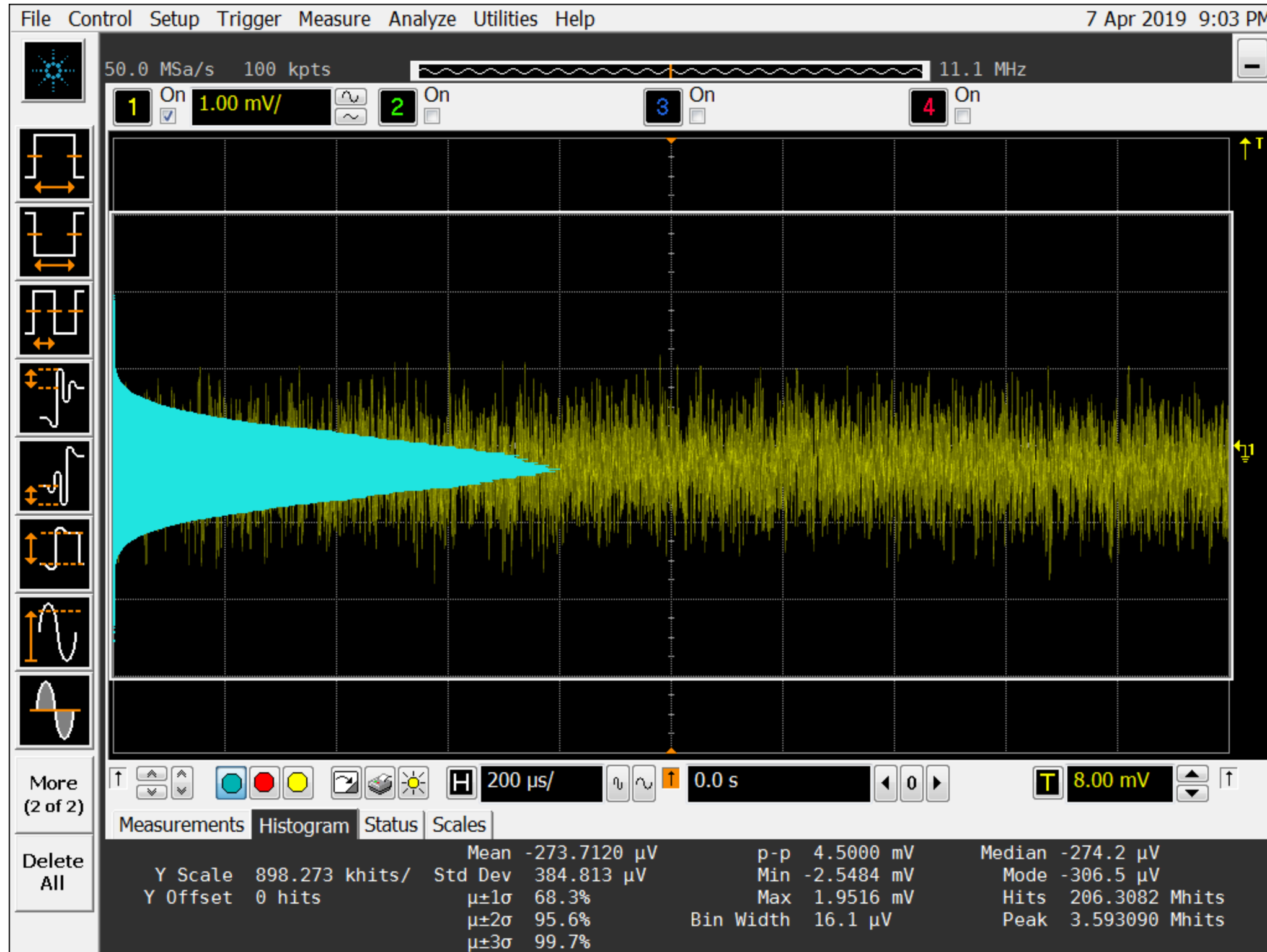

Output noise

385 μ V RMS


Compensated amplifier

Total load capacitance 3.4nF

Corrected for scope noise: 376 μ V

N=2.3dB @ 1MHz NBW

N=2.7dB @ 900kHz NBW

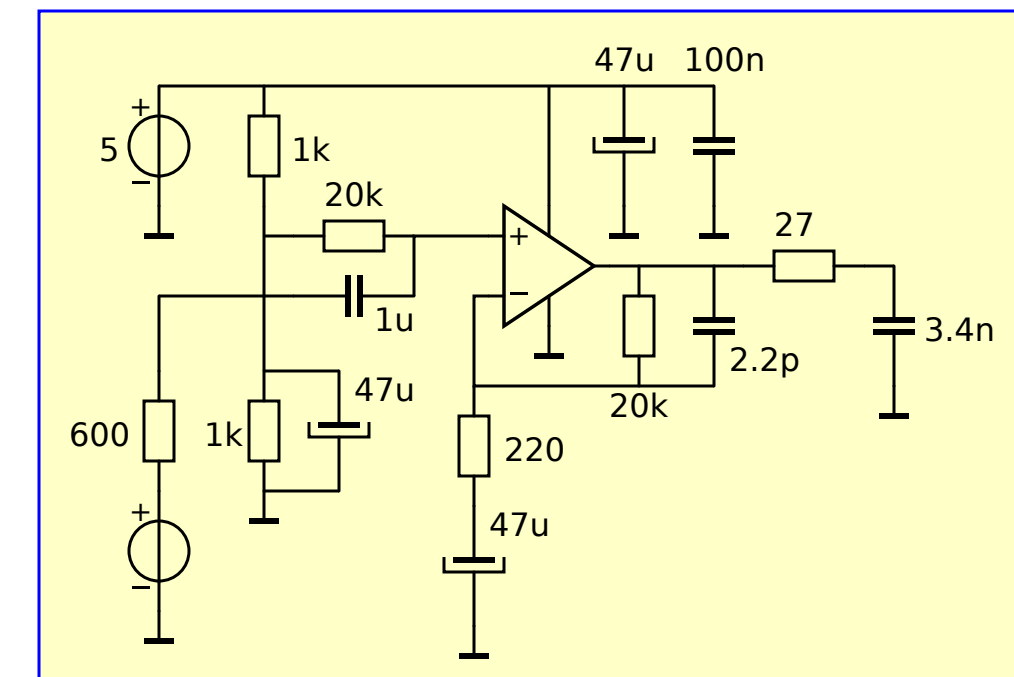

Conclusions and remarks

1. Amplifier performance complies with requirements
2. Spice simulation with TI macro model did not show small-signal instability
3. Modeling of individual performance aspects seems successful approach