


# **Structured Electronic Design**

EE3C11

Determination of T1 matrix parameters

*Anton J.M. Montagne*
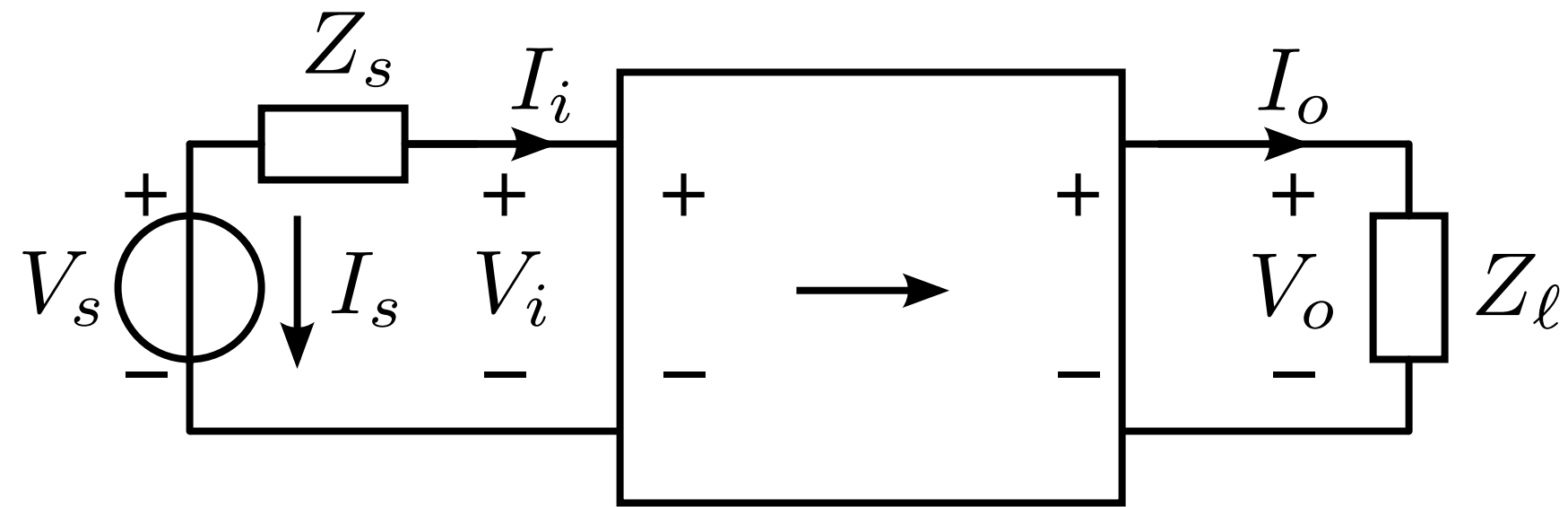
# Determination of the transmission-1 two-port parameters




$$I_i = -I_s$$

$$\mu = \frac{1}{A} = \frac{V_o}{V_i} \Big|_{I_o=0} \quad A = \lim_{Z_\ell \rightarrow \infty} \left( \frac{V_i}{V_o} \right) \quad \zeta = \frac{1}{C} = \frac{V_o}{I_i} \Big|_{I_o=0} \quad C = \lim_{Z_\ell \rightarrow \infty} \left( \frac{I_i}{V_o} \right)$$

$$\gamma = \frac{1}{B} = \frac{I_o}{V_i} \Big|_{V_o=0} \quad B = \lim_{Z_\ell \rightarrow 0} \left( \frac{V_i}{V_o} \right) \quad \alpha = \frac{1}{D} = \frac{I_o}{I_i} \Big|_{V_o=0} \quad D = \lim_{Z_\ell \rightarrow 0} \left( \frac{I_i}{I_o} \right)$$

# Example

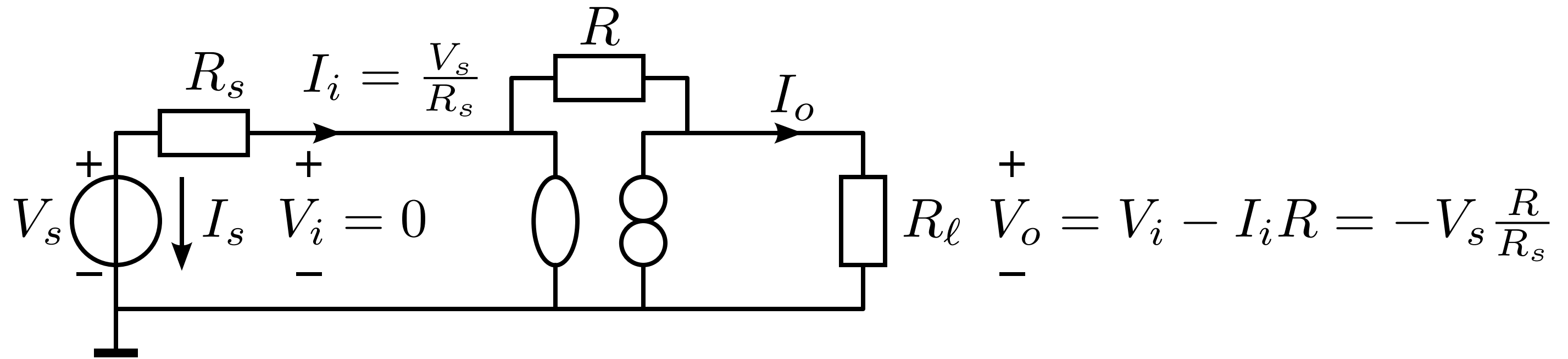


$$A = \lim_{R_\ell \rightarrow \infty} \left( \frac{V_i}{V_o} \right) = 0$$

$$C = \lim_{R_\ell \rightarrow \infty} \left( \frac{I_i}{V_o} \right) = \frac{\frac{V_s}{R_s}}{-V_s \frac{R}{R_s}} = -\frac{1}{R}$$

$$B = \lim_{R_\ell \rightarrow 0} \left( \frac{V_i}{V_o} \right) = 0$$

$$D = \lim_{R_\ell \rightarrow 0} \left( \frac{I_i}{I_o} \right) = 0$$

# Example

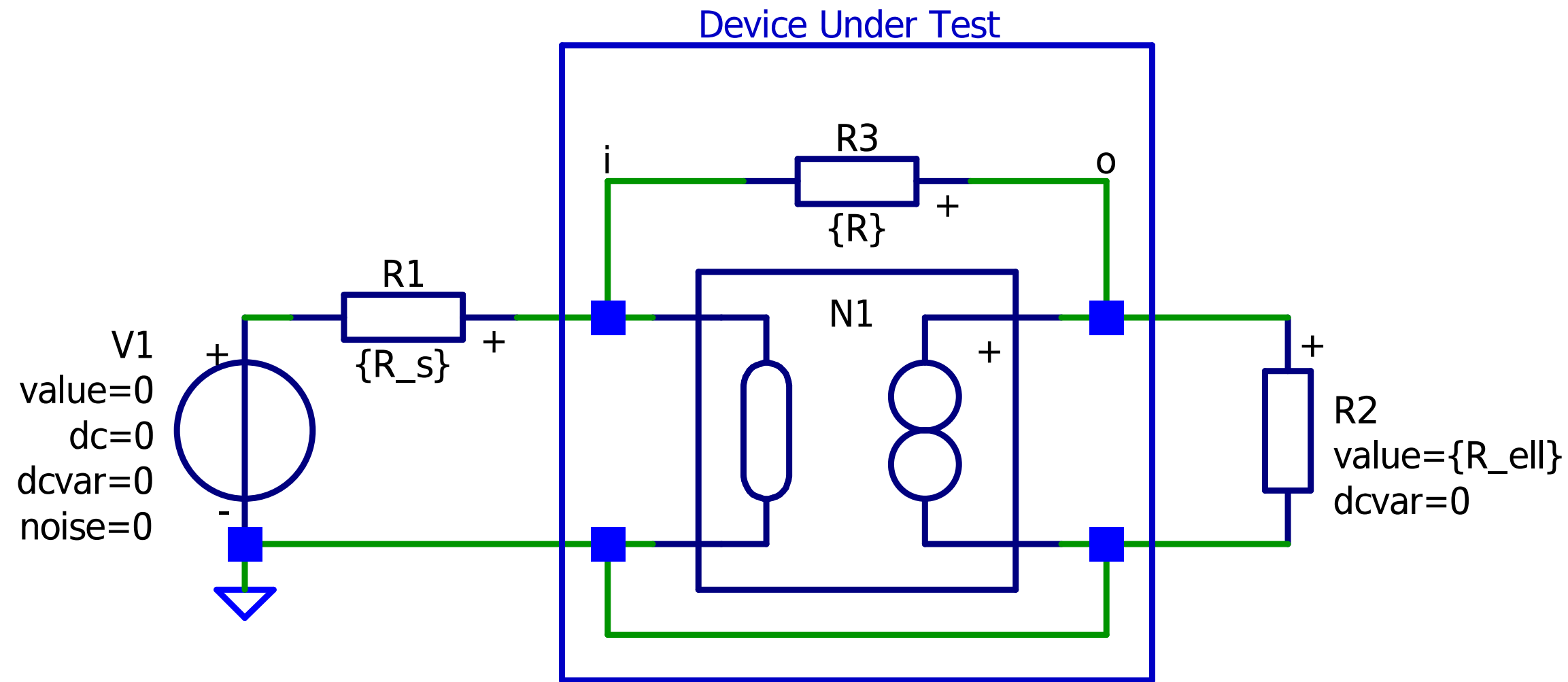

note: R2 is resistor model R\_r

It has the matrix stamp of a voltage source with zero voltage in series with a resistor

It adds its current to the vector with unknown variables

```

from SLiCAP import *
fileName = 'ABCD-test'
prj = initProject(fileName)
i1 = instruction()
i1.setCircuit(fileName + '.cir')
i1.setSimType('symbolic')
i1.setGainType('gain')
i1.setDataTypes('laplace')
i1.setSource('V1')
R_ell = sp.Symbol('R_ell')
V_i = i1.setDetector('V_i')
result = i1.execute()
V_i = result.laplace
I_i = i1.setDetector('I_V1')
result = i1.execute()
I_i = -result.laplace
V_o = i1.setDetector('V_o')
result = i1.execute()
V_o = result.laplace
I_o = i1.setDetector('I_R2')
result = i1.execute()
I_o = result.laplace
A = sp.limit(V_i/V_o, R_ell, 'oo')
B = sp.limit(V_i/I_o, R_ell, 0)
C = sp.limit(I_i/V_o, R_ell, 'oo')
D = sp.limit(I_i/I_o, R_ell, 0)
T1 = sp.Matrix([[A, B], [C, D]])

```